

Electric Vehicle (EE60082)


Lecture 10: Motor drive for EV (part 6)

DR. SHIMUL K. DAM

ASSISTANT PROFESSOR,
DEPARTMENT OF ELECTRICAL ENGINEERING,
INDIAN INSTITUTE OF TECHNOLOGY (IIT), KHARAGPUR.



Switching State Vectors (recap)

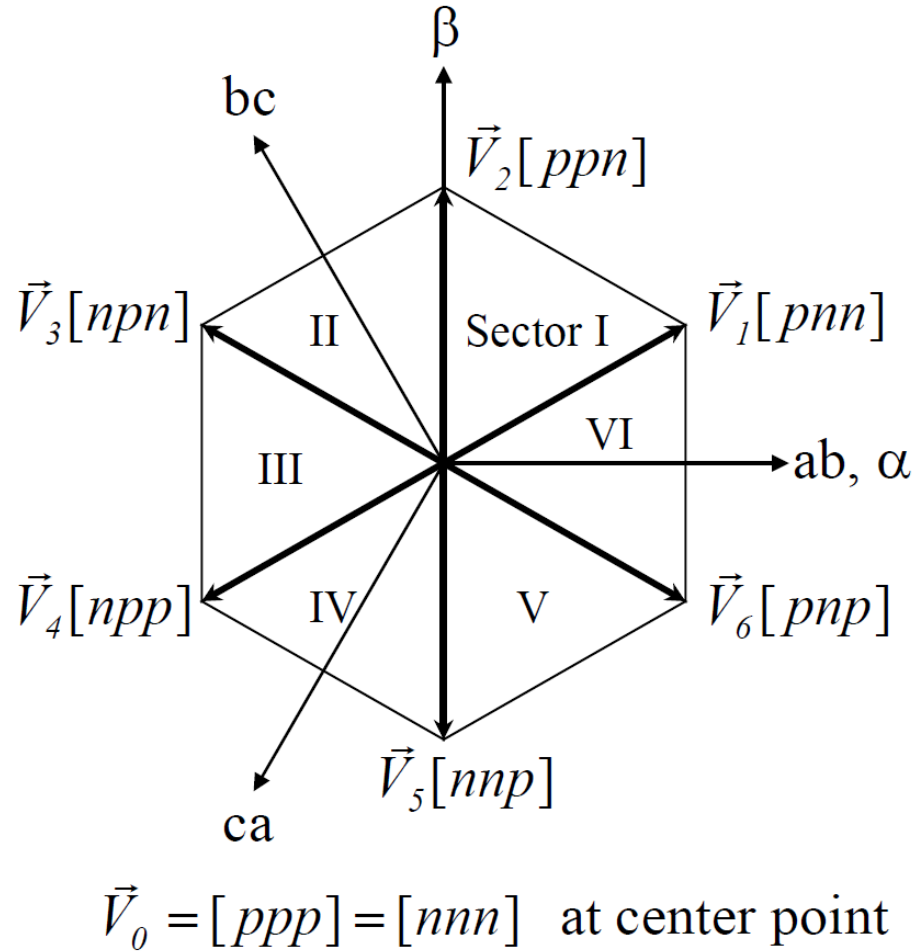


	ρ	$\theta (^\circ)$
$\vec{V}_1[pnn]$	$\sqrt{2} \cdot V_{dc}$	30
$\vec{V}_2[ppn]$		90
$\vec{V}_3[npn]$		150
$\vec{V}_4[npp]$		-150
$\vec{V}_5[nnp]$		-90
$\vec{V}_6[pnp]$		-30
$\vec{V}_0[ppp]$	0	0
$\vec{V}_0[nnn]$		0


Vector synthesis (recap)



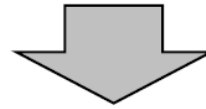Step 1 : Choose desired switching state vectors to synthesize \vec{V}_{ref}



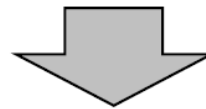Step 2 : Calculate the duty ratios of chosen switching state vectors




Step 3 : Make the sequence of chosen switching state vectors

Vector selection (recap)

- Minimize the number of switching
- Minimize the harmonic distortion


☞ **Nearest Three Vectors (NTV)**

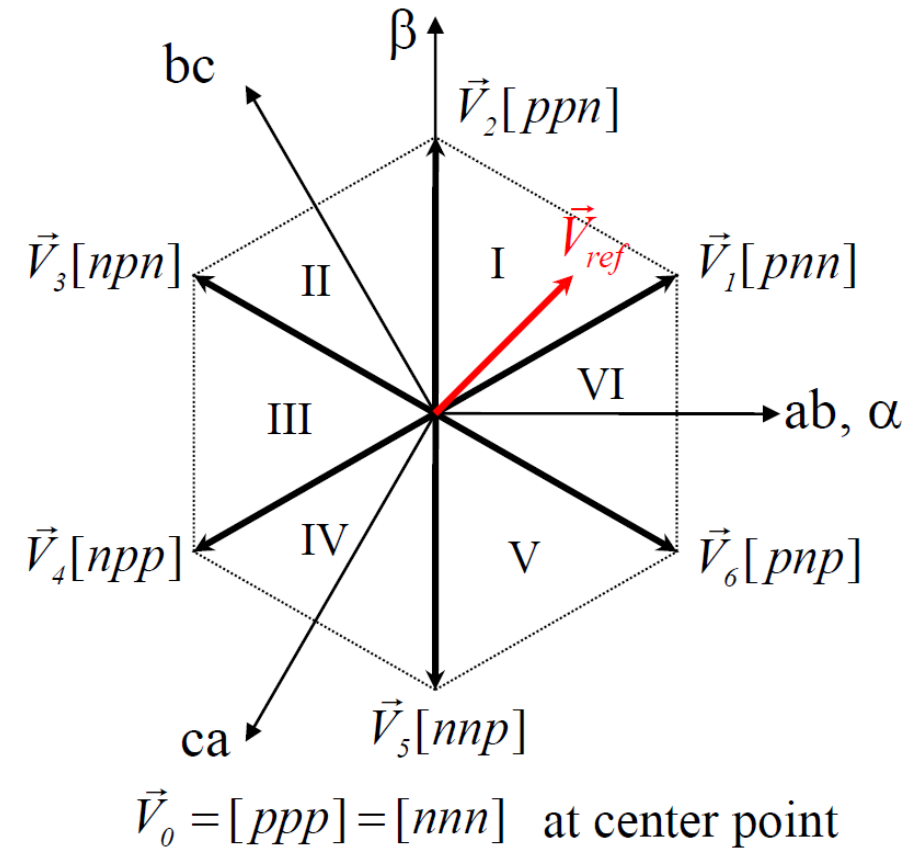


High frequency synthesis (recap)

$$\int_0^{T_S} \vec{V}_{ref} dt = \sum_i \left(\int_0^{T_i} \vec{V}_i dt \right), \quad \sum_i T_i = T_S$$

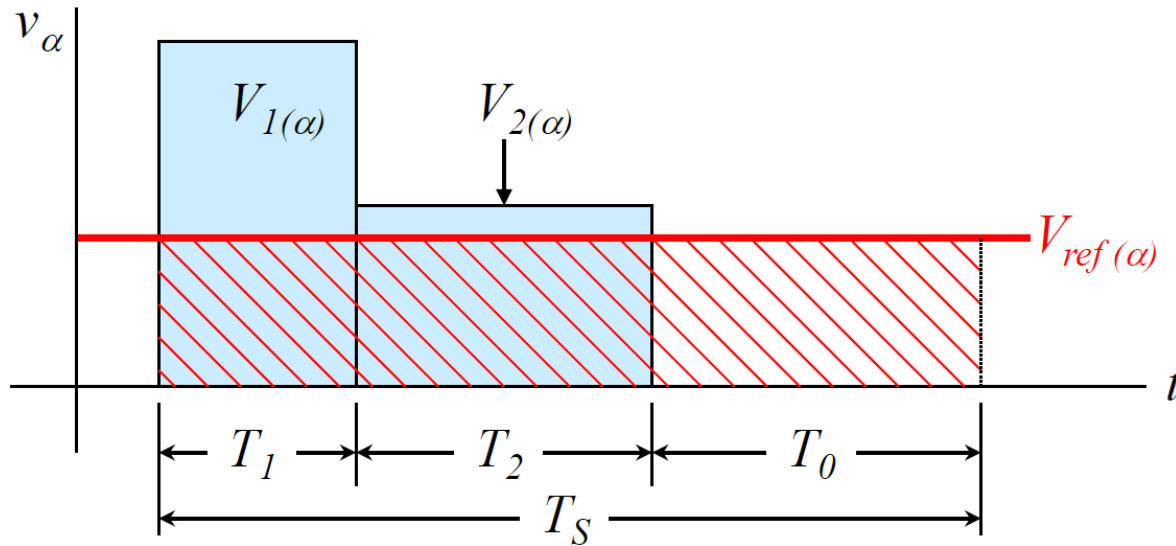For example
$$\int_0^{T_S} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_S} \vec{V}_0 dt$$



Total area of  = Area of 

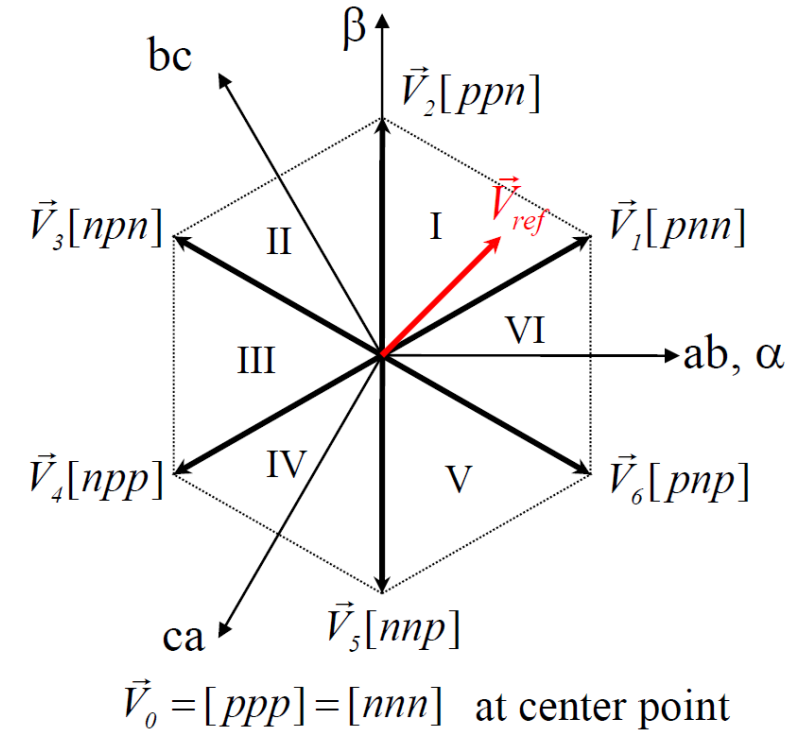

Duty ratio in sector I (recap)

From HF synthesis definition, $\int_0^{T_s} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_s} \vec{V}_0 dt$

Assume \vec{V}_{ref} is constant in T_s , $\vec{V}_{ref} \cdot T_s = \vec{V}_1 \cdot T_1 + \vec{V}_2 \cdot T_2$


$$\rho \cdot \begin{bmatrix} \cos \phi \\ \sin \phi \end{bmatrix} \cdot T_s = \|V_1\| \cdot \begin{bmatrix} 1 \\ 0 \end{bmatrix} \cdot T_1 + \|V_2\| \cdot \begin{bmatrix} \cos 60^\circ \\ \sin 60^\circ \end{bmatrix} \cdot T_2$$

where $\phi = \theta - 30^\circ$

$$\frac{T_1}{T_s} = d_1 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_1\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_2}{T_s} = d_2 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_2\|} \cdot \sin \phi$$

$$d_0 = 1 - d_1 - d_2$$

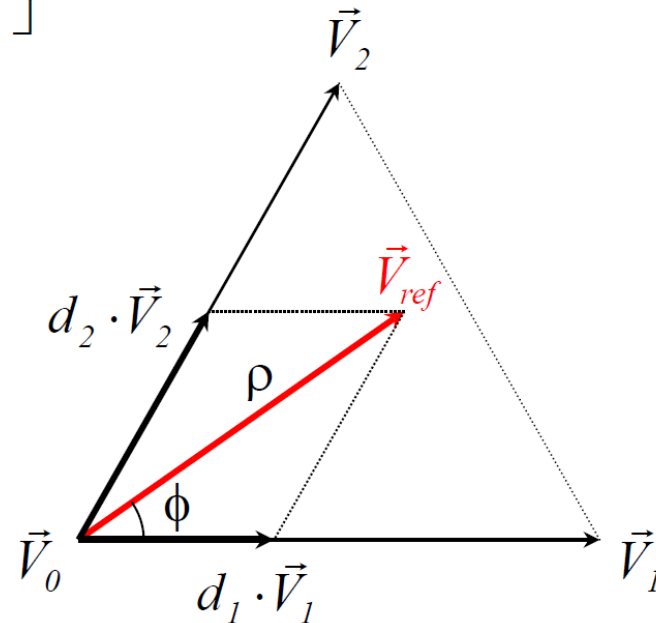

Duty ratio in other sectors (recap)


➡ Other sectors have the same results of duty ratio.

$$\frac{T_N}{T_S} = d_N = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_N\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_{N+1}}{T_S} = d_{N+1} = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_{N+1}\|} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

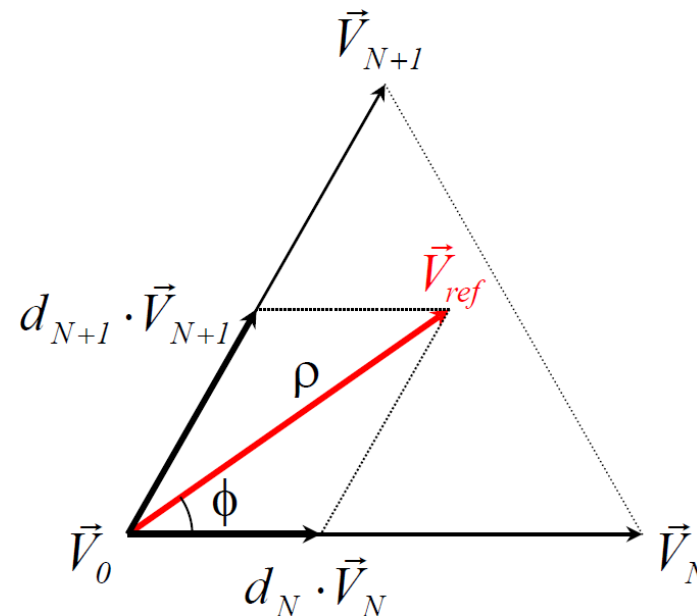where $\phi = \theta - (N-1) \cdot 60^\circ - 30^\circ$
 N : sector number (1 ~ 6)



$$\vec{V}_{ref(steady-state)} = \rho \cdot e^{j\theta} = \sqrt{\frac{3}{2}} \cdot V_m \cdot e^{j\omega t}$$

Modulation index (recap)

For all the switching state vectors, $\|V_N\| = \sqrt{2} \cdot V_{dc}$ and $\rho = \sqrt{\frac{3}{2}} \cdot V_m$

$$d_N = \frac{V_m}{V_{dc}} \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = \frac{V_m}{V_{dc}} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

Define the modulation index $M = \frac{V_m}{V_{dc}}$

$$d_N = M \cdot \sin(60^\circ - \phi)$$


$$d_{N+1} = M \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

Vector sequence – 3ph, symmetric (recap)



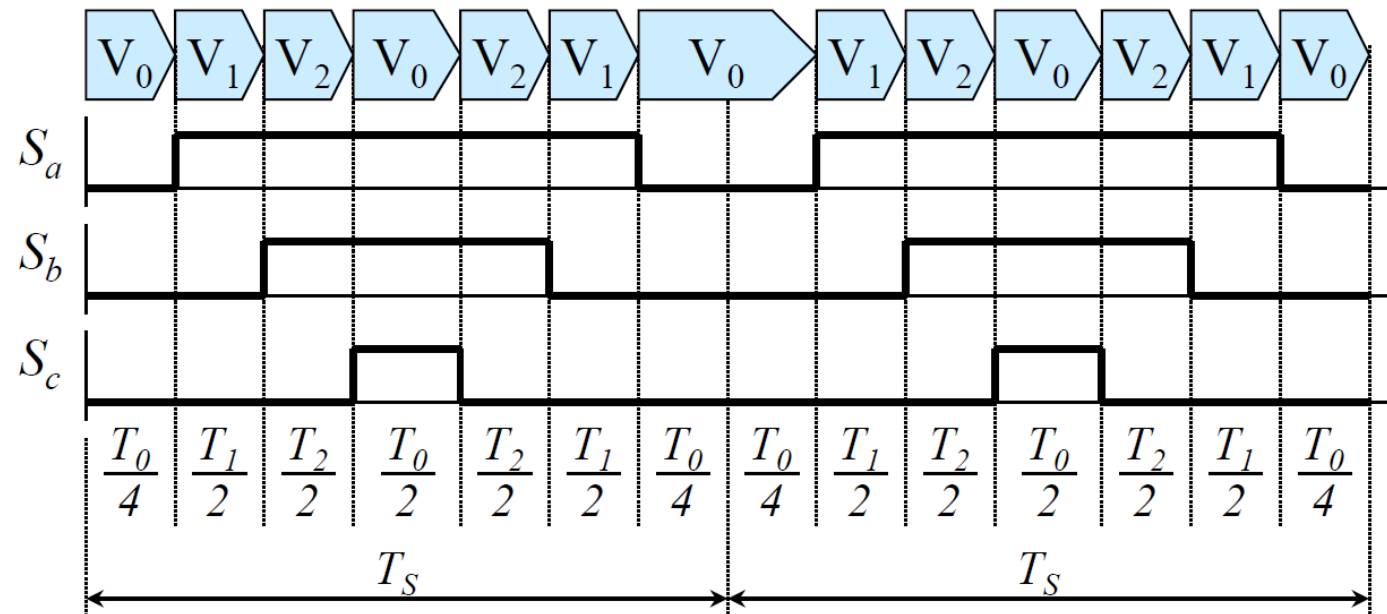
- Use both zero switching state vectors
- Symmetrical sequence \longrightarrow Low THD
- Six commutations per switching cycle



Vector sequence – 2ph, asymmetric (recap)



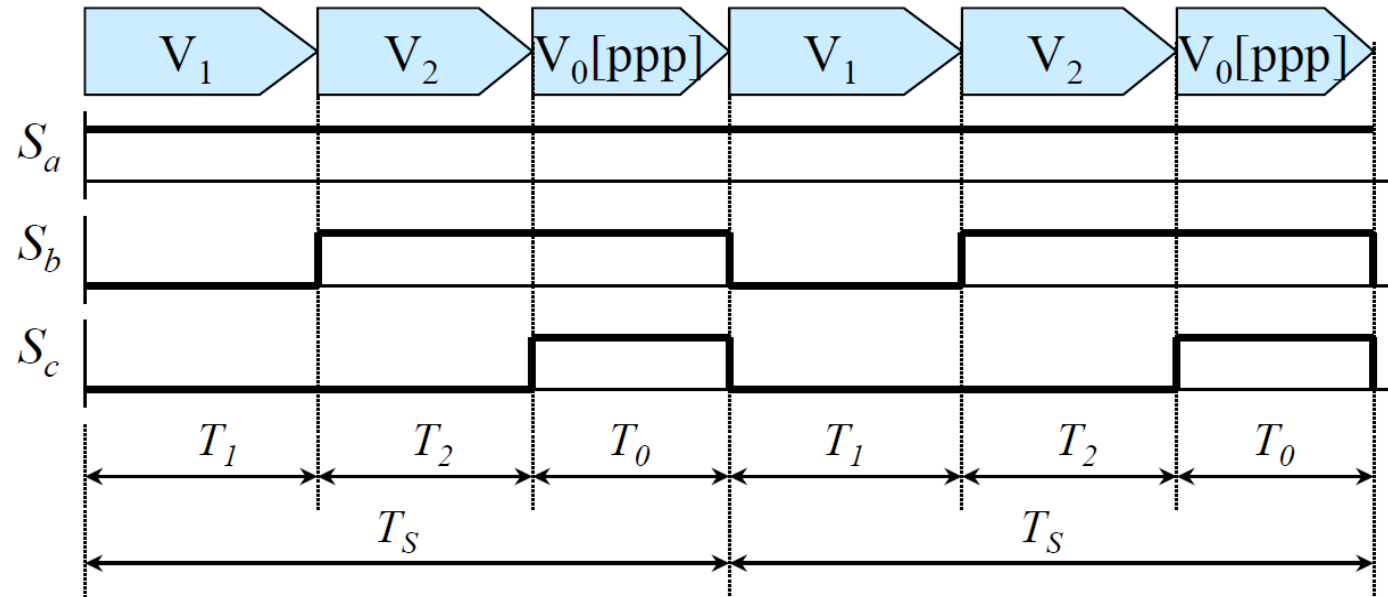
- Use a zero vector in one switching cycle $\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Asymmetrical sequence
- Four commutations \longrightarrow Reduced switching losses



Vector sequence – 2ph, symmetric (recap)



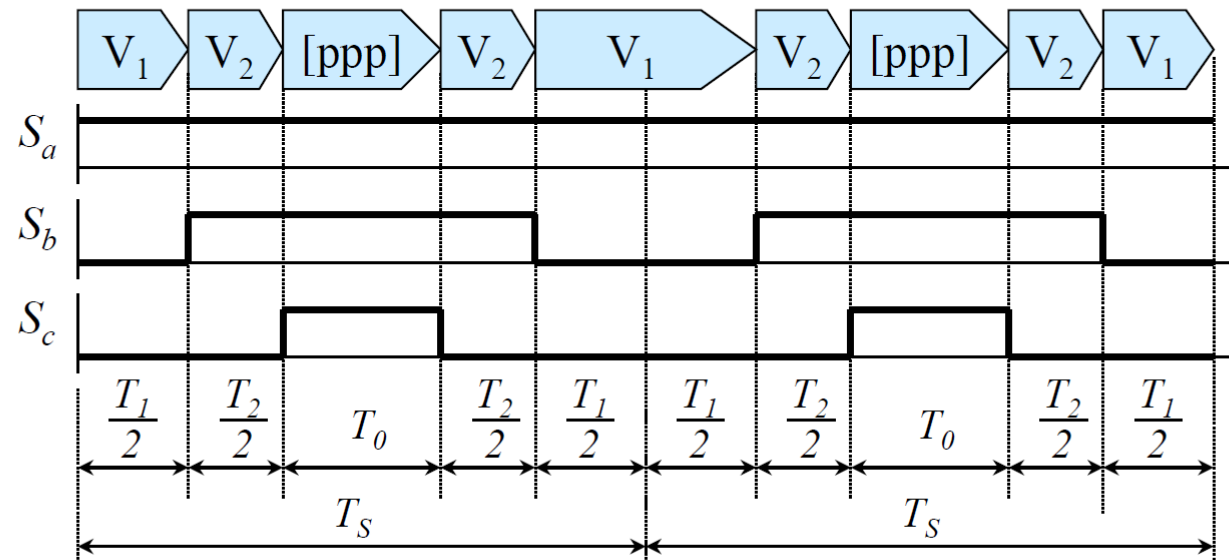- Use a zero vector in one switching cycle $\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Symmetrical sequence \longrightarrow Low THD
- Four commutations \longrightarrow Reduced switching losses



< Example in sector I >


AC voltage generation with space vector (recap)




Example:

- DC voltage, $V_{dc} = 400V$
- Switching frequency, $f_{sw} = 100 \text{ kHz}$
- Line frequency, $f_{line} = 100 \text{ Hz}$
- R-L load, $1\Omega, 1\mu H$


VSI simulation (recap)

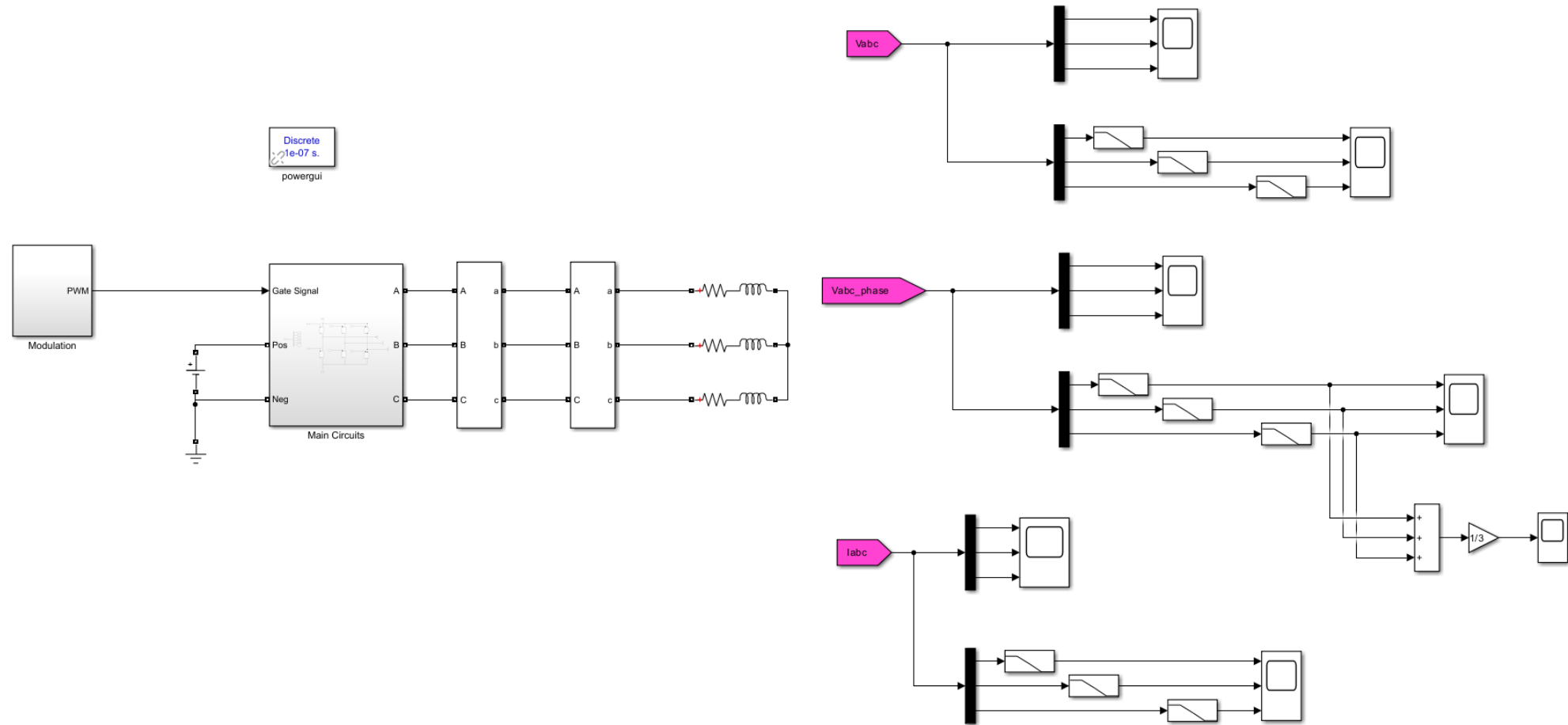

VSI simulation (recap)

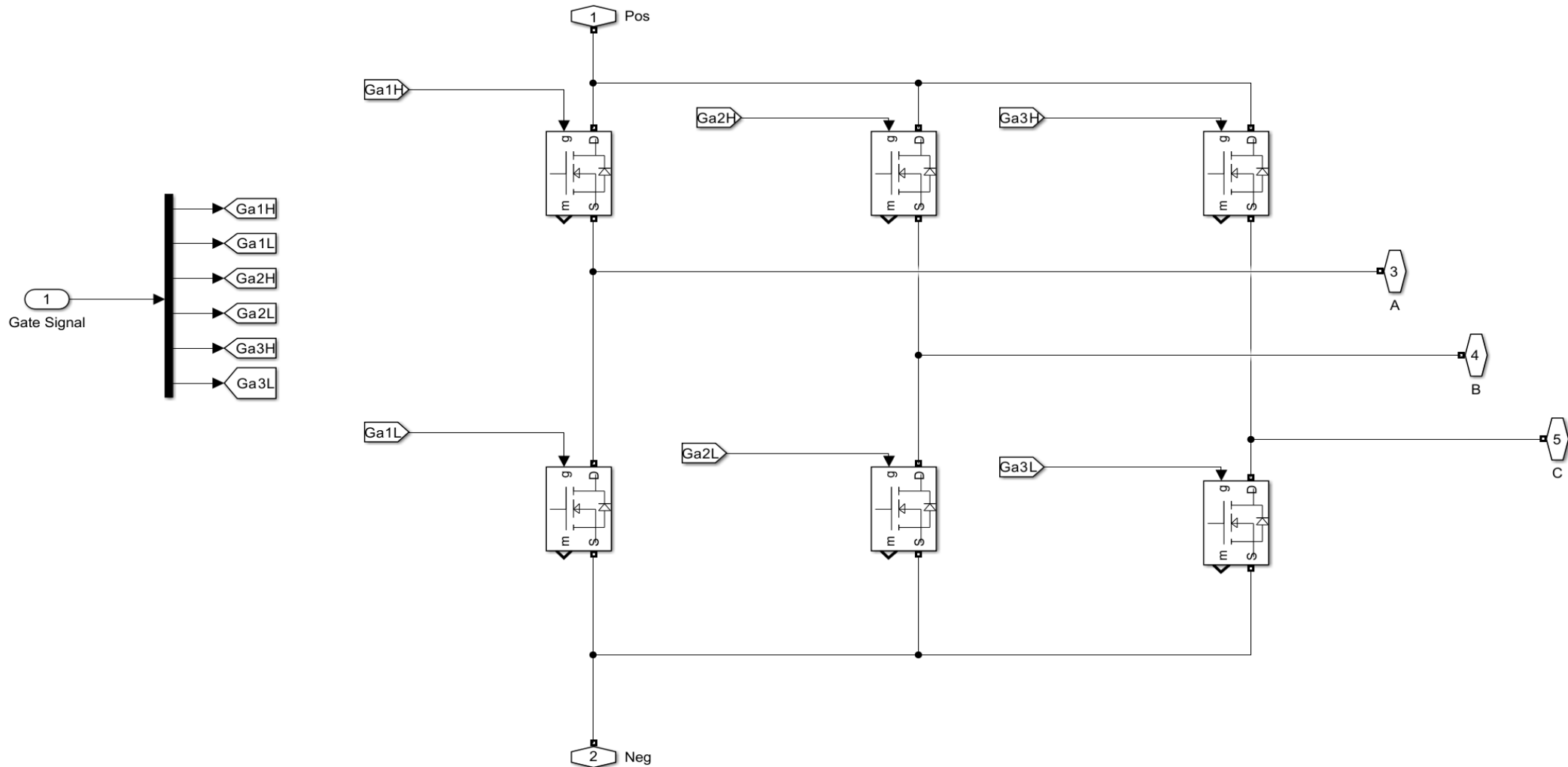

VSI simulation - modulation (recap)

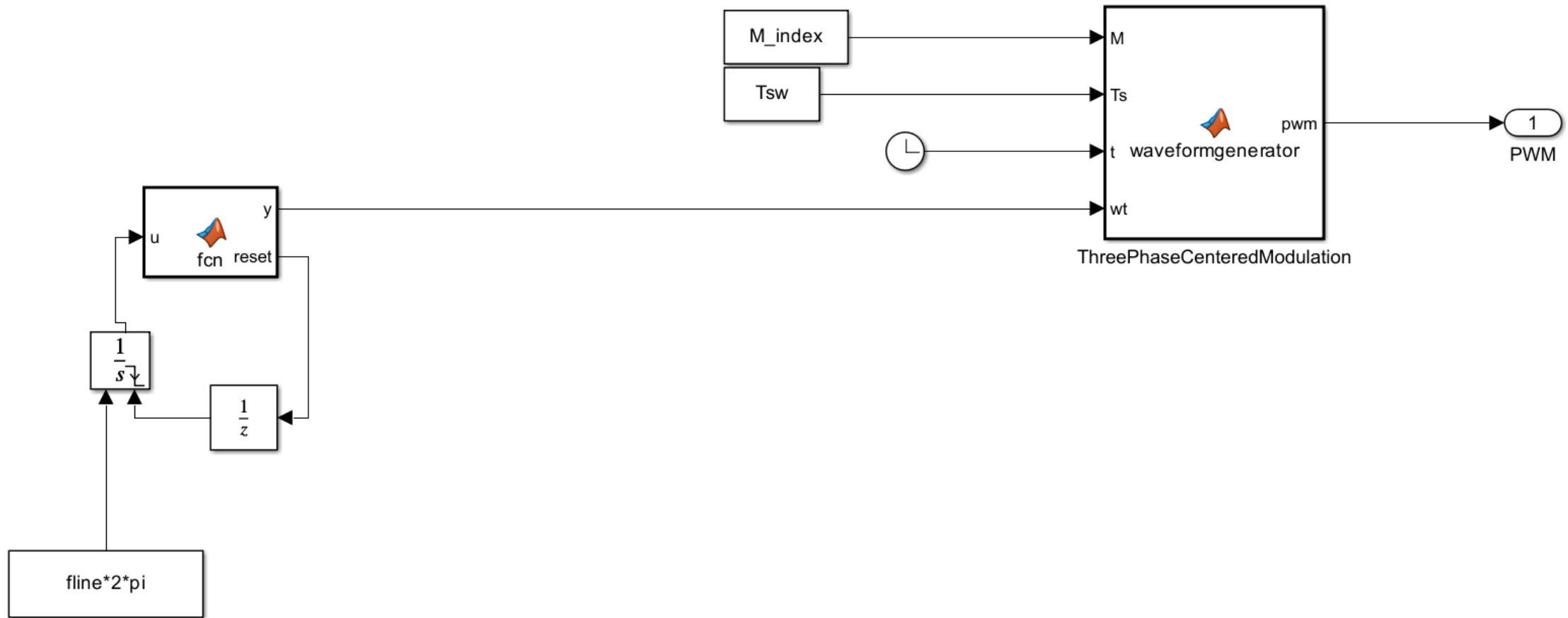

VSI simulation - modulation (recap)

```
% inputs: M=modulation index, Ts=switching period, t=simulation time,
% wt=fundamental angle
function pwm = waveformgenerator(M,Ts,t,wt)
```

```
p=[1;0]; n=[0;1];
% find the current sector and relative angle phi
```

```
theta=rem((wt),2*pi)-pi/6;
if theta<0
    theta=theta+2*pi;
end
```

```
if theta<(pi/3)
    phi=theta; V1=[p;n;n]; V2=[p;p;n]; % sector 1
elseif theta<(2*pi/3)
    phi=theta-pi/3; V1=[p;p;n]; V2=[n;p;n]; % sector 2
elseif theta<(3*pi/3)
    phi=theta-2*pi/3; V1=[n;p;n]; V2=[n;p;p]; % sector 3
elseif theta<(4*pi/3)
    phi=theta-3*pi/3; V1=[n;p;p]; V2=[n;n;p]; % sector 4
elseif theta<(5*pi/3)
    phi=theta-4*pi/3; V1=[n;n;p]; V2=[p;n;p]; % sector 5
else
    phi=theta-5*pi/3; V1=[p;n;p]; V2=[p;n;n]; % sector 6
end
```

```
V0=[n;n;n];
V7=[p;p;p];
```

```
% find time durations for vectors
T1=M*sin(pi/3-phi)*Ts;
T2=M*sin(phi)*Ts;
T0=Ts-T1-T2;
```

```
% relative time in a switching period
tsec=rem(t,Ts);
```

```
% apply the vectors -- for three phase centered modulation (0127-7210)
if tsec<T0/4
    pwm=V0;
elseif tsec<(T0/4+T1/2)
    pwm=V1;
elseif tsec<(T0/4+T1/2+T2/2)
    pwm=V2;
elseif tsec<(T0/4+T1/2+T2/2+T0/2)
    pwm=V7;
elseif tsec<(T0/4+T1/2+T2/2+T0/2+T2/2)
    pwm=V2;
elseif tsec<(T0/4+T1/2+T2/2+T0/2+T2/2+T1/2)
    pwm=V1;
else
    pwm=V0;
end
```


VSI simulation - modulation (recap)

Exercise:

Implement modulation with three phase symmetric (0127210) and two phase symmetric (01210) PWM


- Compare filtered voltage and current waveforms
- Compare common mode voltage waveforms
- Compare unfiltered current waveforms
- Which one is better?

Electromagnetic Interference




- In 1992, a woman died because pacemaker failure when the technicians turned on their radio transmitter to ask for advice
- Another example is the explosion of the Texaco refinery in Milford Haven UK, on the 24th of July 1994,
 - which was caused by an electrical storm giving rise to power surges
 - tripped out a number of pump motors while leaving others running.
 - The explosion led to 26 people being sustainably injured and damage of £48 million .

Electromagnetic Interference

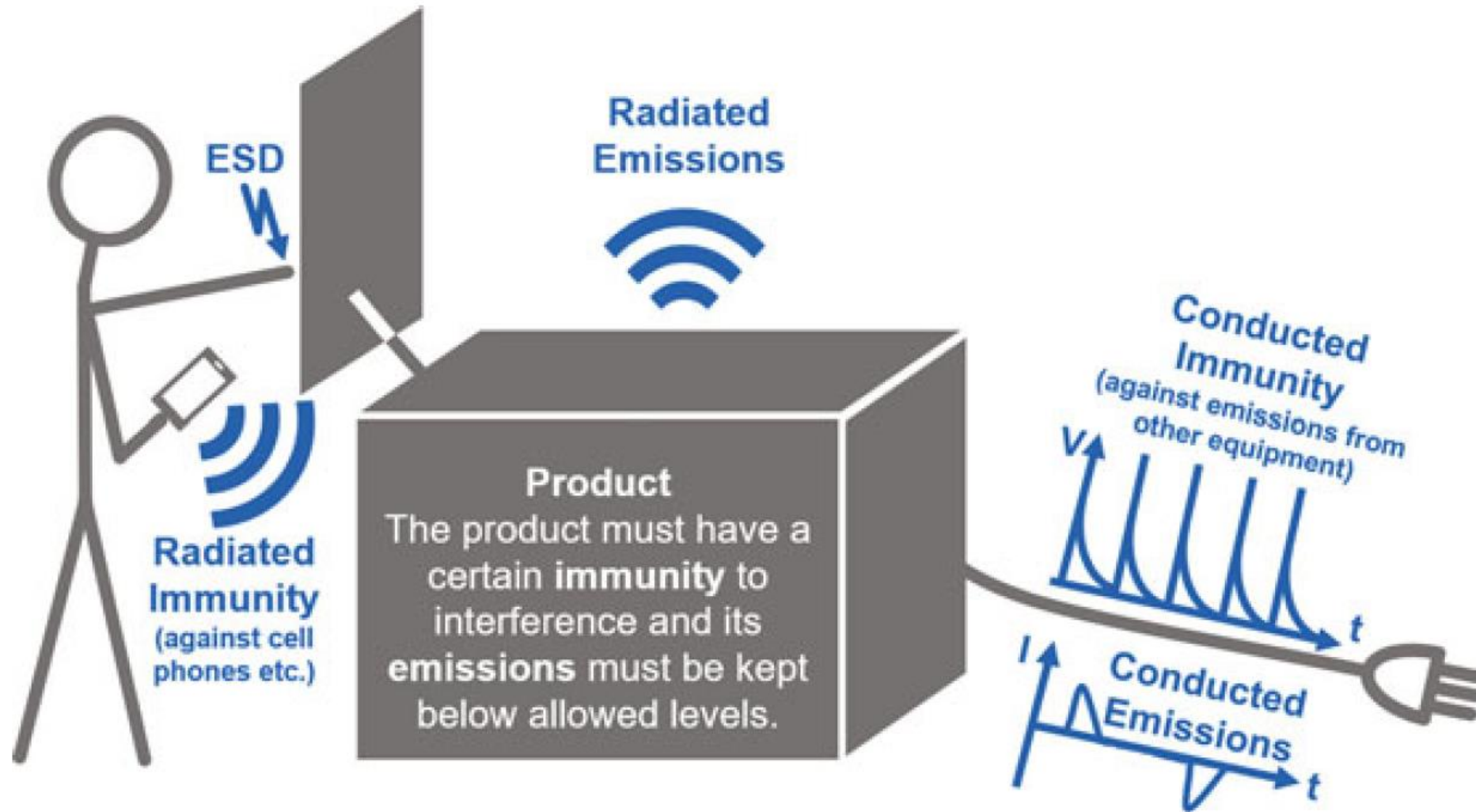

Electromagnetic Compatibility (EMC)

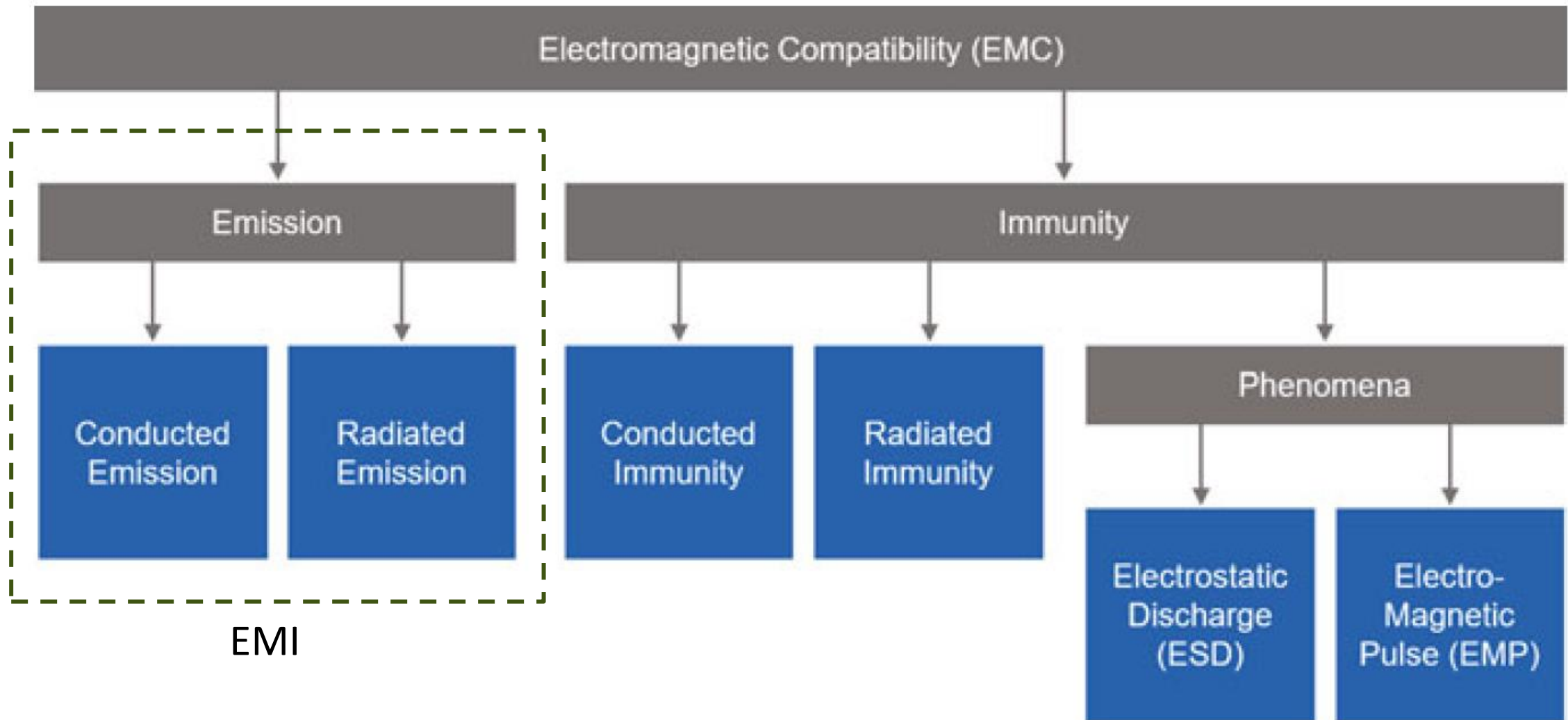

Electromagnetic emissions


- Reduce Conducted emissions
 - Radio frequency conducted emissions
 - To prevent connected cables from radiating and
 - To avoid the interference of connected equipment
 - Harmonics
 - To prevent distortion of public mains supply
 - Flickers
 - to avoid unsteadiness
- Reduce Radiated emissions
 - To prevent disturbance of nearby electrical and electromechanical equipment

EMI standards

- Conducted EMI standards
 - measurement done on the connecting cables
 - Frequency range depends on products and standards to comply
 - 150 kHz to 30MHz (CISPR 32 and FCC 47)

- Radiated EMI standards
 - measured in an anechoic or semi-anechoic chamber or at an open area test site (OATS).
 - frequency range depends on products and standards to comply
 - 30MHz to 6 GHz (CISPR 32)
 - 30MHz up to 40 GHz (FCC 47)


EMC regulations

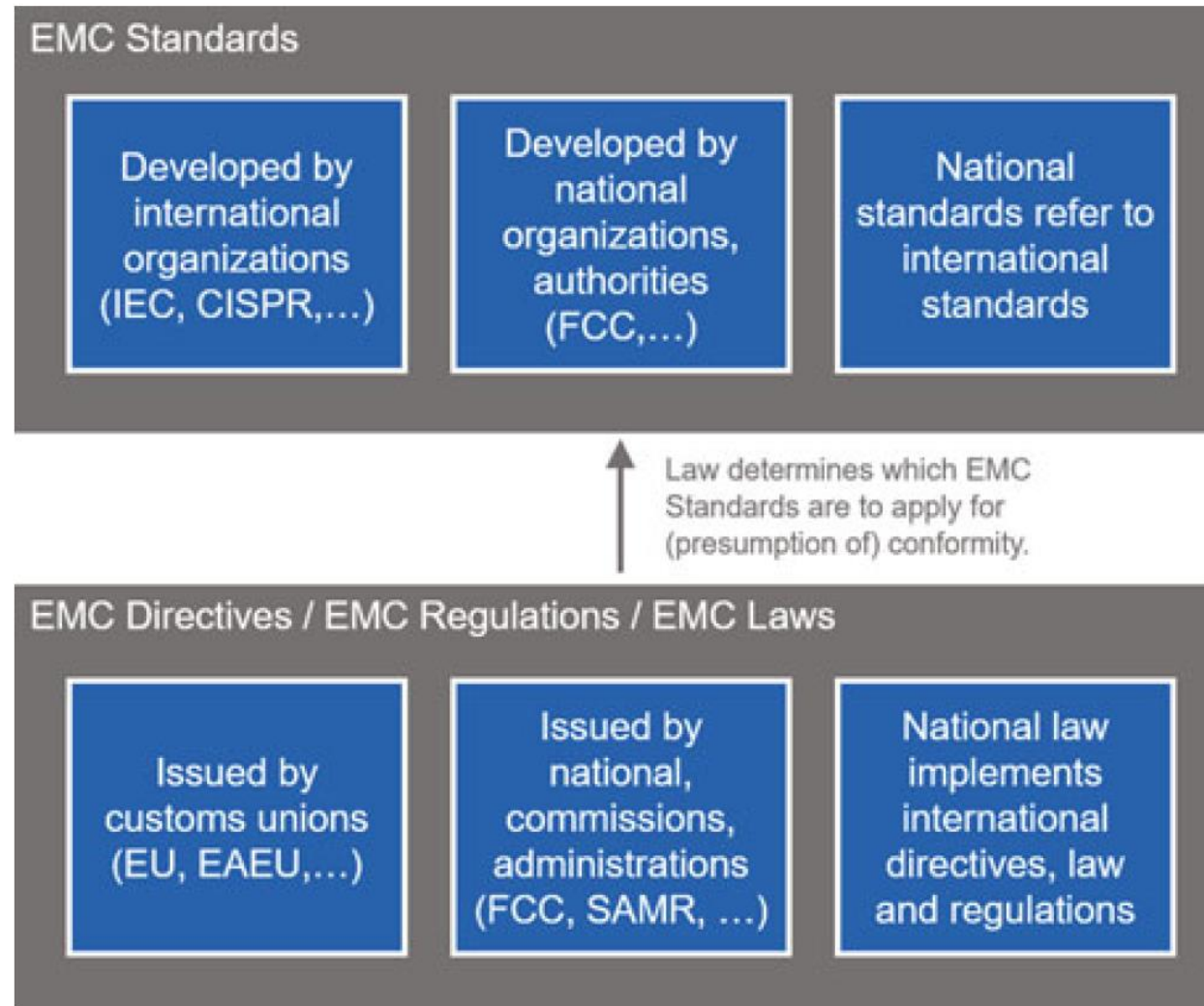

EMC compliance mark


- Bureau of Indian Standards (BIS) mandates Compulsory Registration Scheme (CRS)

- BIS CRS Mark

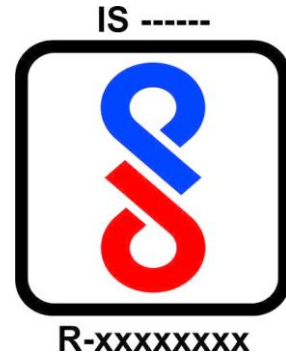


- For imported products, following marks are recognized,

- CE Mark (Europe)
- FCC Mark (USA)

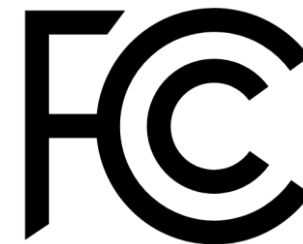


CISPR 25 EMI test setup

Side view

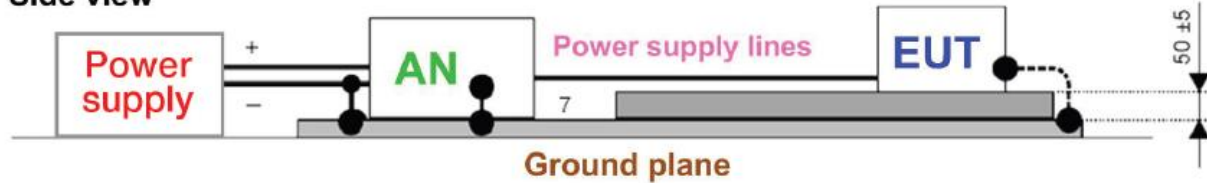

Top view

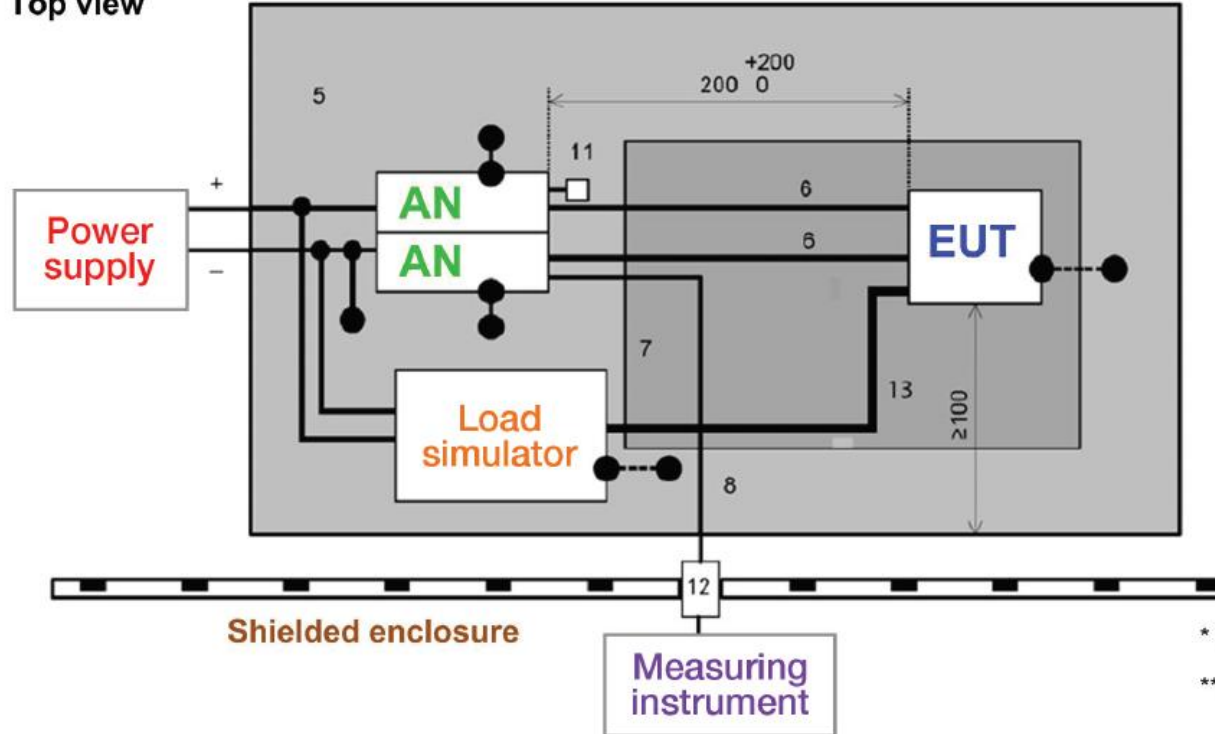

5 = Reference ground plane

6 = Power supply lines

7 = Low relative permittivity support, $\epsilon_R \leq 1.4$

8 = High-quality 50-Ω coaxial cable,

11 = 50 Ω load termination


12 = Bulkhead connector

13 = Test harness (excluding power lines)


* Image adapted from CISPR 25 ed. 4 specification

** Spatial distances in mm

CISPR 25 EMI test example


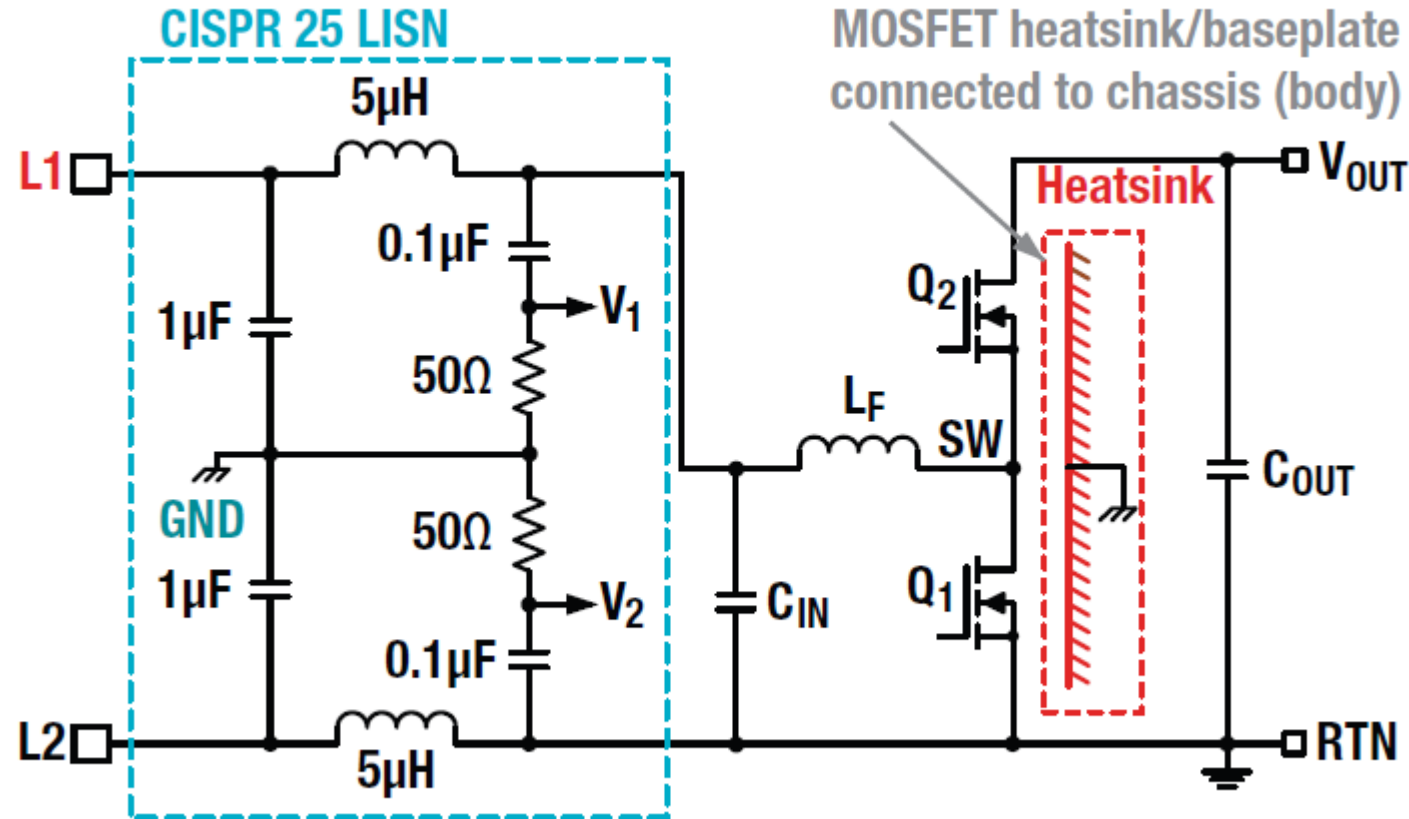


EMI Filter

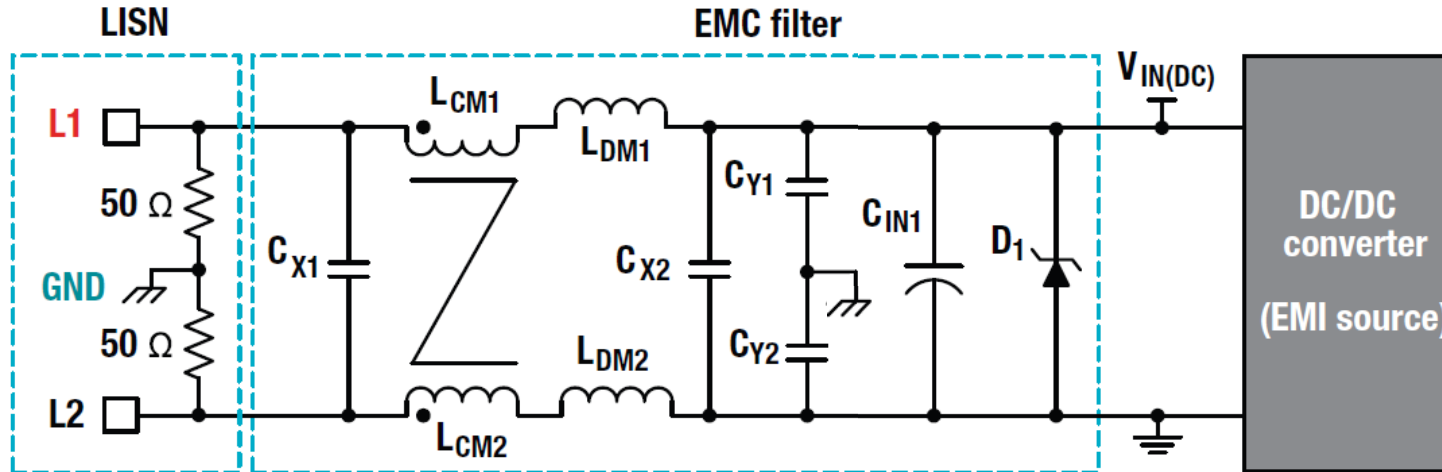


DM

CM

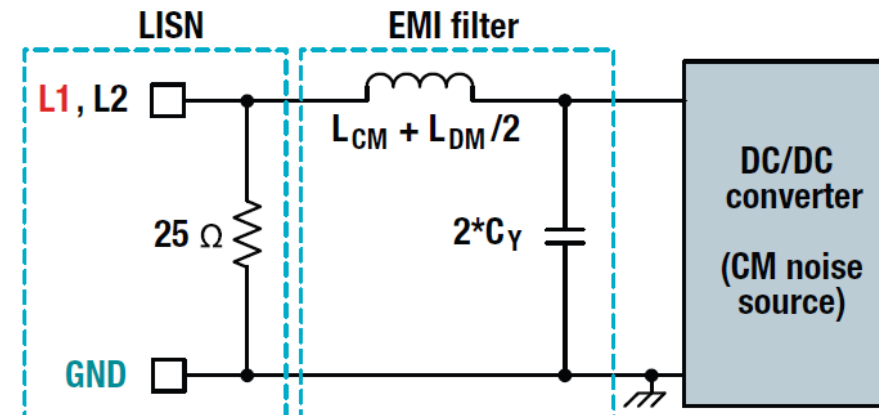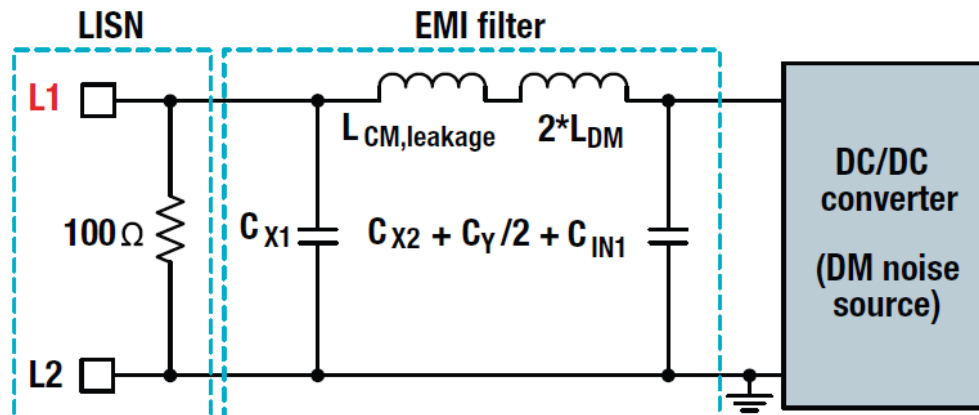





LISN model

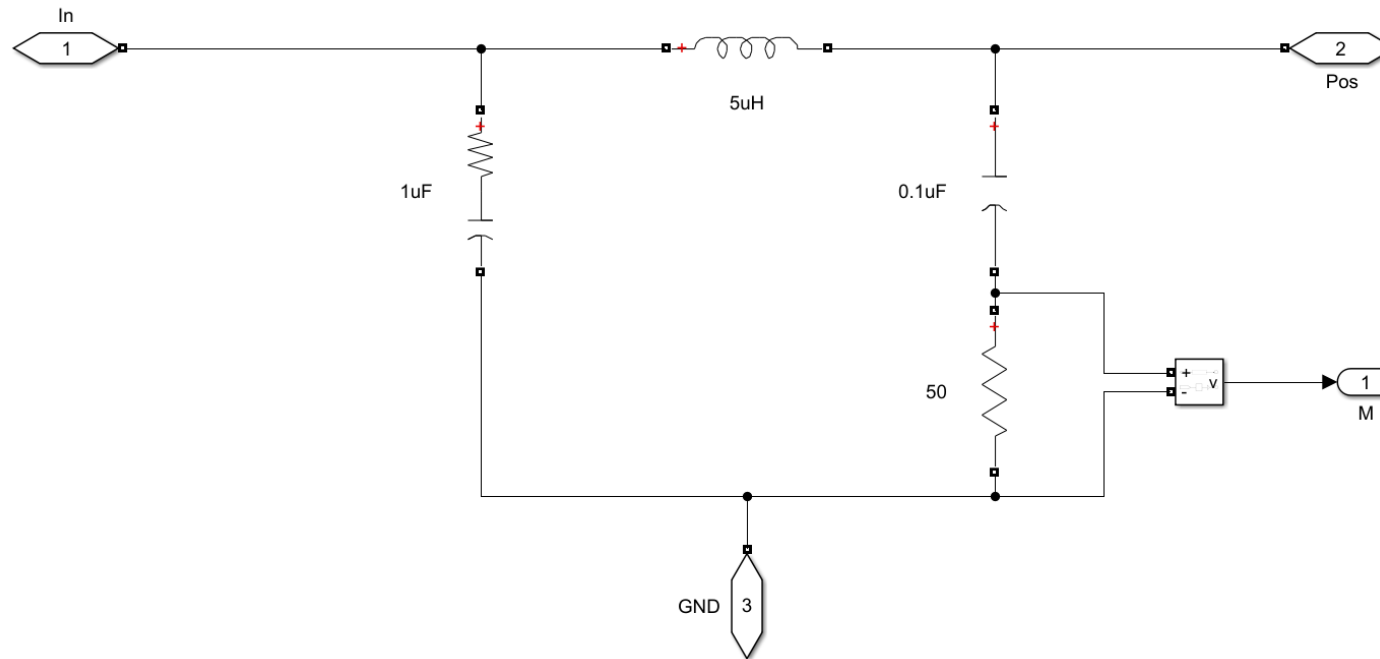

EMI DM noise comparison

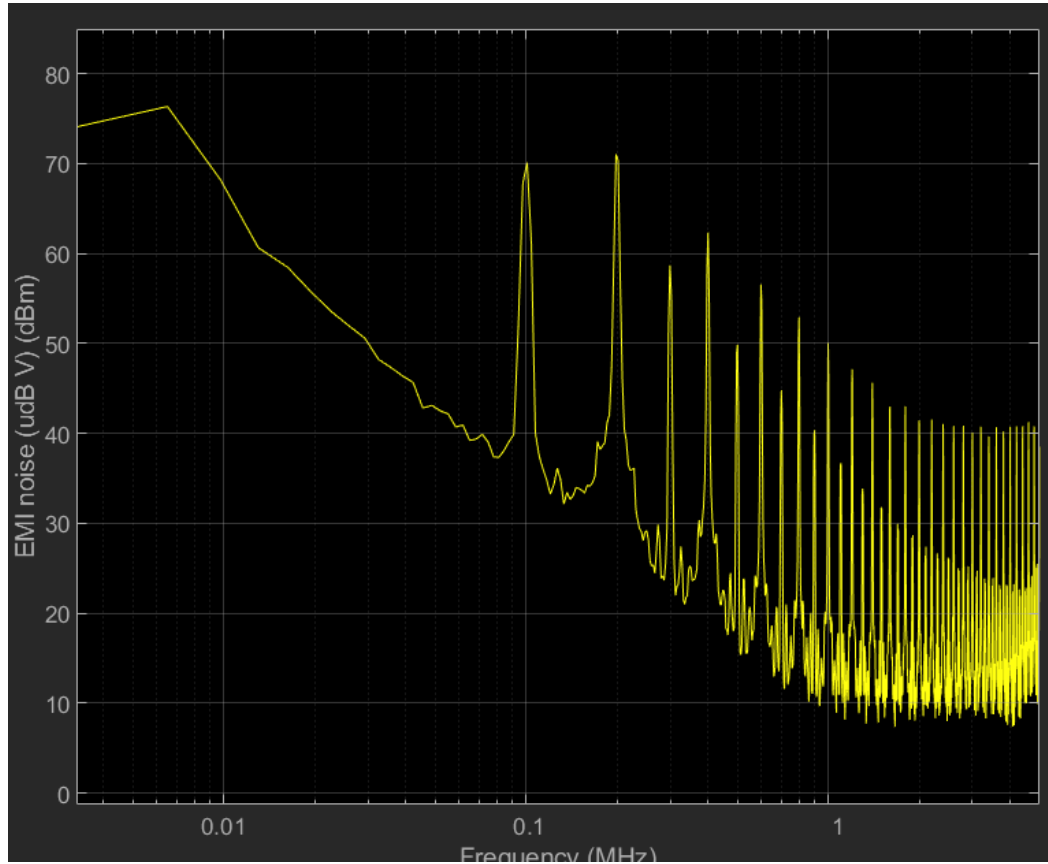

3-ph symmetric SVPWM

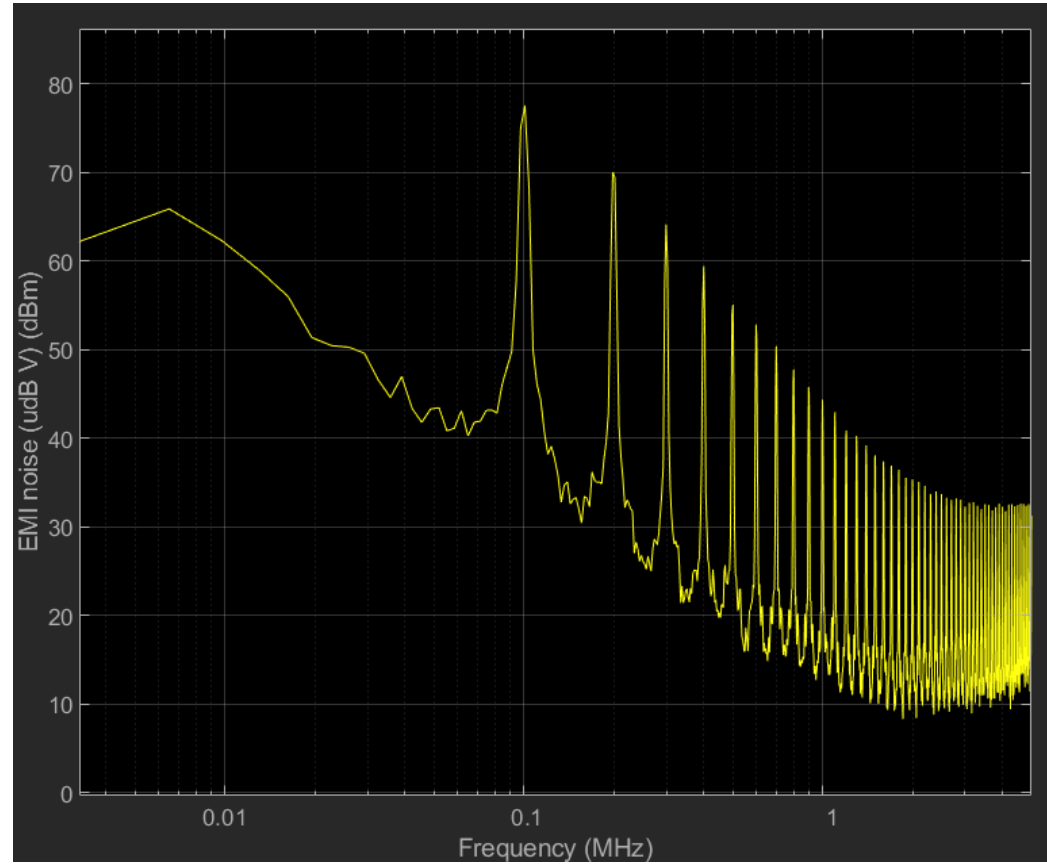

2-ph symmetric SVPWM

Thank you!