

Electric Vehicle (EE60082)

Lecture 8: Motor drive for EV (part 4)

DR. SHIMUL K. DAM

ASSISTANT PROFESSOR,
DEPARTMENT OF ELECTRICAL ENGINEERING,
INDIAN INSTITUTE OF TECHNOLOGY (IIT), KHARAGPUR.



Traction motors for EV (recap)


Commonly used motors:

- Brushed DC motor
- Brushless DC motor (BLDC)
- Induction motor
- Permanent magnet synchronous motor (PMSM)
- Switched reluctance motor (SRM)



AC Machines

Rotating magnetic field (recap)

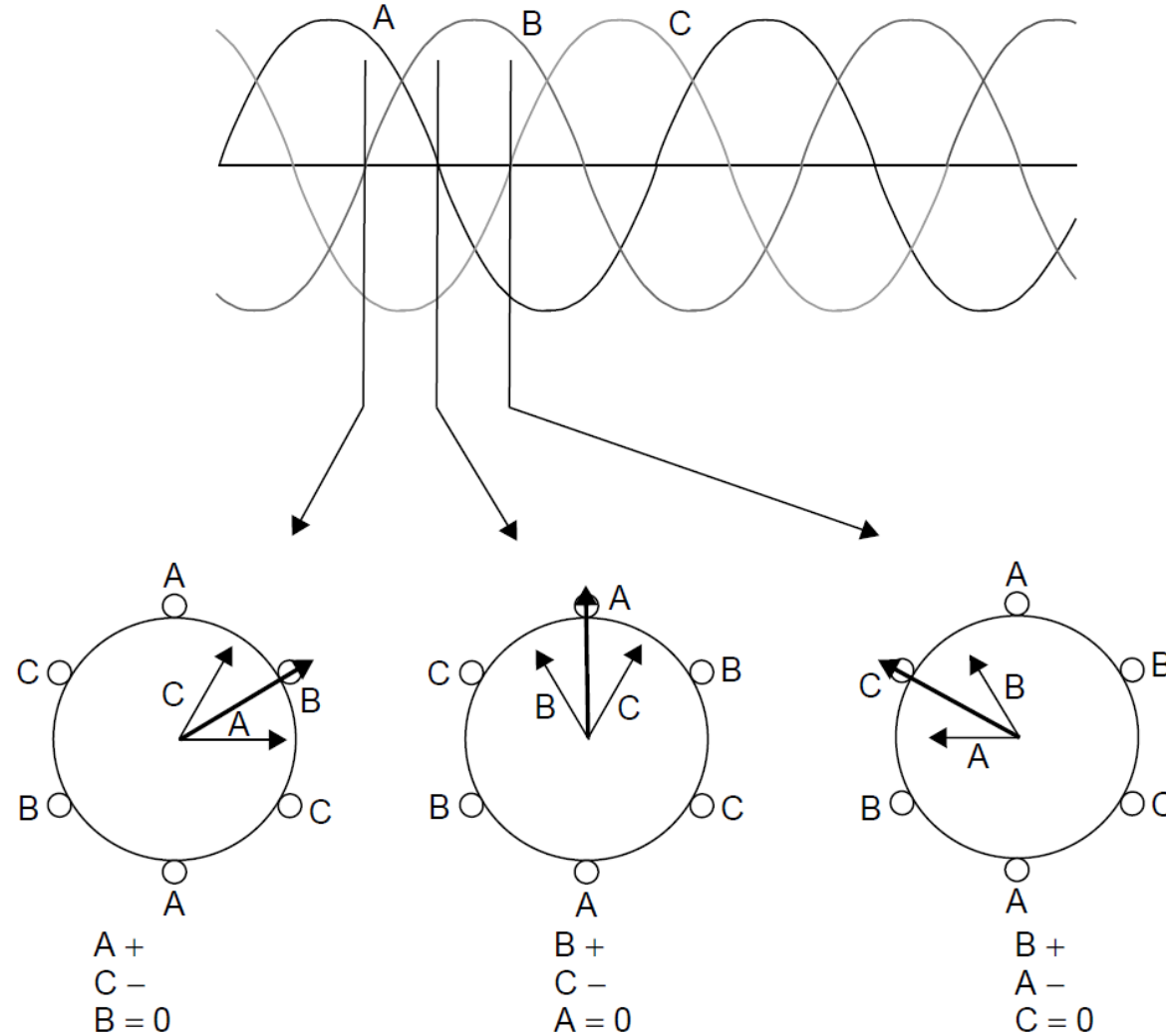

$$n_s = \frac{60f}{p}$$

$$\omega_s = \frac{2\pi n_s}{60}$$

Synchronous speed (recap)




**Assume the wheel radius is 0.25m. The final drive ratio is 1, i.e., gearless.
 $f=50\text{Hz}$ is the rated frequency.**


Pole pair	Synchronous speed (rpm)	Vehicle speed (kmph)
1	3000	282
2	1500	141
3	1000	94
4	750	70
5	600	56
6	500	47

Induction motor construction (recap)

Rotor, oblique view

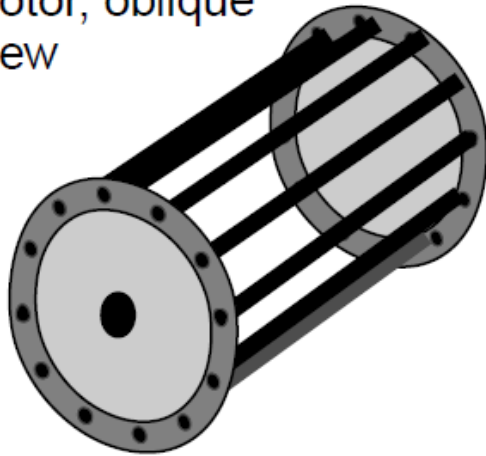


Rotor, end view

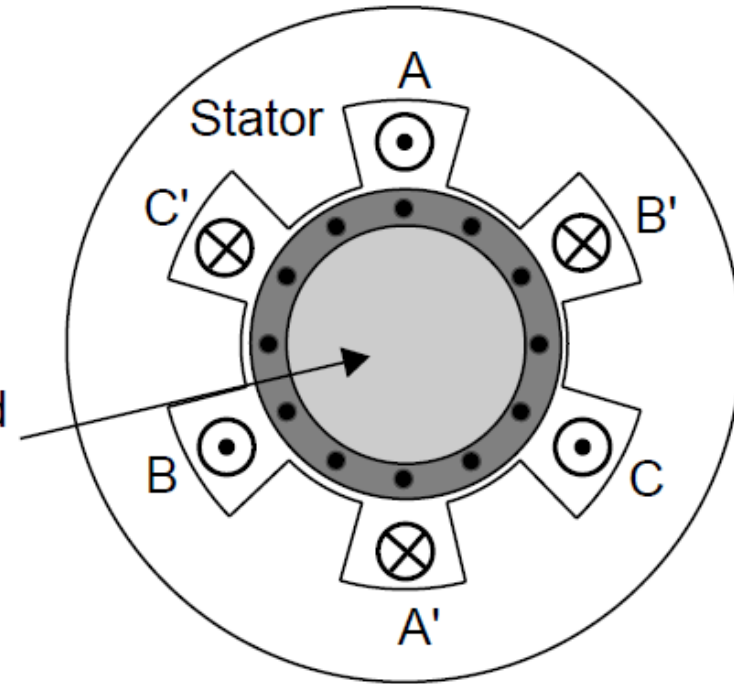

Equivalent circuit (recap)

When the load is heavy...

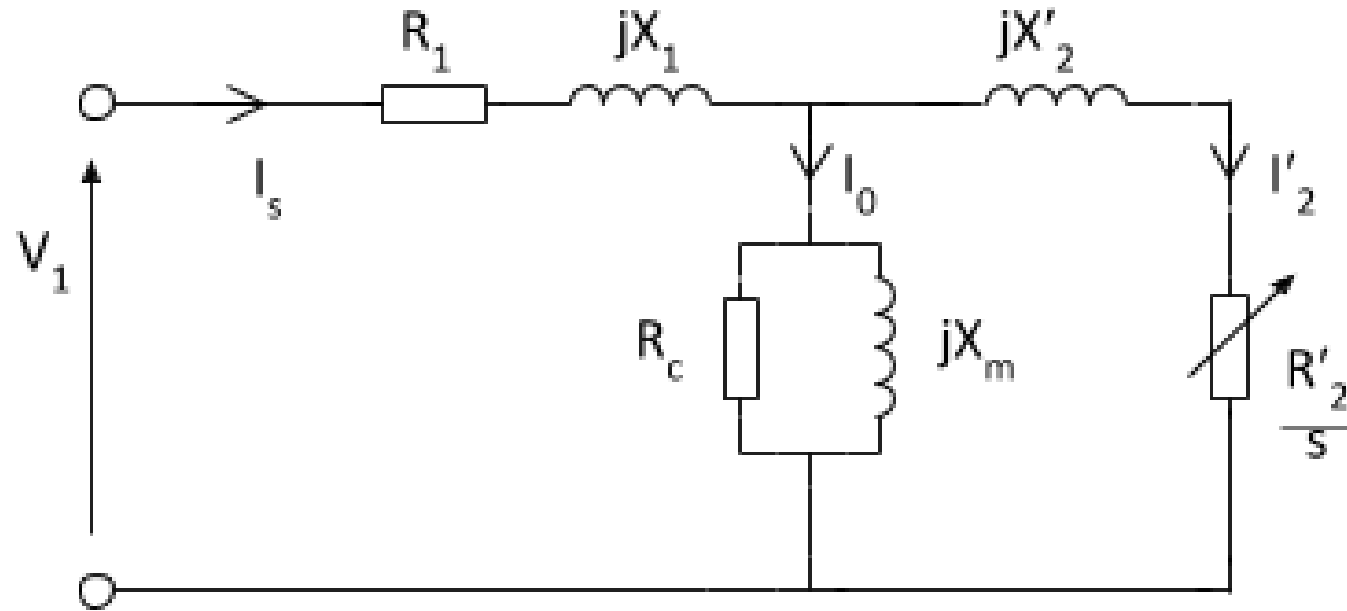


$$P_o = \left| \frac{V_1}{R_1 + R_2'/s + jX_1 + jX_2'} \right|^2 R_2' (1-s)/s$$

$$P_o = \frac{R_2' V_1^2}{(R_1 + R_2'/s)^2 + (X_1 + X_2')^2} \frac{1-s}{s}$$


Voltage control (recap)
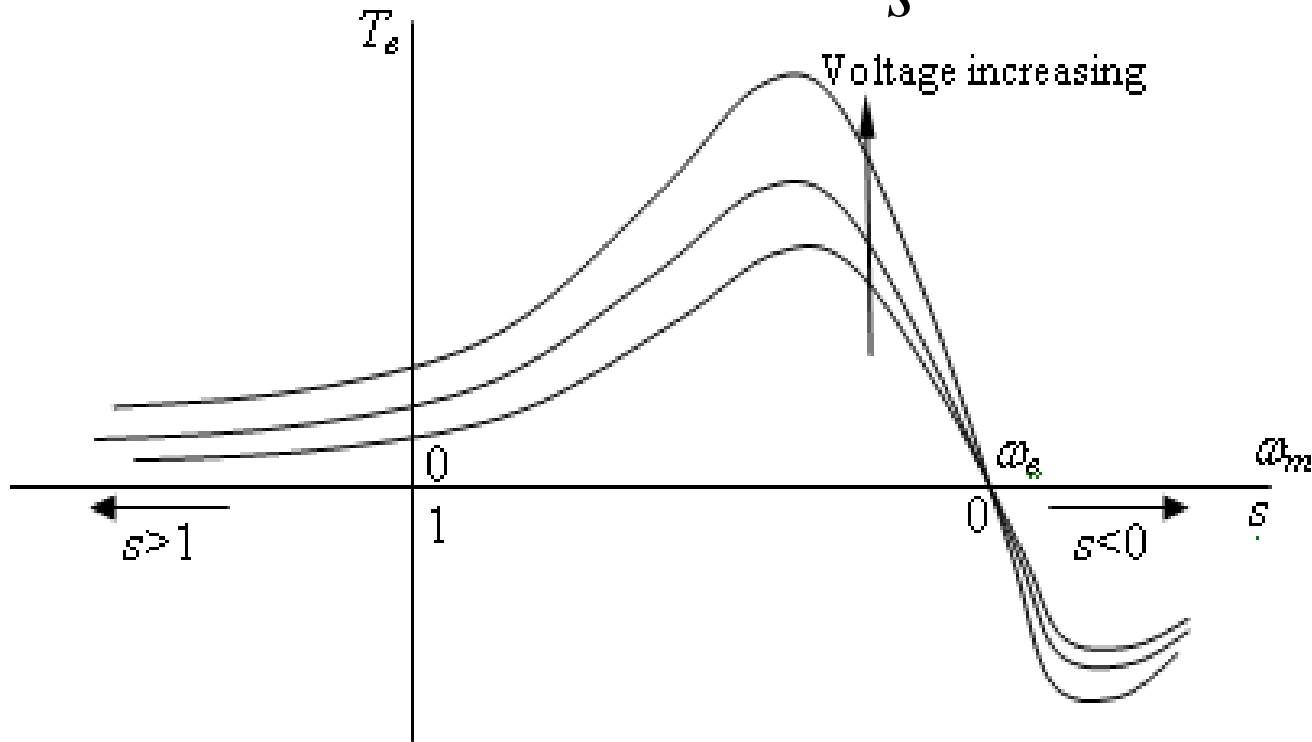
$$T = \frac{R_2' V_1^2}{s \{ R_1^2 + (X_1 + X_2')^2 \} + \frac{R_2'^2}{s} + 2R_1 R_2'} \frac{1}{\omega_s}$$



V/F control

Ignore the stator loss.

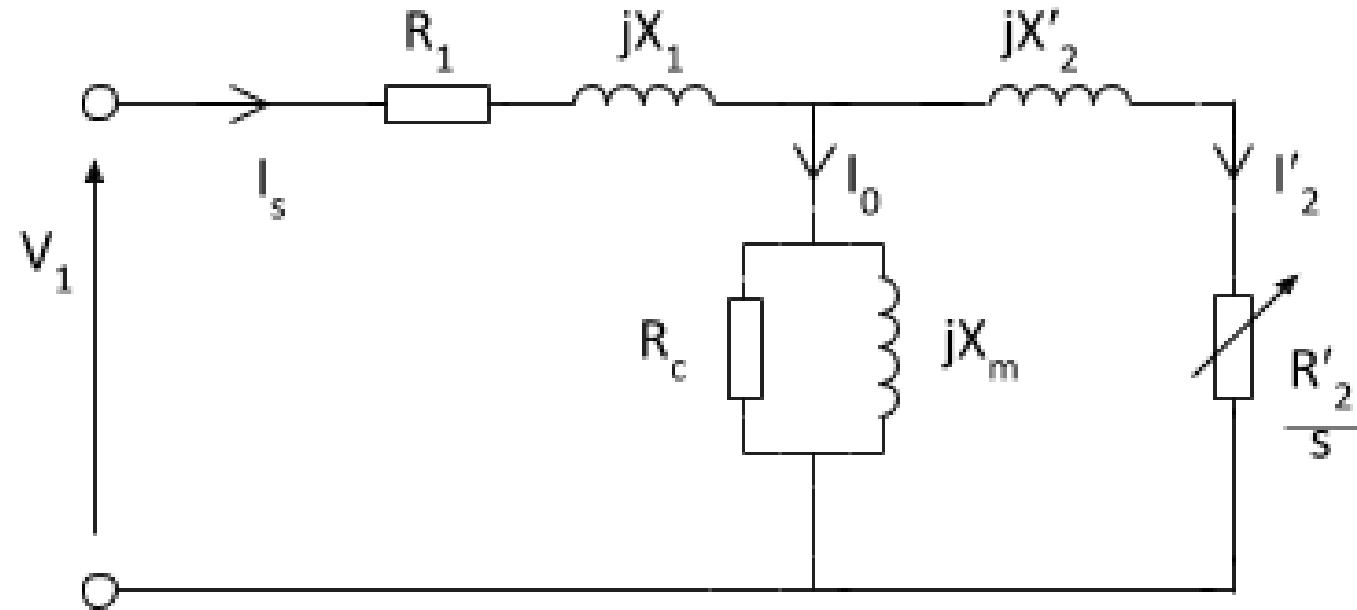


$$V_1 = j\omega_s L_m I_0 \quad V_1 = j2\pi f_s \psi_m \quad \frac{V_1}{f_s} = j2\pi \psi_m$$

To avoid potential saturation, VVVF control is used.

Frequency control (recap)

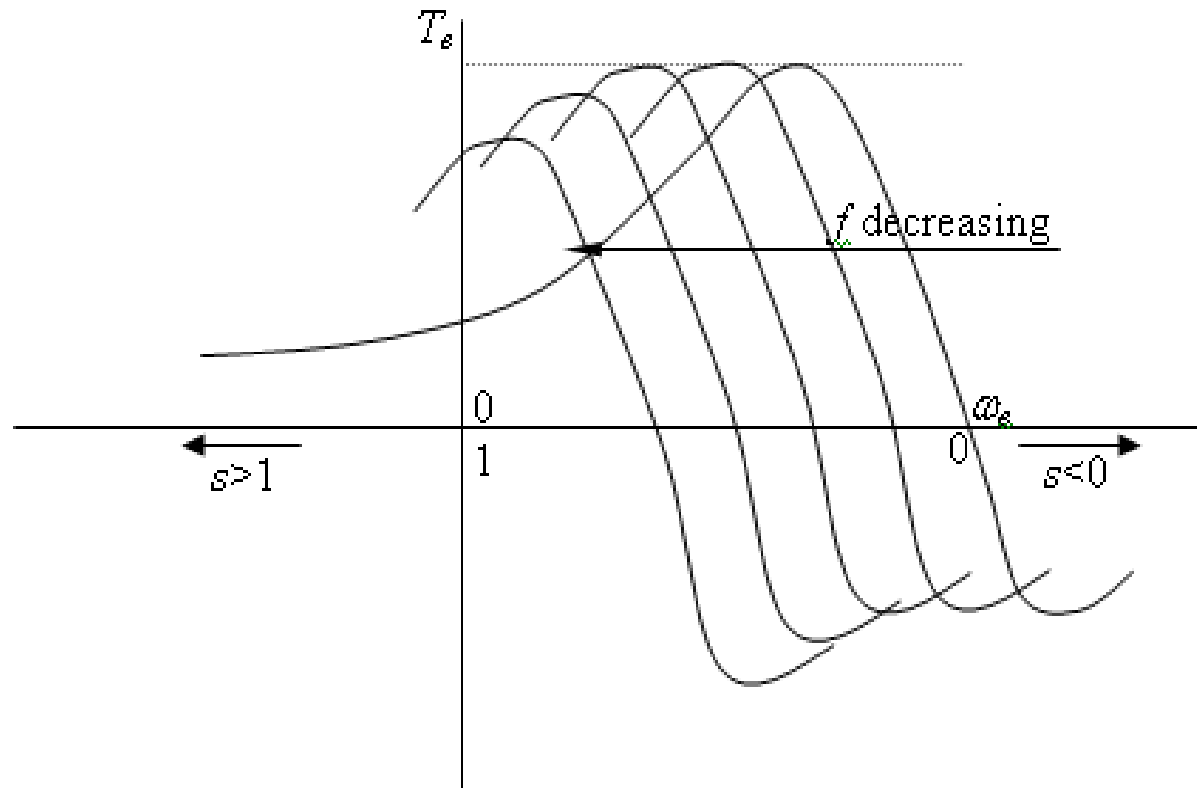
$$T = \frac{R_2' V_1^2}{s \{ R_1^2 + (X_1 + X_2')^2 \} + \frac{R_2'^2}{s} + 2R_1 R_2' \omega_s} \frac{1}{\omega_s}$$



Design for higher starting torque (recap)



$$R_1 > R_2 > R_3 > R_4$$

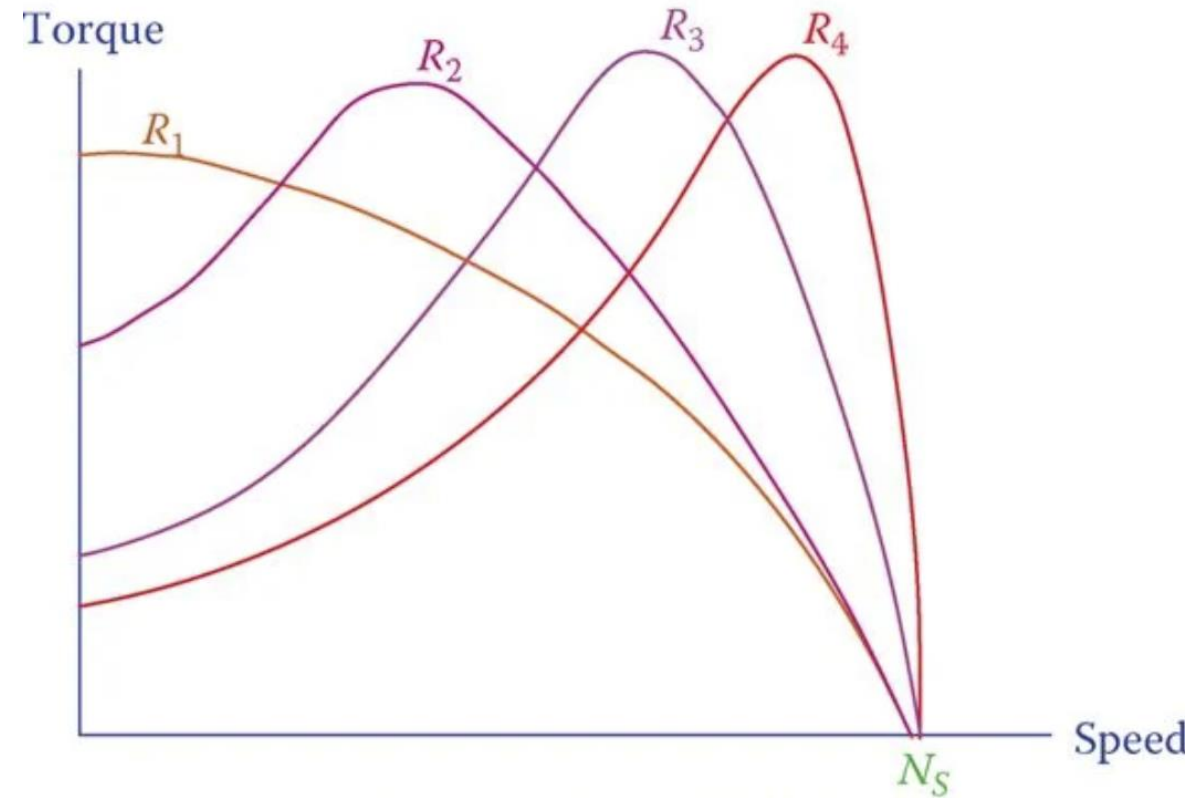

Induction motor- advantages and limitations (recap)



➤ Advantages:

- Simple construction
 - harsh environments with minimal maintenance
- no permanent magnet
 - Lower cost
 - No need for rare-earth elements
- Self-starting
 - No special arrangement needed for starting
- minimal noise and vibration
- can be designed for a wide range of power outputs



➤ Drawbacks:

- Losses in rotor
 - Relatively lower efficiency
 - Heating in rotor
- Complicated torque and speed control
 - complex controller required
- High in-rush current
 - When DOL starter used
- Lower starting torque

Switched reluctance motor (SRM)

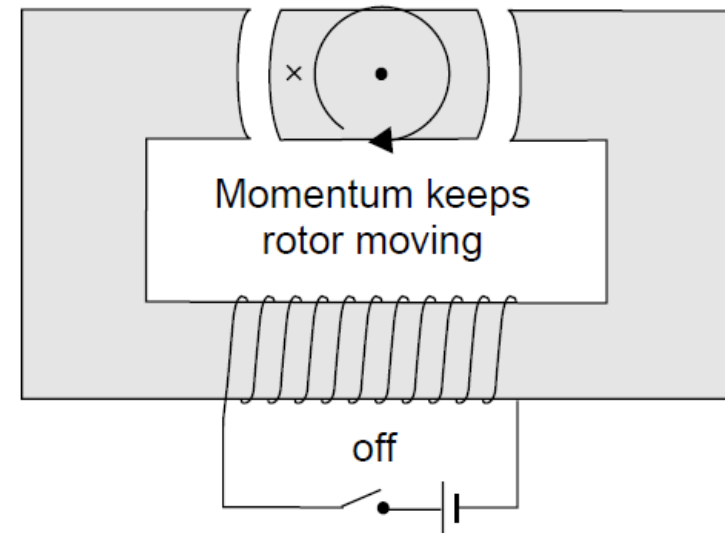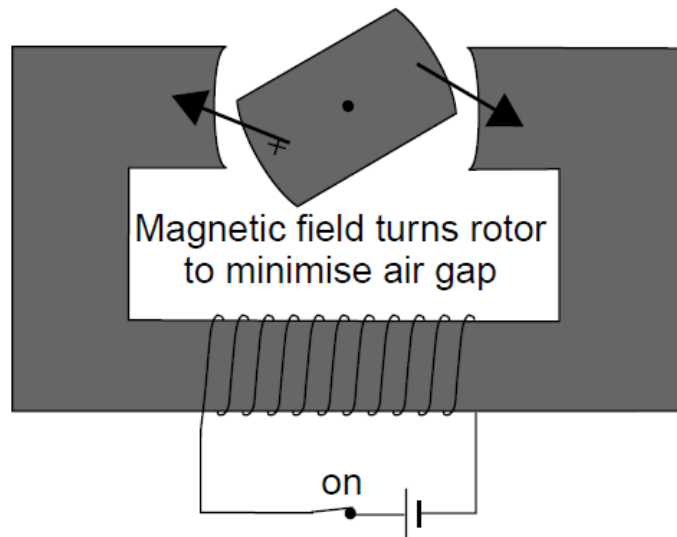

SRM structure

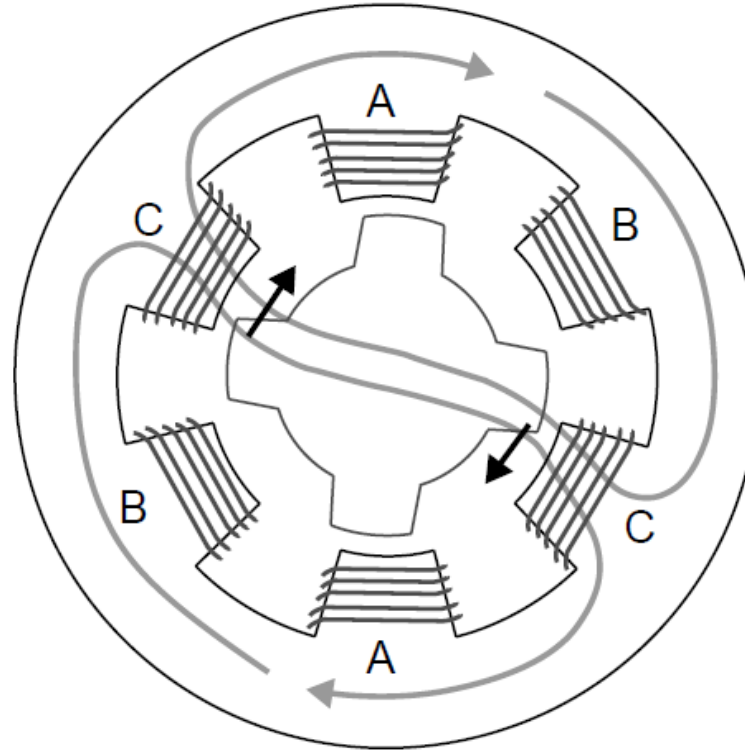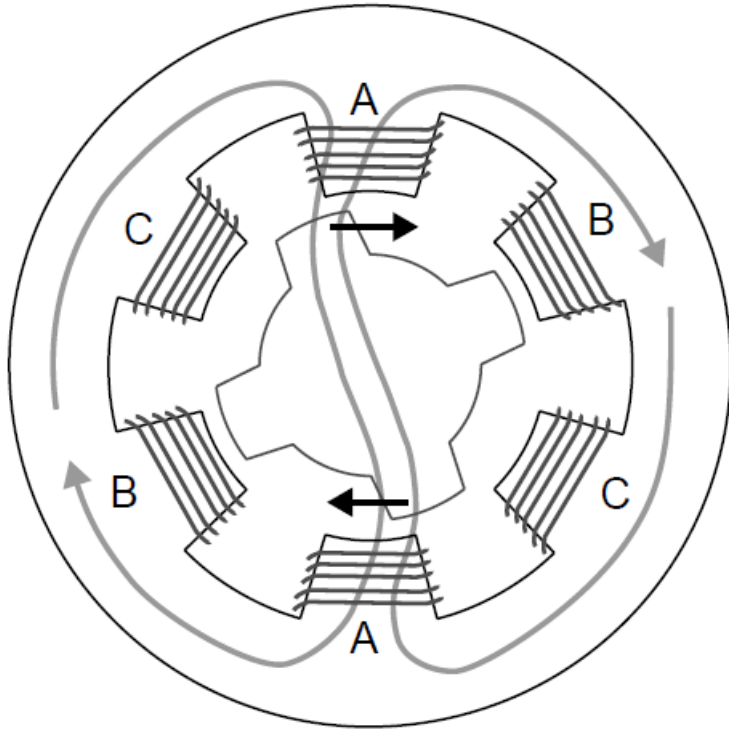

SRM-advantages and limitations



➤ Advantages:



- Simple rotor
 - Rugged construction
 - minimal maintenance
- no permanent magnet
 - Lower cost
 - No need for rare-earth elements
- No current in rotor
 - No conduction loss in rotor
- Good for high speed applications

➤ Drawbacks:

- Higher torque ripple
 - Noisy
- Complicated control
 - complex controller required
- Need for accurate position sensing
 - Costly sensors


Rotating magnetic field

Stator winding

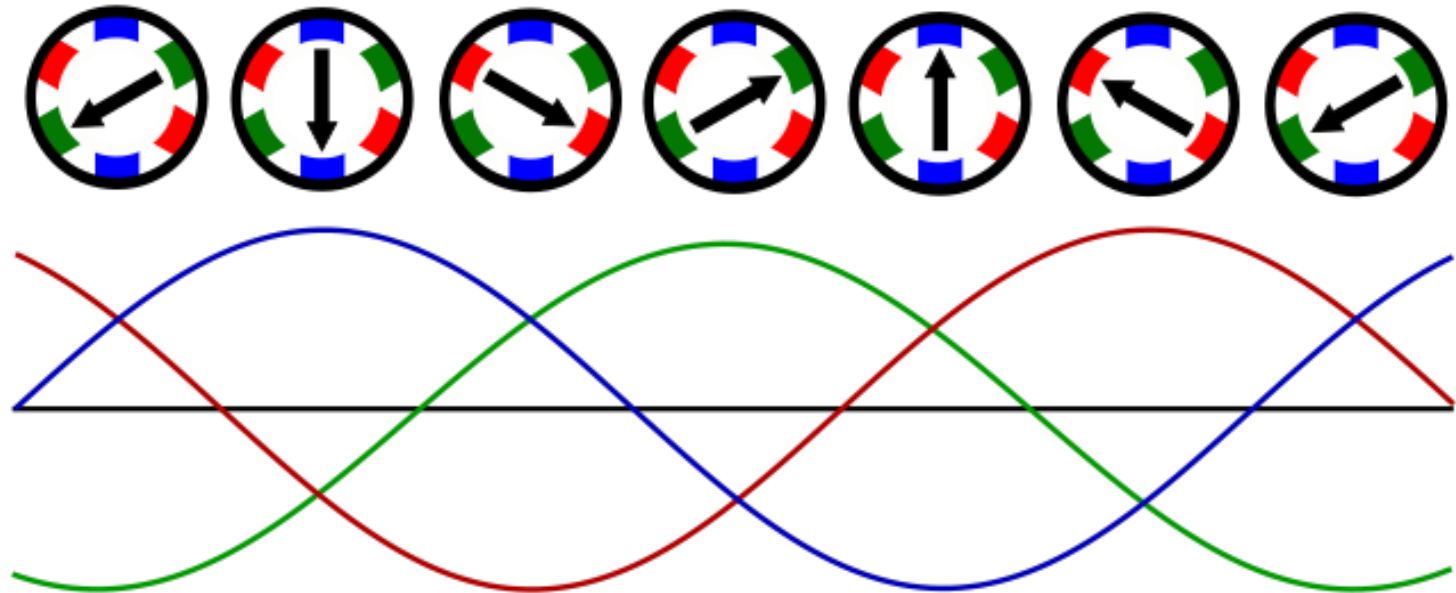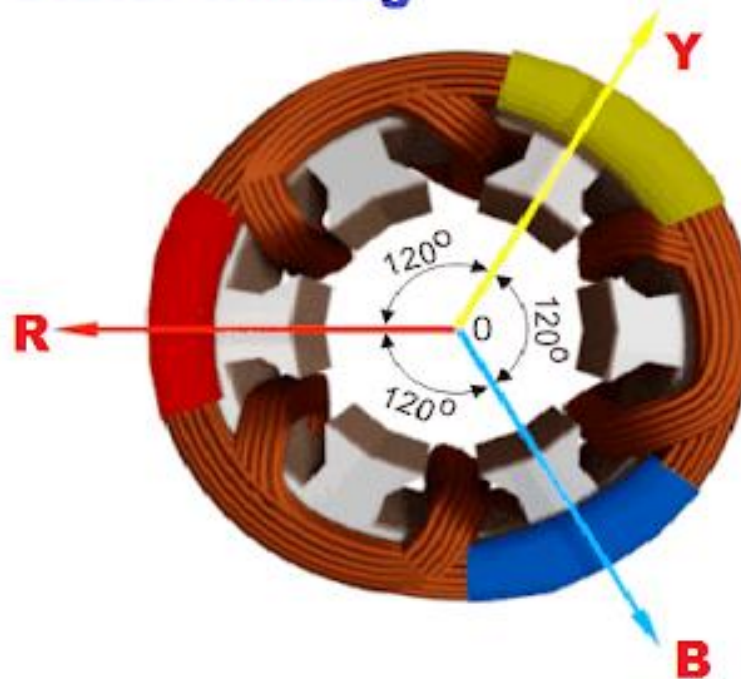


Permanent Magnet Synchronous Machine (PMSM)


Rotor, oblique view

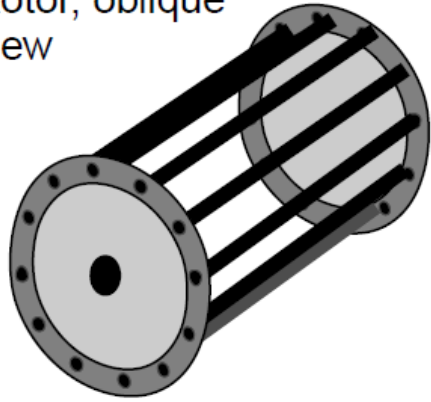

Rotor, end view

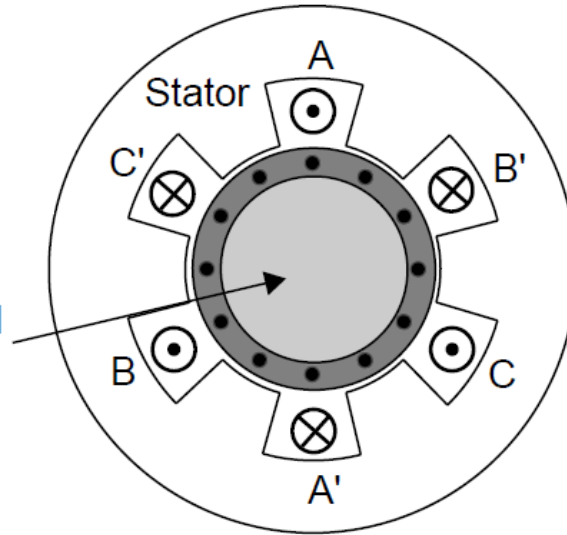


Induction motor

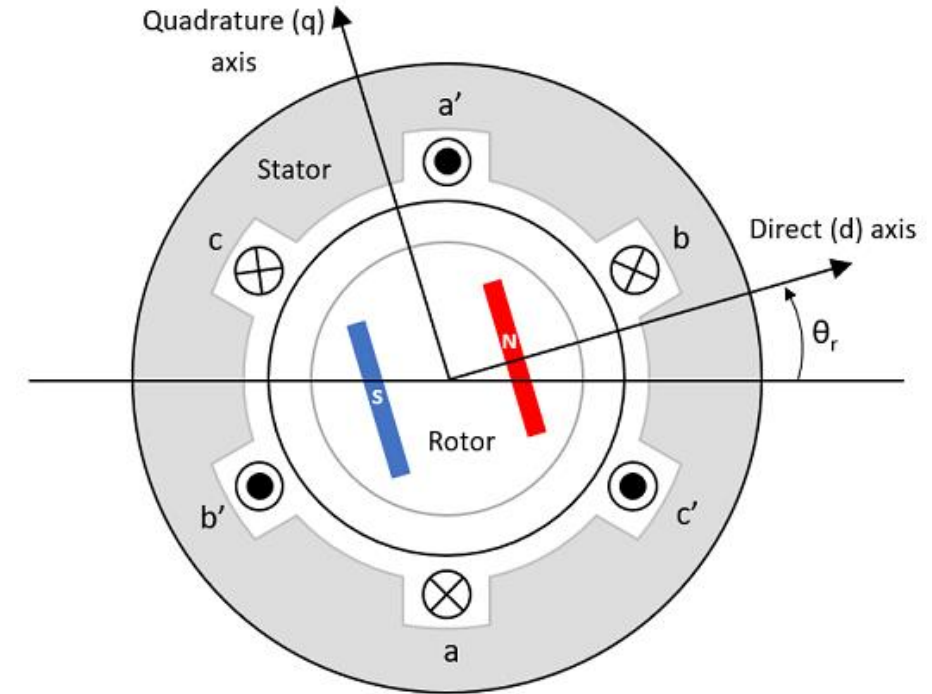


PMSM motor

PMSM induced voltage

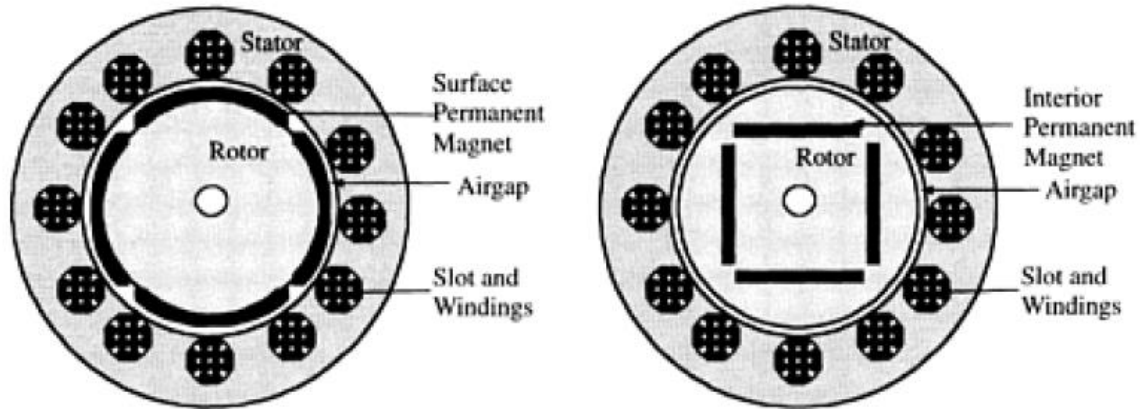


Surface mount and interior mount magnets

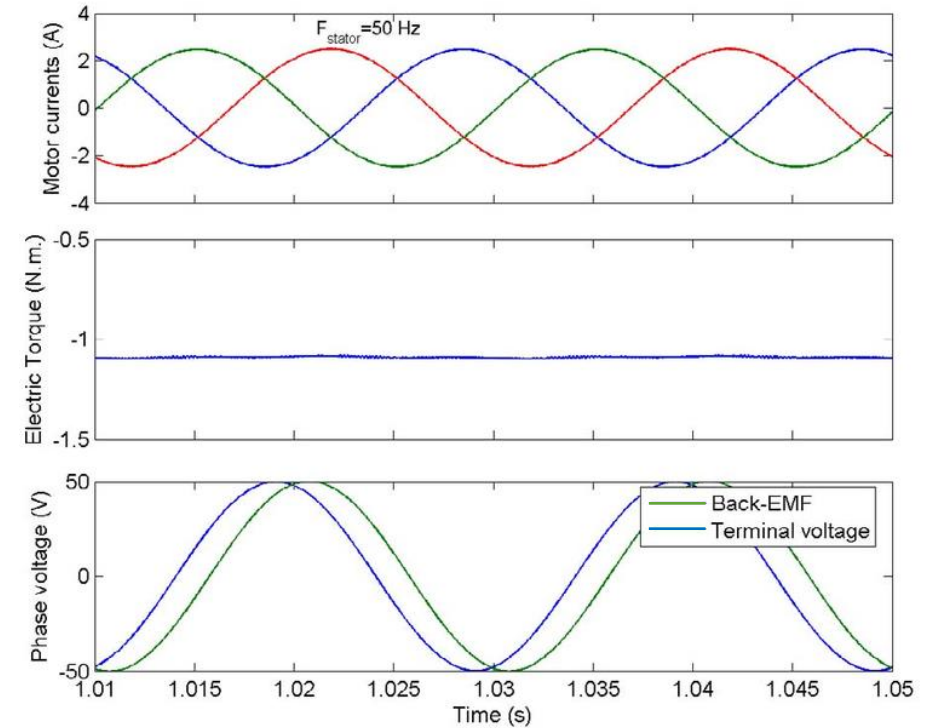

Speed control



Torque-speed characteristics

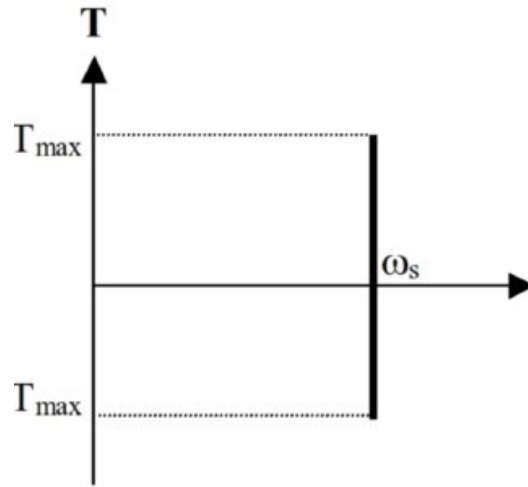

- How to start the motor?
 - Damper winding
 - Auxiliary motor
 - Using control (VFD)

PMSM-advantages and limitations

➤ Advantages:


- Higher power density
 - More flux due to permeant magnet
- Higher efficiency
 - No conduction loss in rotor
- Smooth torque
 - No conduction loss in rotor
- Easier thermal management

➤ Drawbacks:



- Higher cost
 - Costly permanent magnets
- Risk of demagnetization
 - when exposed to higher temperature and reverse magnetic field
- Complex control
- Hazardous fault condition

AC sources for AC Machines



Generation of AC voltage

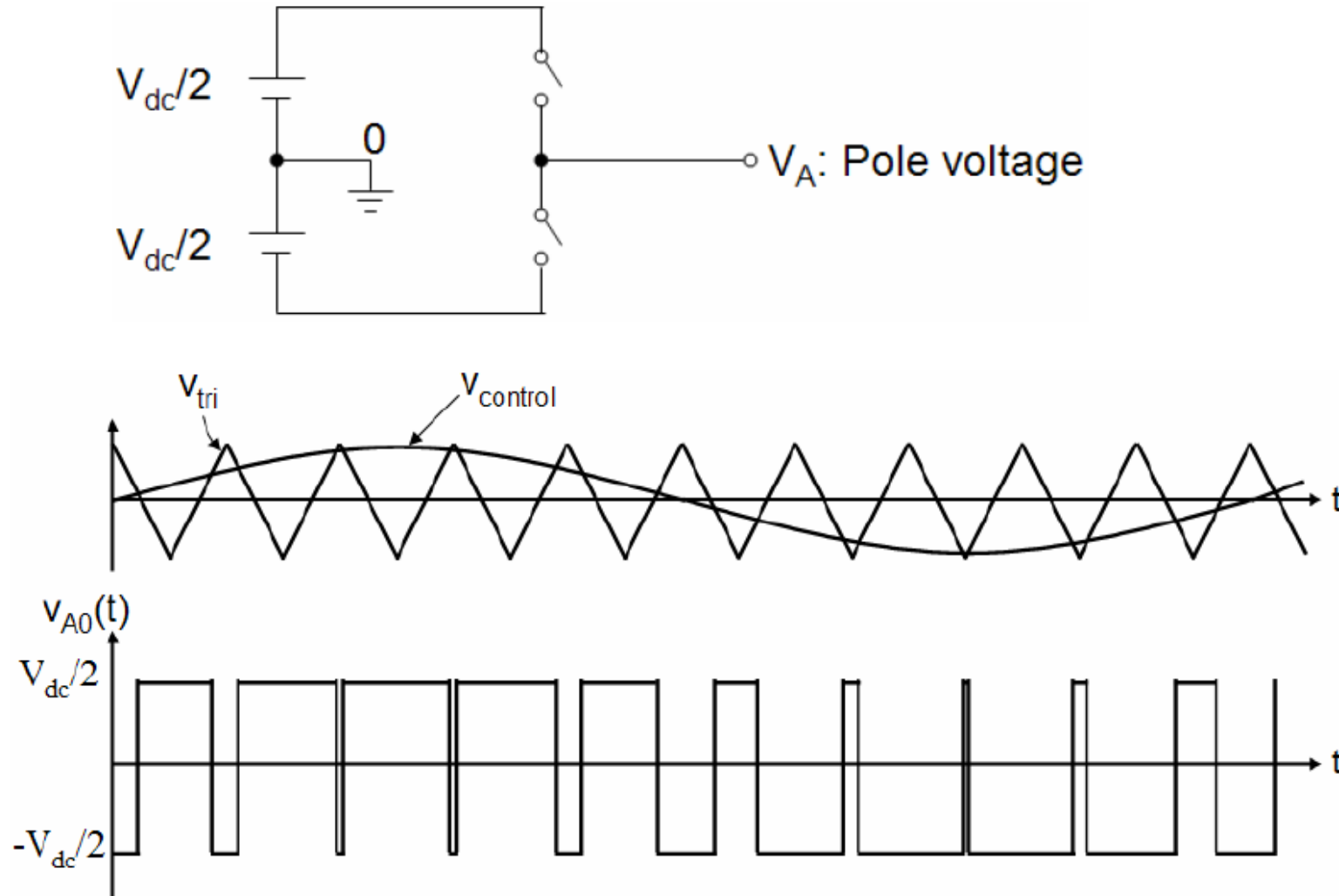


AC generation with H-bridge

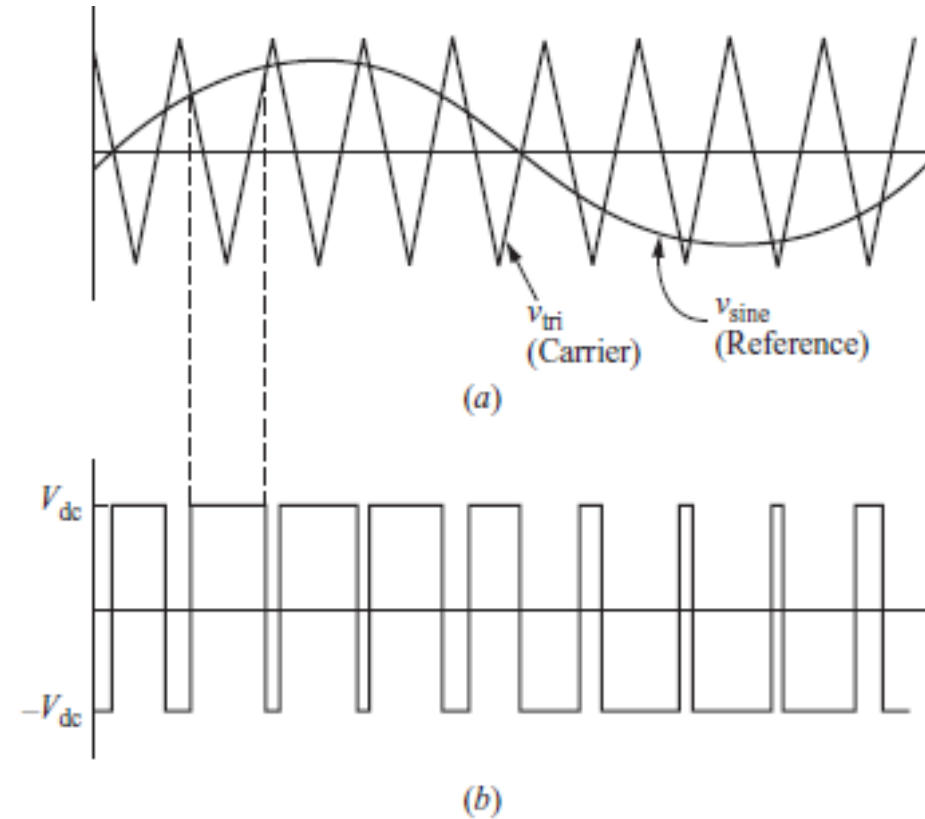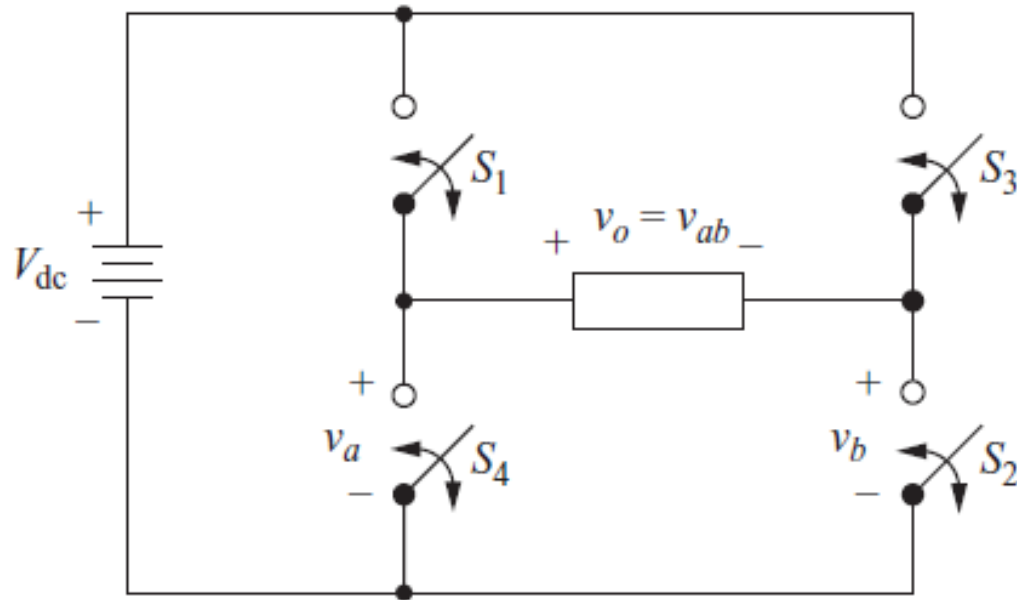

Three-phase voltage generation

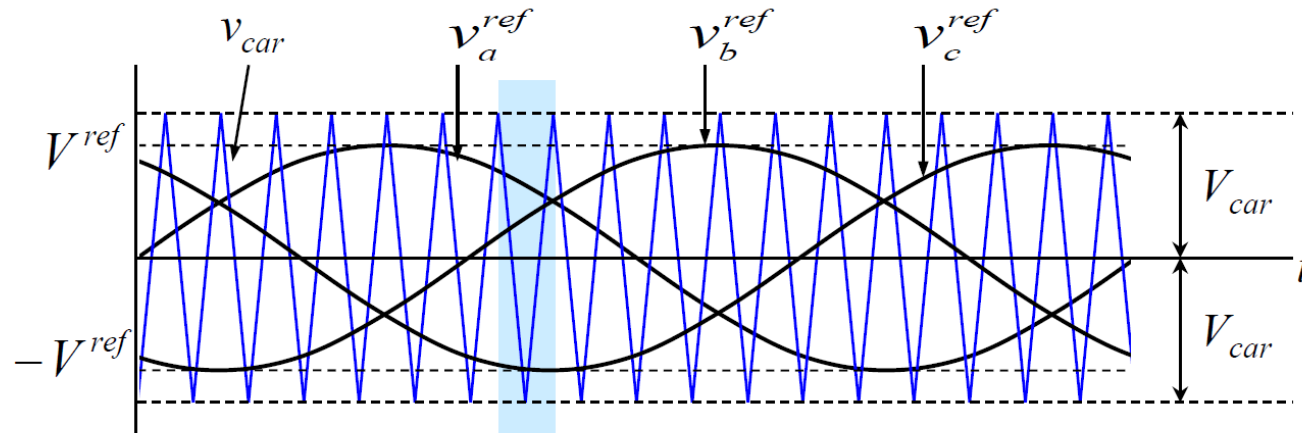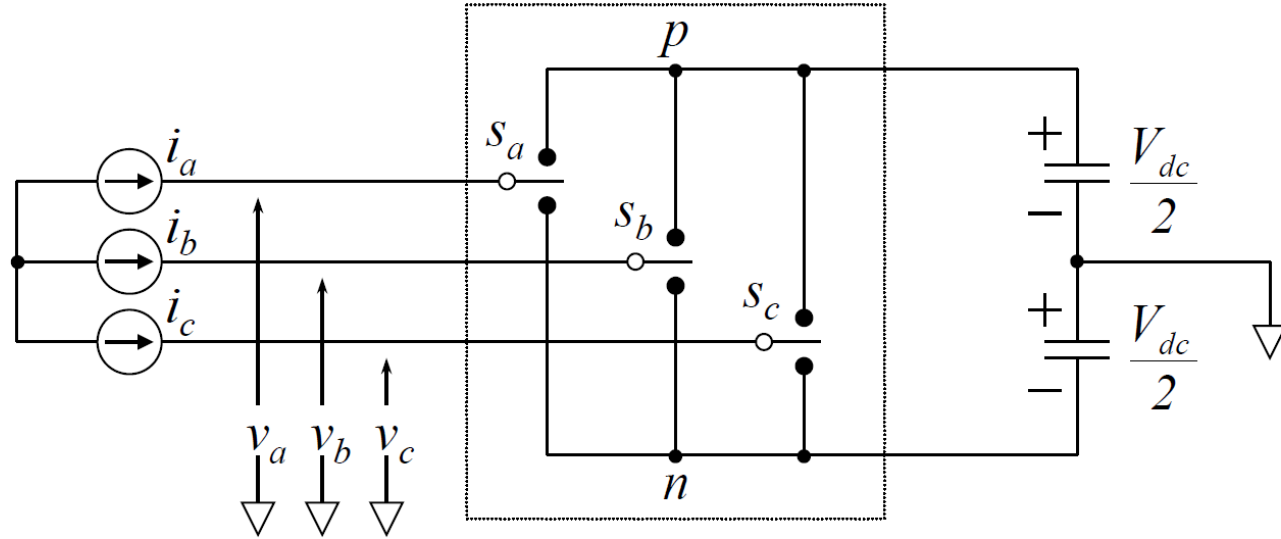

Clarke's Transformation

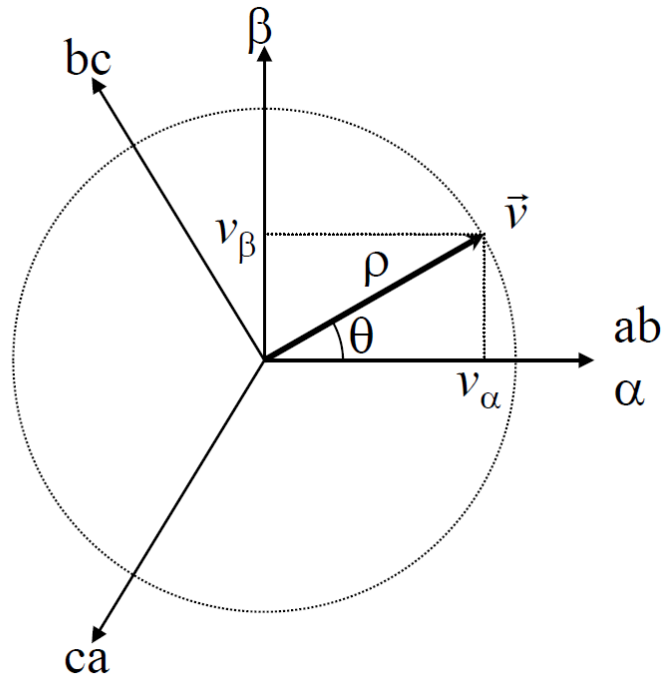

$$T_{\alpha\beta/abc} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$

➤ A bit of history

➤ Edith Clarke (1883-1959)


- The first professional woman electrical engineer in US
- first female professor of electrical engineering
- first woman to deliver a paper at the *American Institute of Electrical Engineers (AIEE)*
- first woman named as a fellow of AIEE



Space vector

$$T_{\alpha\beta/abc} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$
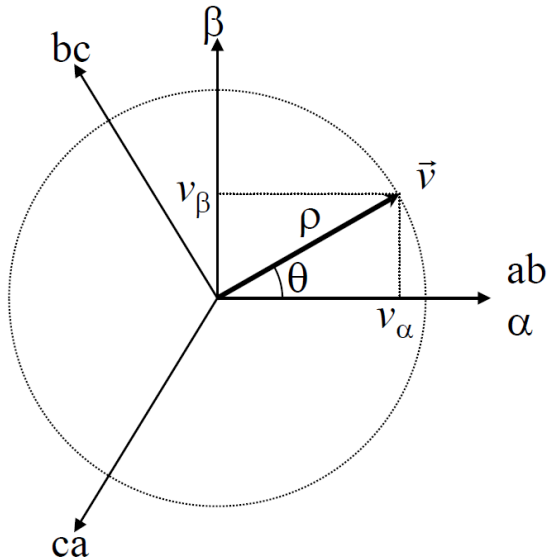
$$\vec{v} = \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} = \begin{bmatrix} V_m \cos(\omega t) \\ V_m \cos(\omega t - 2\pi/3) \\ V_m \cos(\omega t + 2\pi/3) \end{bmatrix}$$




$$\vec{v} = \rho \cdot e^{j\theta}$$

$$\begin{bmatrix} v_{\alpha} \\ v_{\beta} \end{bmatrix} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}$$



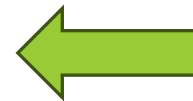
$$\rho = \sqrt{\frac{3}{2}} \cdot V_m, \quad \theta = \omega t$$



$$\rho = \sqrt{v_{\alpha}^2 + v_{\beta}^2}$$

$$\theta = \tan^{-1} \left(\frac{v_{\beta}}{v_{\alpha}} \right)$$

Switching states

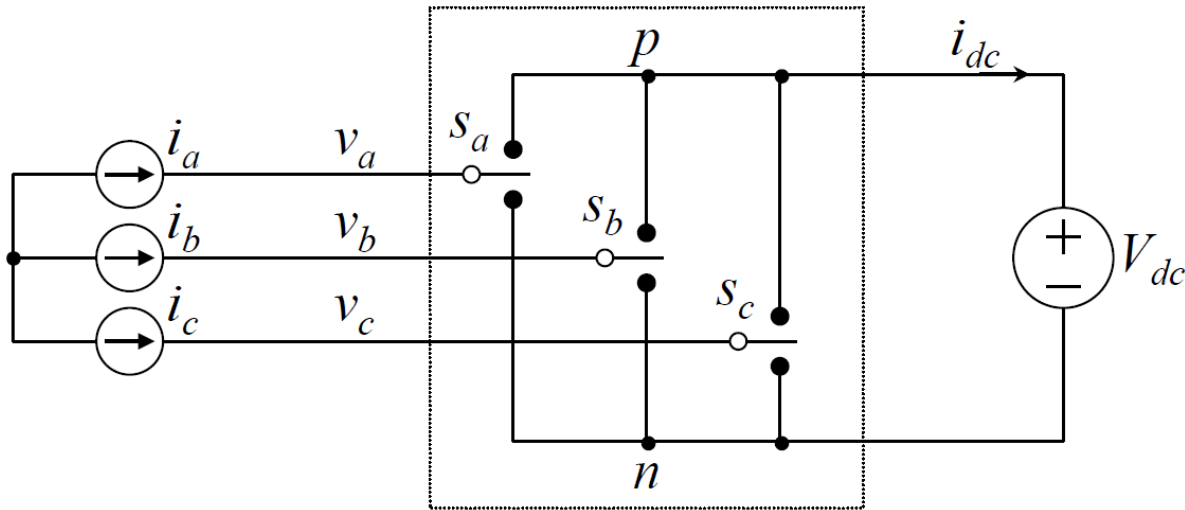


Switching state	i_{dc}	v_{ab}	v_{bc}	v_{ca}
<i>nnn</i>	0	0	0	0
<i>nnp</i>	i_c	0	$-V_{dc}$	V_{dc}
<i>npn</i>	i_b	$-V_{dc}$	V_{dc}	0
<i>npp</i>	$i_b + i_c$	$-V_{dc}$	0	V_{dc}
<i>pnn</i>	i_a	V_{dc}	0	$-V_{dc}$
<i>pnp</i>	$i_a + i_c$	V_{dc}	$-V_{dc}$	0
<i>ppn</i>	$i_a + i_b$	0	V_{dc}	$-V_{dc}$
<i>ppp</i>	$i_a + i_b + i_c$	0	0	0

s_a	s_b	s_c	Switching state
0	0	0	<i>nnn</i>
0	0	1	<i>nnp</i>
0	1	0	<i>npn</i>
0	1	1	<i>npp</i>
1	0	0	<i>pnn</i>
1	0	1	<i>pnp</i>
1	1	0	<i>ppn</i>
1	1	1	<i>ppp</i>

Space vector for state pnn

Switch state: pnn


$$\vec{V}_{pnn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{pnn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{pnn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} V_{dc} \\ 0 \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} \sqrt{\frac{3}{2}} \cdot V_{dc} \\ \sqrt{\frac{1}{2}} \cdot V_{dc} \end{bmatrix}$$

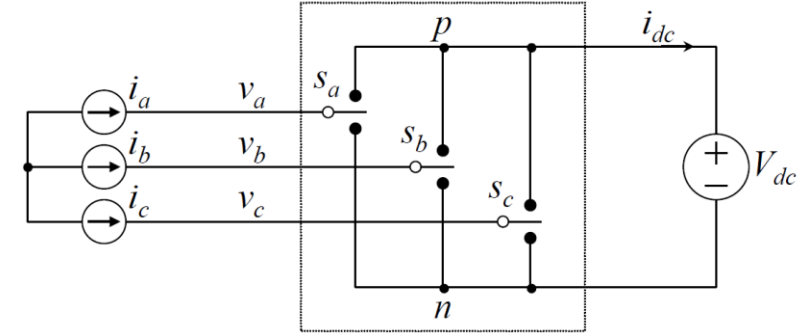

$$\vec{V}_{pnn} = \vec{V}_1 = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$

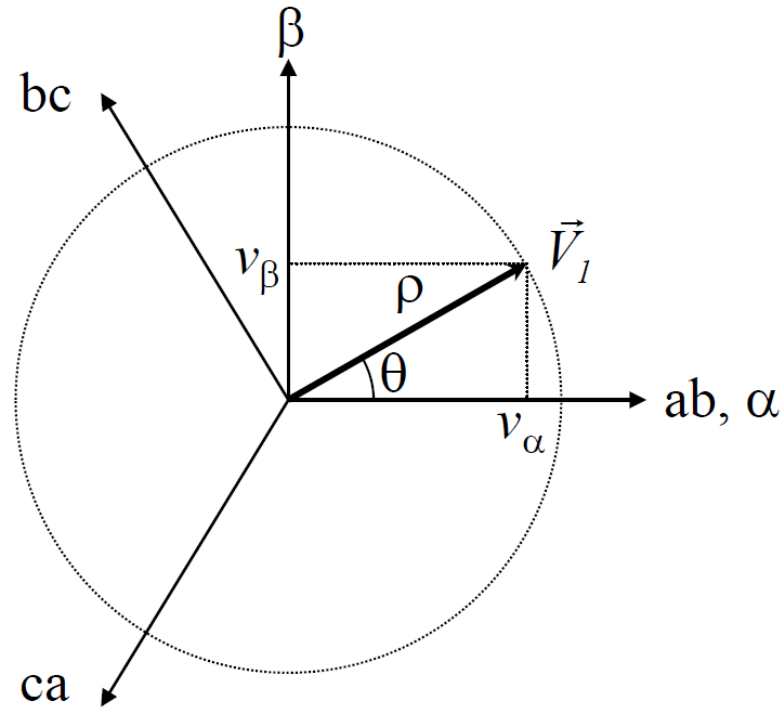
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 30^\circ$$



Space vector for state ppn

Switch state: ppn


$$\vec{V}_{ppn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ V_{dc} \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} 0 \\ \sqrt{2} \cdot V_{dc} \end{bmatrix}$$

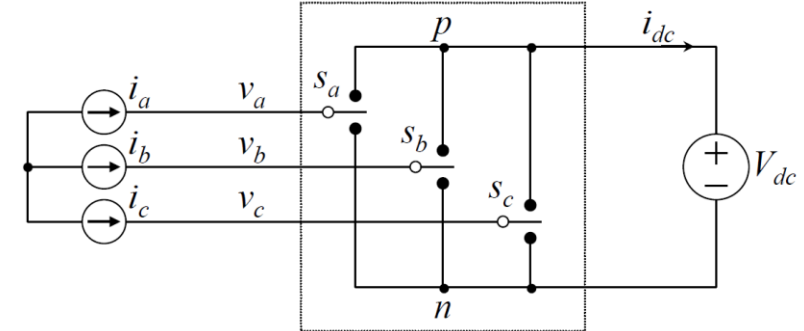

$$\vec{V}_{ppn} = \vec{V}_2 = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$

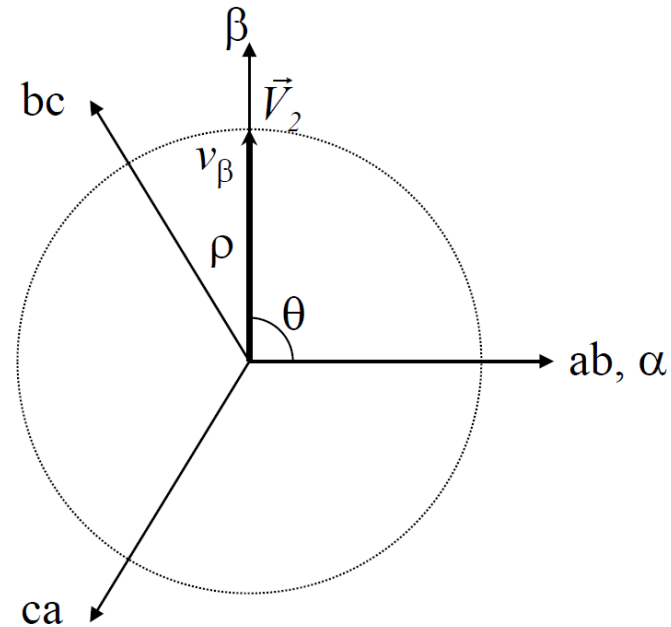
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 90^\circ$$




Space vector for state ppp

Switch state: ppp

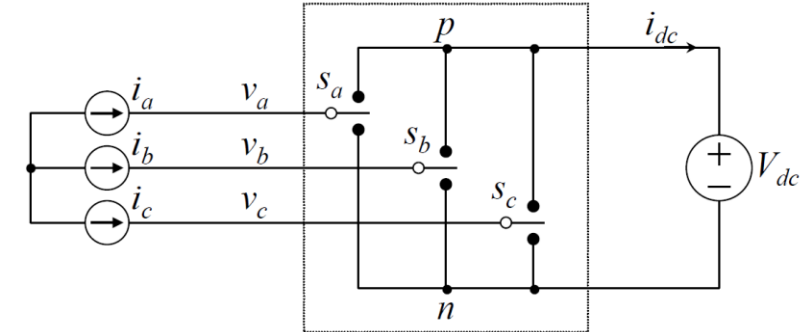
$$\vec{V}_{ppp} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppp} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppp} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$



$$\vec{V}_{ppp} = \vec{V}_0 = 0$$

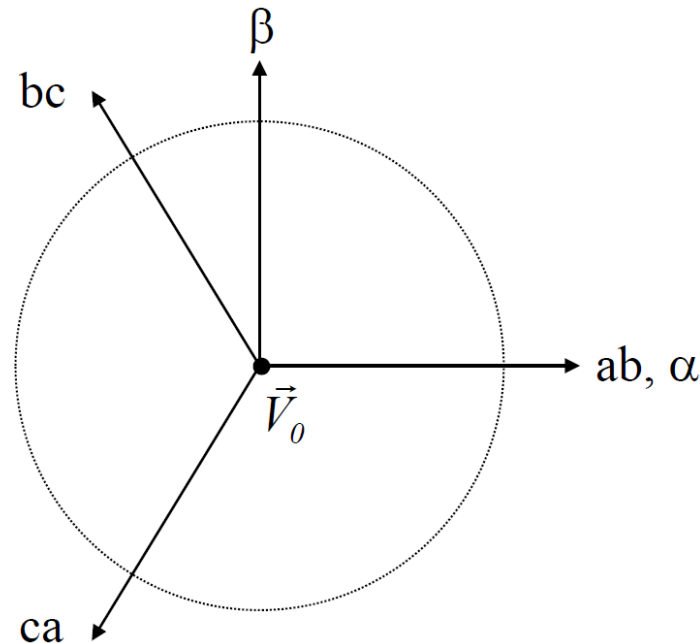

Switching State Vectors

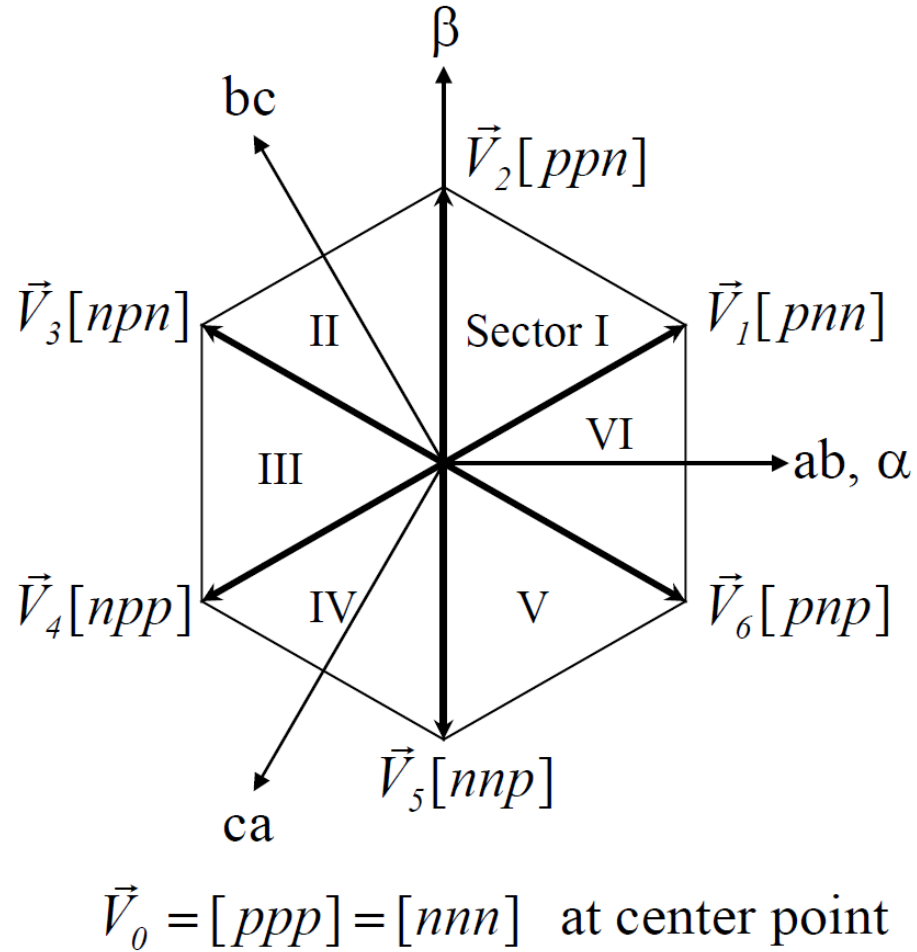


	ρ	$\theta (^{\circ})$
$\vec{V}_1[pnn]$	$\sqrt{2} \cdot V_{dc}$	30
$\vec{V}_2[ppn]$		90
$\vec{V}_3[npn]$		150
$\vec{V}_4[npp]$		-150
$\vec{V}_5[nnp]$		-90
$\vec{V}_6[pnp]$		-30
$\vec{V}_0[ppp]$	0	0
$\vec{V}_0[nnn]$		0


Vector synthesis



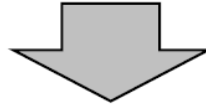Step 1 : Choose desired switching state vectors to synthesize \vec{V}_{ref}



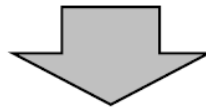Step 2 : Calculate the duty ratios of chosen switching state vectors




Step 3 : Make the sequence of chosen switching state vectors

Vector selection

- Minimize the number of switching
- Minimize the harmonic distortion


☞ **Nearest Three Vectors (NTV)**

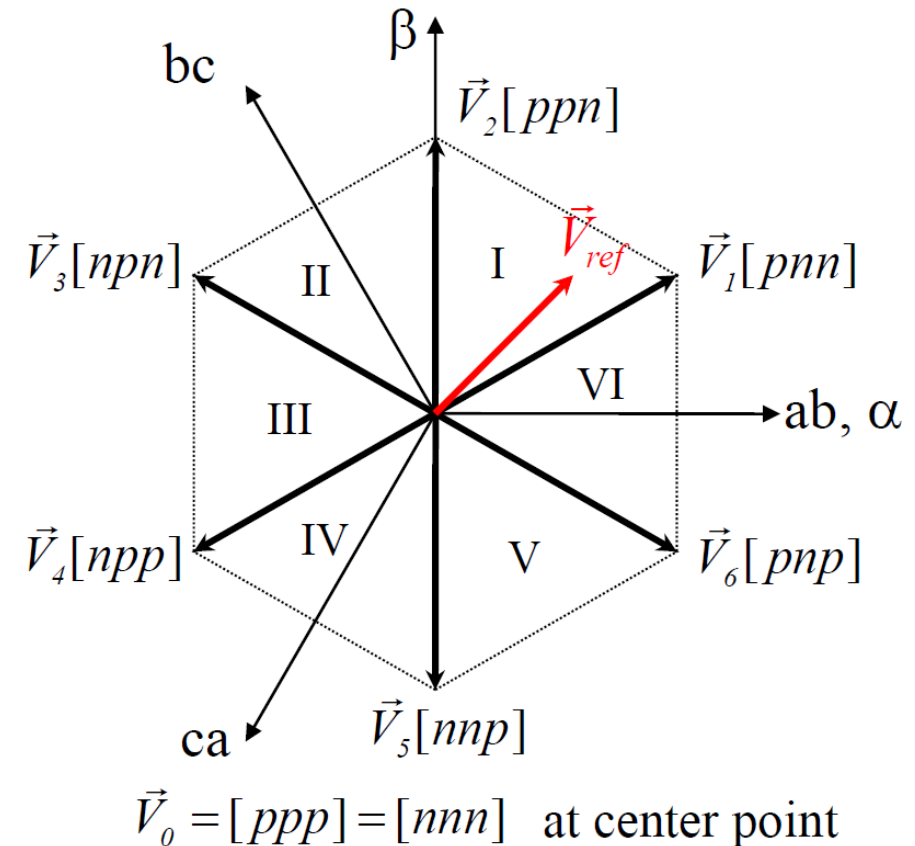


High frequency synthesis

$$\int_0^{T_S} \vec{V}_{ref} dt = \sum_i \left(\int_0^{T_i} \vec{V}_i dt \right), \quad \sum_i T_i = T_S$$

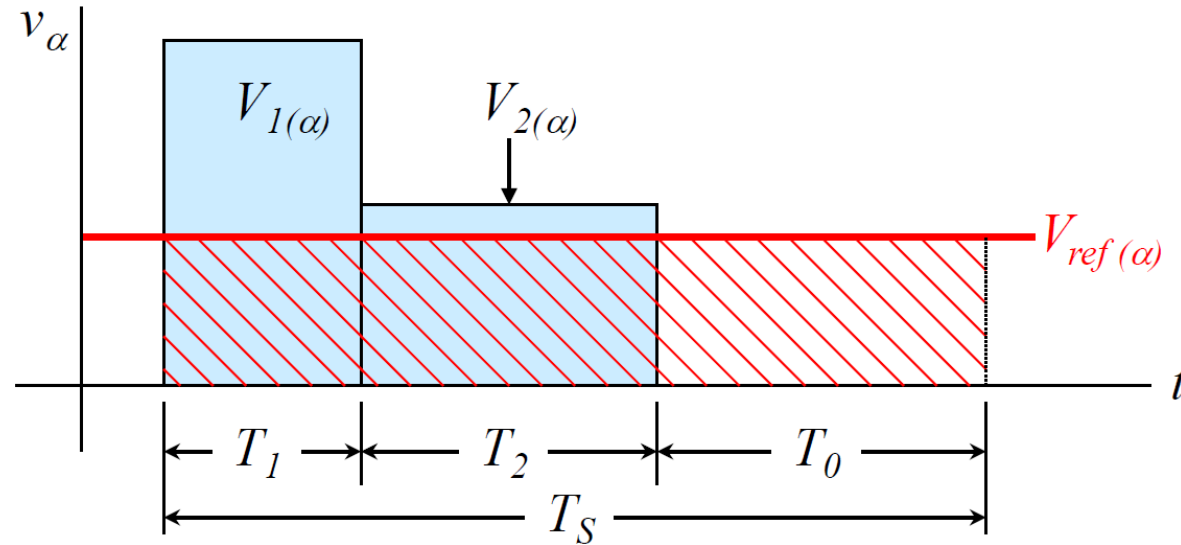For example
$$\int_0^{T_S} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_S} \vec{V}_0 dt$$



Total area of  = Area of 

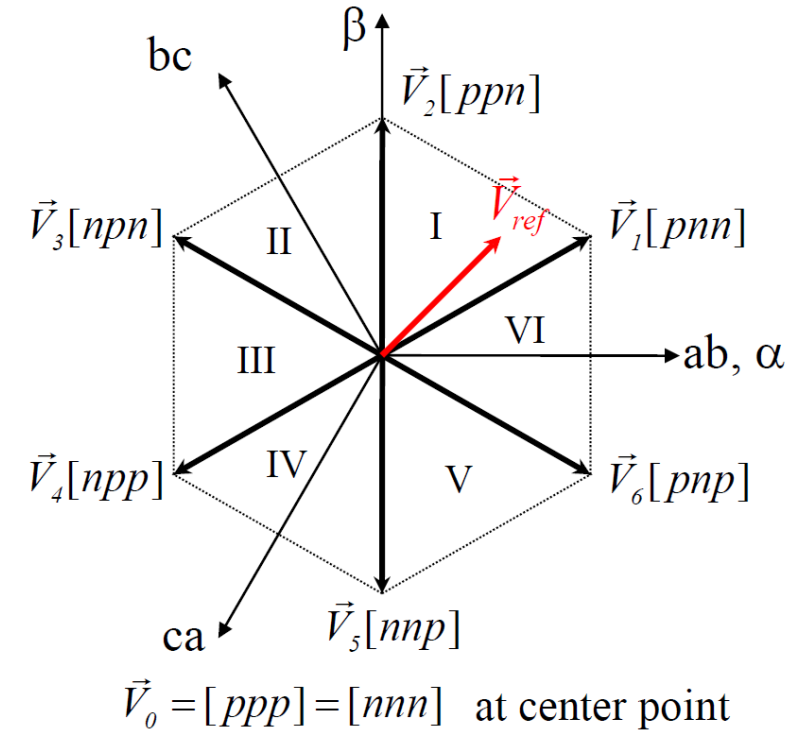

Duty ratio in sector I

From HF synthesis definition, $\int_0^{T_s} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_s} \vec{V}_0 dt$

Assume \vec{V}_{ref} is constant in T_s , $\vec{V}_{ref} \cdot T_s = \vec{V}_1 \cdot T_1 + \vec{V}_2 \cdot T_2$


$$\rho \cdot \begin{bmatrix} \cos \phi \\ \sin \phi \end{bmatrix} \cdot T_s = \|V_1\| \cdot \begin{bmatrix} 1 \\ 0 \end{bmatrix} \cdot T_1 + \|V_2\| \cdot \begin{bmatrix} \cos 60^\circ \\ \sin 60^\circ \end{bmatrix} \cdot T_2$$

where $\phi = \theta - 30^\circ$

$$\frac{T_1}{T_s} = d_1 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_1\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_2}{T_s} = d_2 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_2\|} \cdot \sin \phi$$

$$d_0 = 1 - d_1 - d_2$$

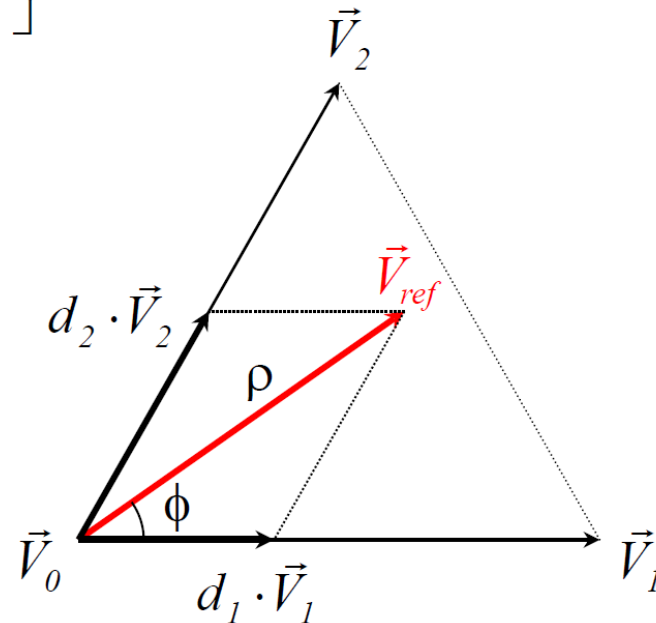

Duty ratio in other sectors


➡ Other sectors have the same results of duty ratio.

$$\frac{T_N}{T_S} = d_N = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_N\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_{N+1}}{T_S} = d_{N+1} = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_{N+1}\|} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

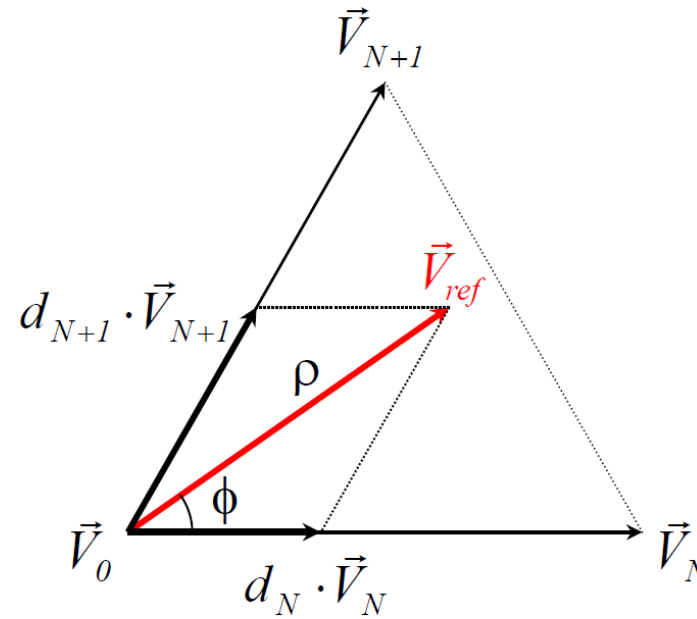where $\phi = \theta - (N-1) \cdot 60^\circ - 30^\circ$
 N : sector number (1 ~ 6)



$$\vec{V}_{ref(steady-state)} = \rho \cdot e^{j\theta} = \sqrt{\frac{3}{2}} \cdot V_m \cdot e^{j\omega t}$$

Modulation index

For all the switching state vectors, $\|V_N\| = \sqrt{2} \cdot V_{dc}$ and $\rho = \sqrt{\frac{3}{2}} \cdot V_m$

$$d_N = \frac{V_m}{V_{dc}} \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = \frac{V_m}{V_{dc}} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

Define the modulation index $M = \frac{V_m}{V_{dc}}$


$$d_N = M \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = M \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$


Vector sequence – 3ph, symmetric

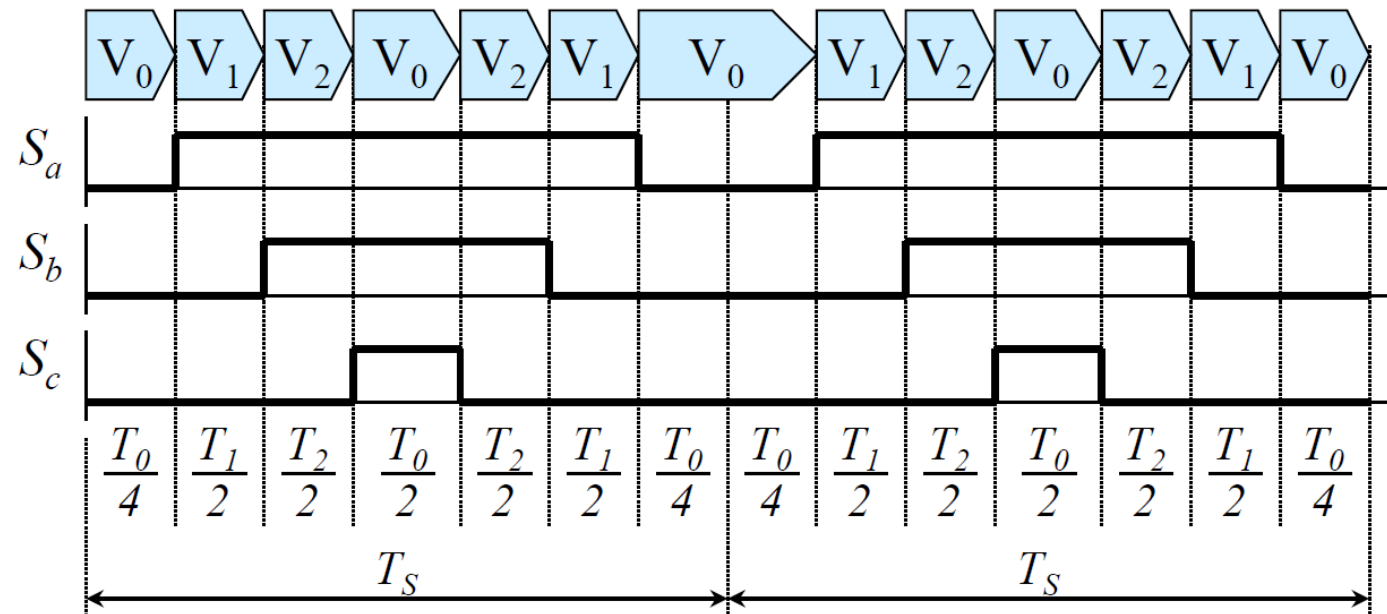- Use both zero switching state vectors
- Symmetrical sequence \longrightarrow Low THD
- Six commutations per switching cycle



Vector sequence – 2ph, symmetric

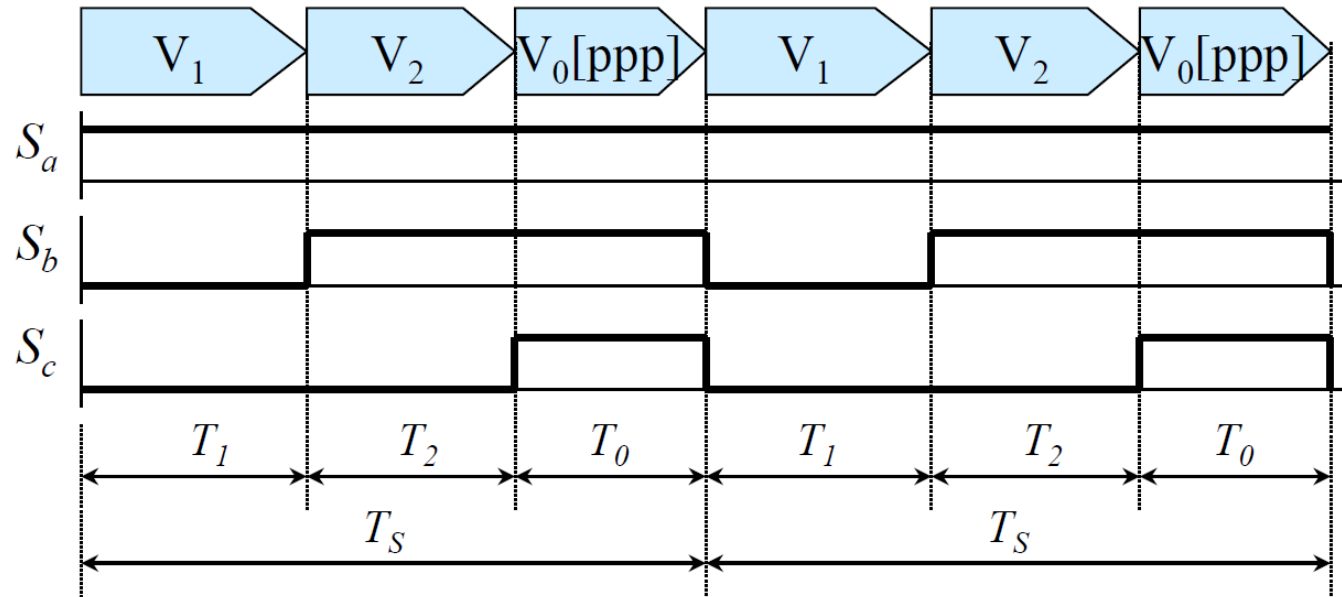- Use a zero vector in one switching cycle $\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Asymmetrical sequence
- Four commutations \longrightarrow Reduced switching losses



Thank you!