

Electric Vehicle (EE60082)

Lecture 9: Motor drive for EV (part 5)


DR. SHIMUL K. DAM

ASSISTANT PROFESSOR,
DEPARTMENT OF ELECTRICAL ENGINEERING,
INDIAN INSTITUTE OF TECHNOLOGY (IIT), KHARAGPUR.





AC sources for AC Machines



Generation of AC voltage(recap)

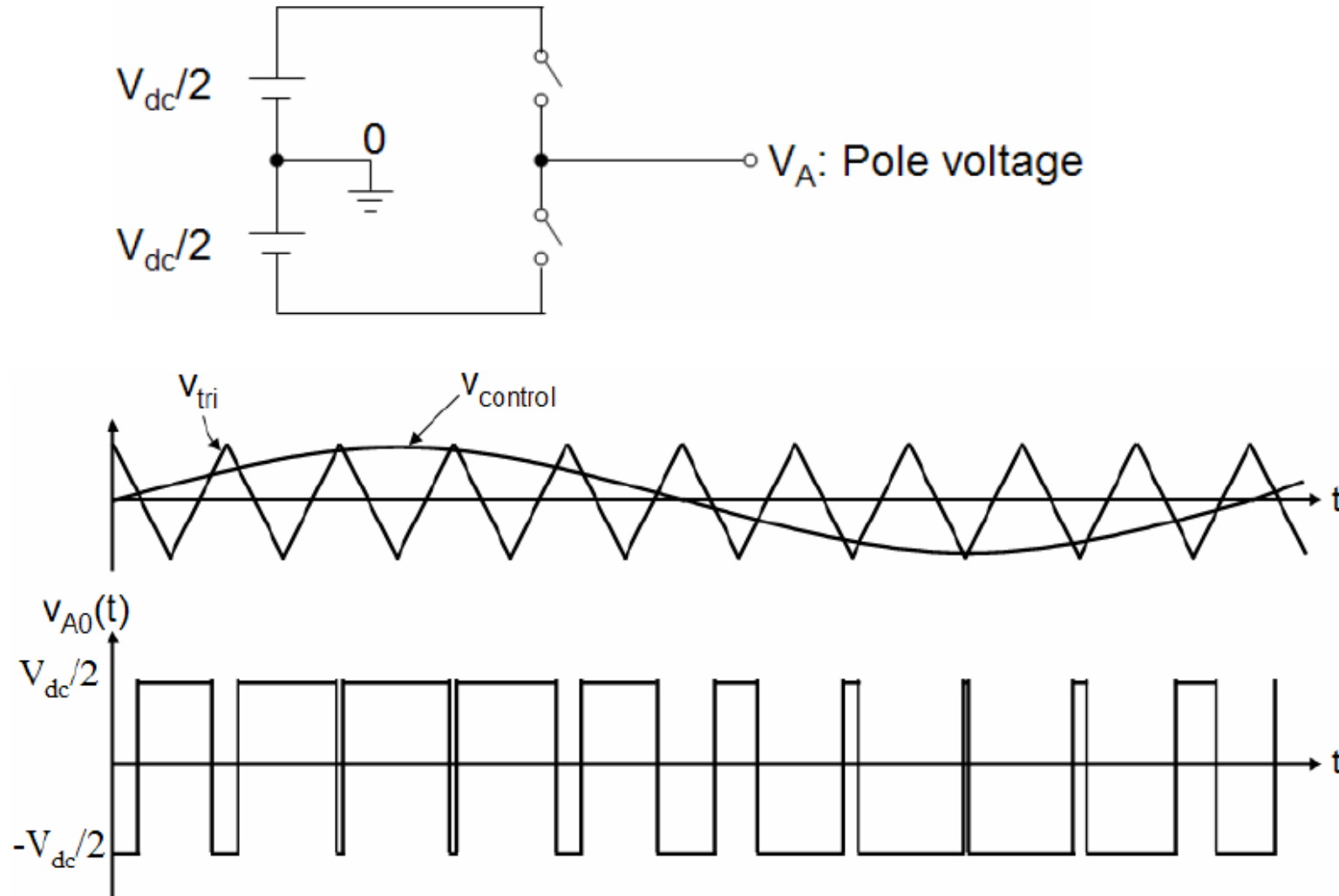


AC generation with H-bridge (recap)

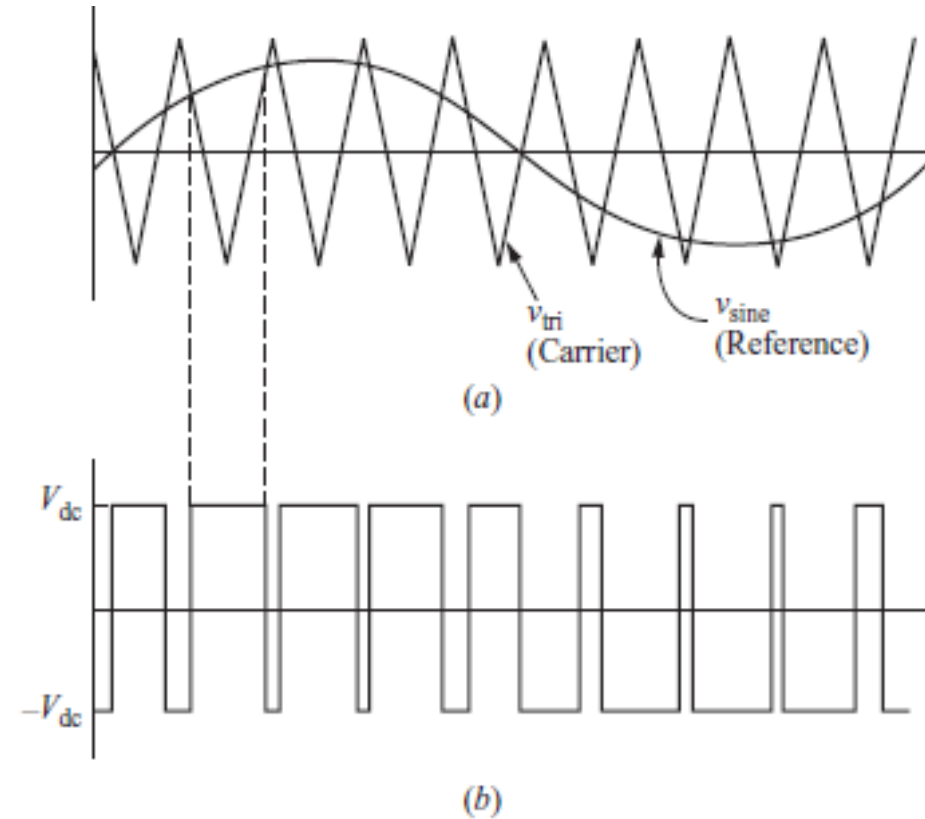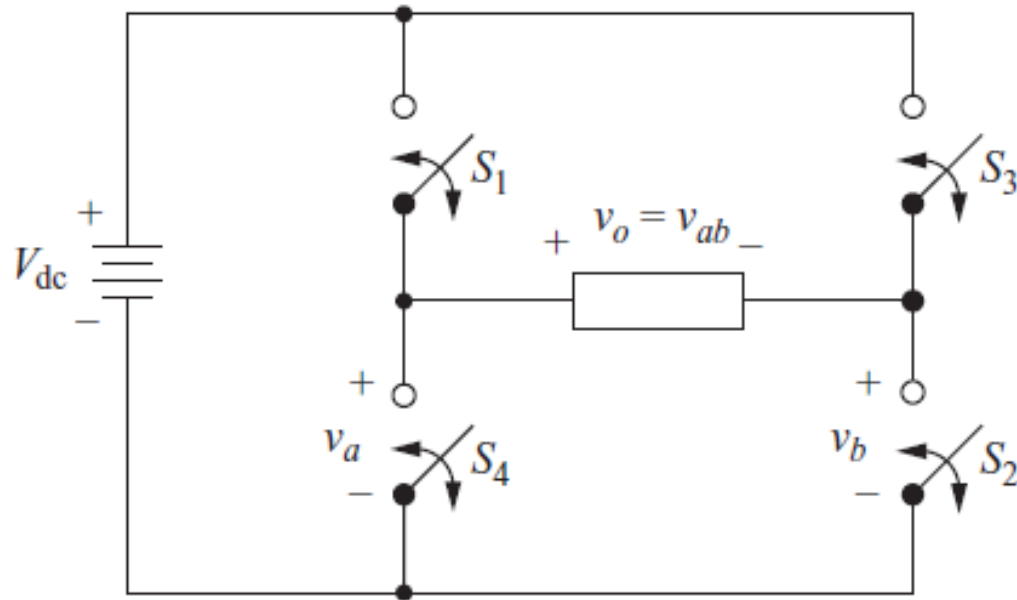

Three-phase voltage generation (recap)

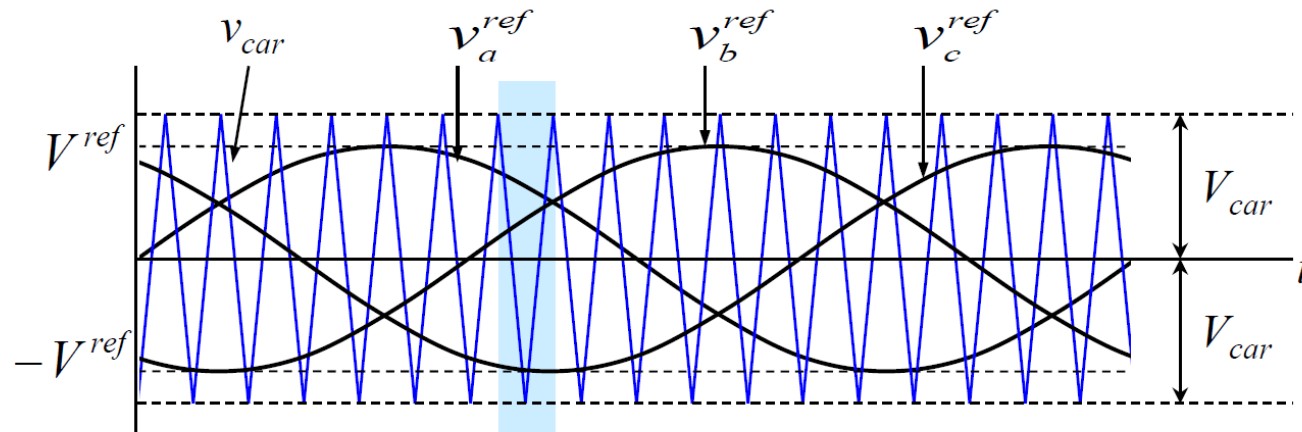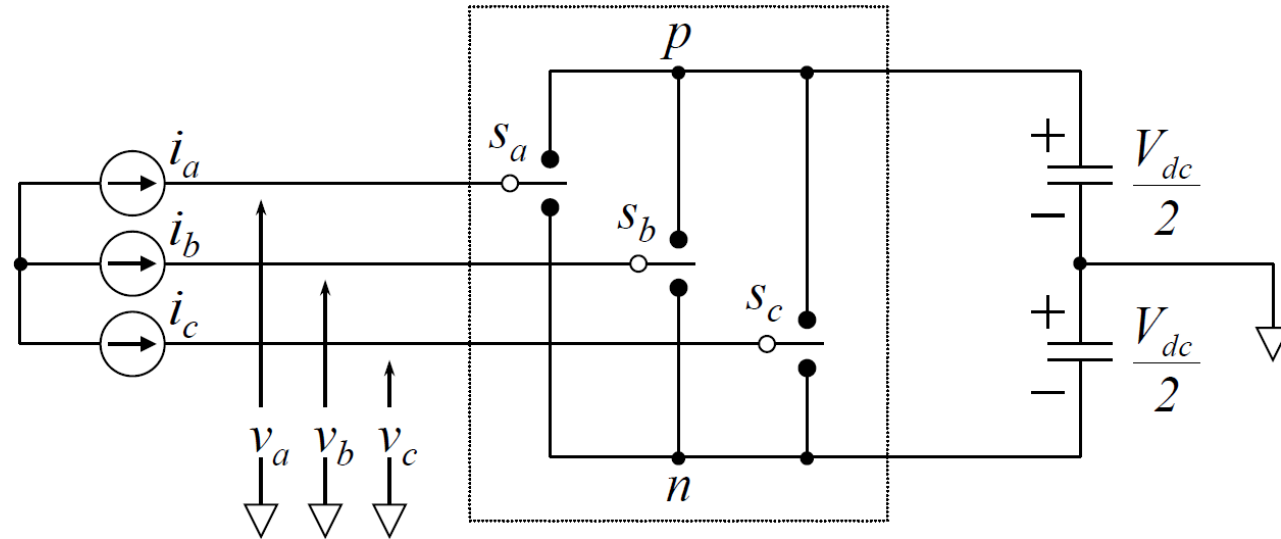

Clarke's Transformation (recap)

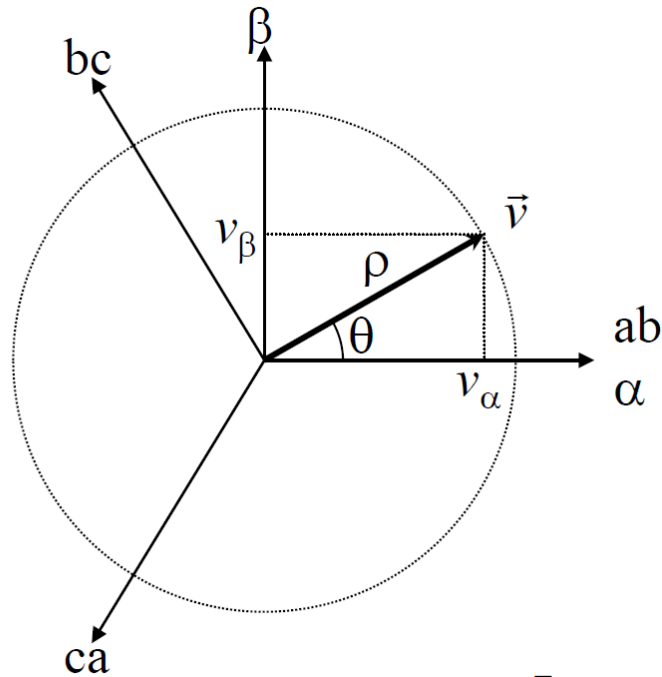

$$T_{\alpha\beta/abc} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$

➤ A bit of history

➤ Edith Clarke (1883-1959)


- The first professional woman electrical engineer in US
- first female professor of electrical engineering
- first woman to deliver a paper at the *American Institute of Electrical Engineers (AIEE)*
- first woman named as a fellow of AIEE



Space vector (recap)

$$T_{\alpha\beta/abc} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$
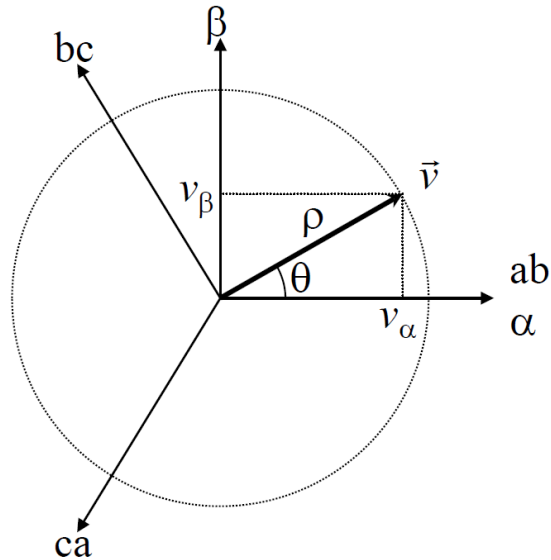
$$\vec{v} = \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} = \begin{bmatrix} V_m \cos(\omega t) \\ V_m \cos(\omega t - 2\pi/3) \\ V_m \cos(\omega t + 2\pi/3) \end{bmatrix}$$



$$\vec{v} = \rho \cdot e^{j\theta}$$

$$\begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}$$




$$\rho = \sqrt{\frac{3}{2}} \cdot V_m, \quad \theta = \omega t$$



$$\rho = \sqrt{v_\alpha^2 + v_\beta^2}$$

$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right)$$

Switching states (recap)

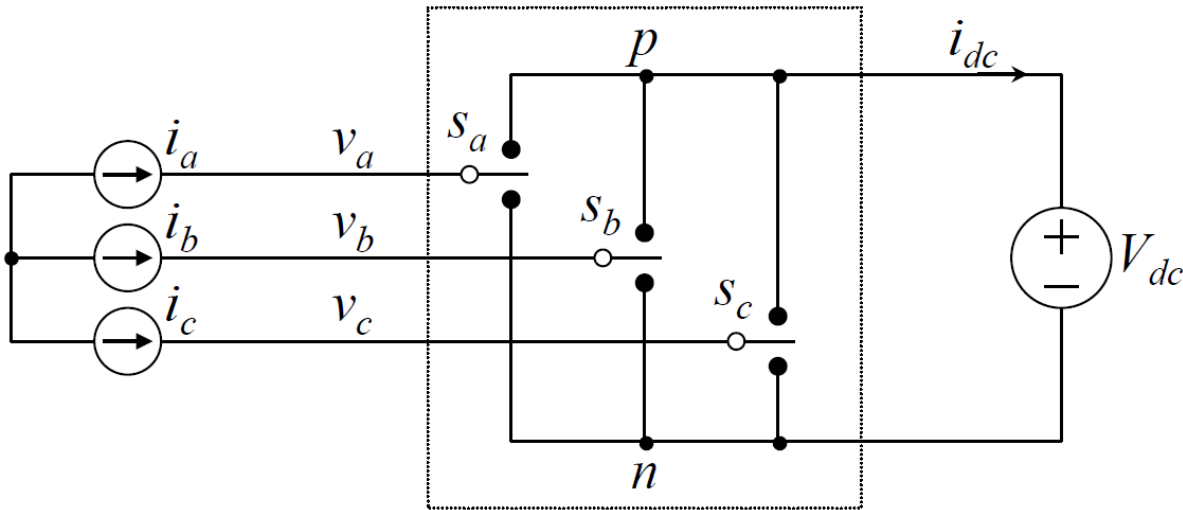


Switching state	i_{dc}	v_{ab}	v_{bc}	v_{ca}
<i>nnn</i>	0	0	0	0
<i>nnp</i>	i_c	0	$-V_{dc}$	V_{dc}
<i>npn</i>	i_b	$-V_{dc}$	V_{dc}	0
<i>npp</i>	$i_b + i_c$	$-V_{dc}$	0	V_{dc}
<i>pnn</i>	i_a	V_{dc}	0	$-V_{dc}$
<i>pnp</i>	$i_a + i_c$	V_{dc}	$-V_{dc}$	0
<i>ppn</i>	$i_a + i_b$	0	V_{dc}	$-V_{dc}$
<i>ppp</i>	$i_a + i_b + i_c$	0	0	0

s_a	s_b	s_c	Switching state
0	0	0	<i>nnn</i>
0	0	1	<i>nnp</i>
0	1	0	<i>npn</i>
0	1	1	<i>npp</i>
1	0	0	<i>pnn</i>
1	0	1	<i>pnp</i>
1	1	0	<i>ppn</i>
1	1	1	<i>ppp</i>

Space vector for state pnn (recap)

Switch state: pnn


$$\vec{V}_{pnn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{pnn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{pnn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} V_{dc} \\ 0 \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} \sqrt{\frac{3}{2}} \cdot V_{dc} \\ \sqrt{\frac{1}{2}} \cdot V_{dc} \end{bmatrix}$$

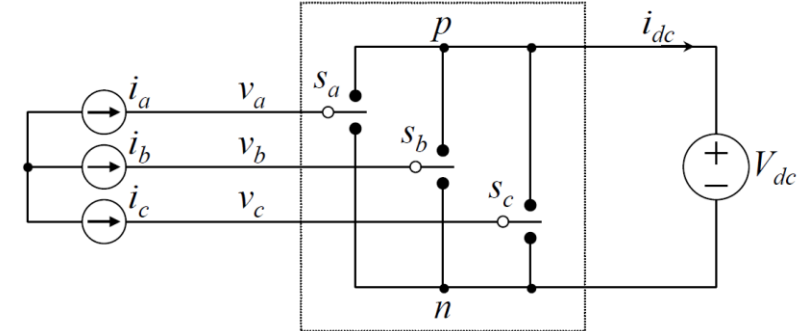

$$\vec{V}_{pnn} = \vec{V}_1 = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$

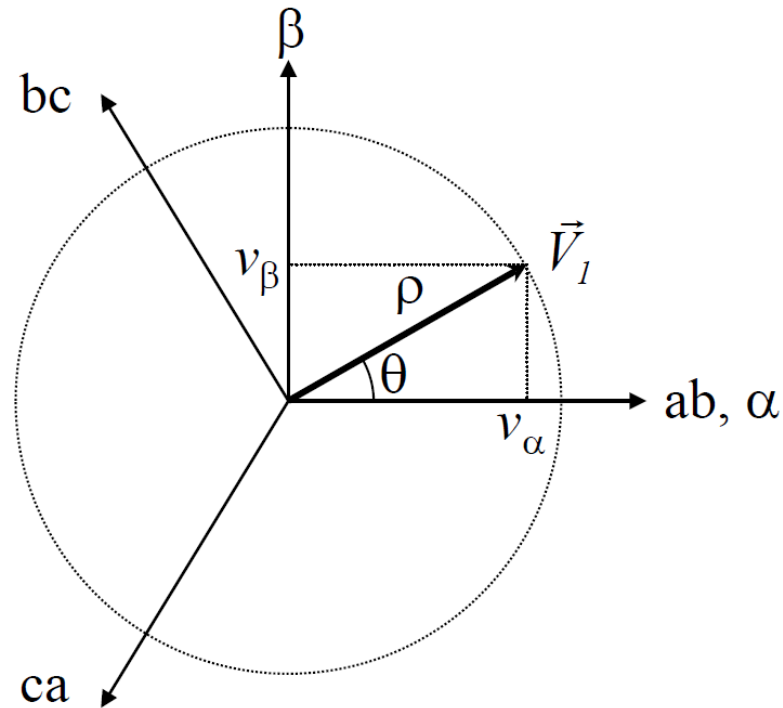
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 30^\circ$$



Space vector for state ppn (recap)

Switch state: ppn


$$\vec{V}_{ppn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ V_{dc} \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} 0 \\ \sqrt{2} \cdot V_{dc} \end{bmatrix}$$

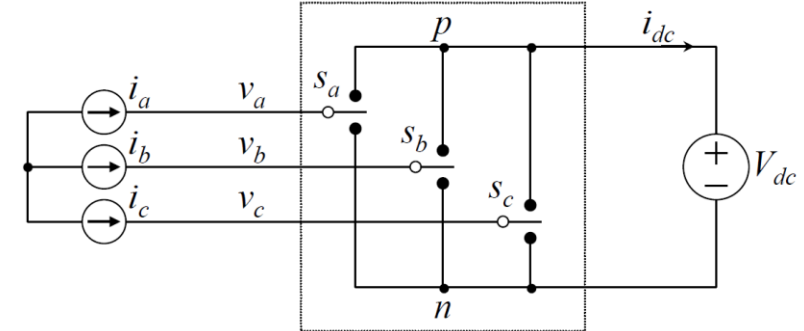

$$\vec{V}_{ppn} = \vec{V}_2 = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$

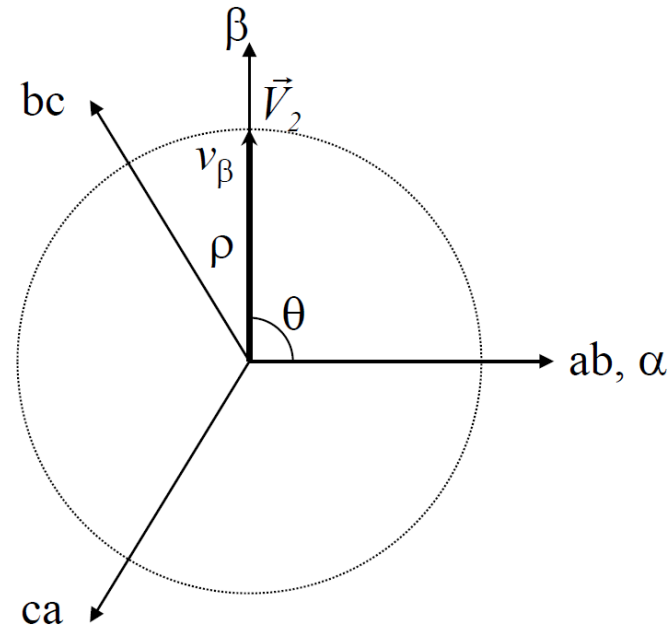
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 90^\circ$$




Space vector for state ppp (recap)

Switch state: ppp

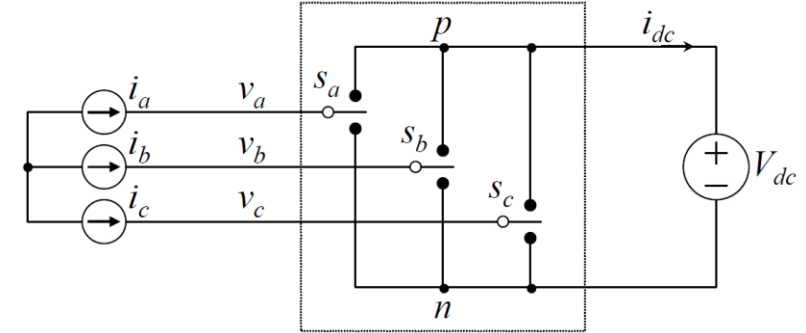
$$\vec{V}_{ppp} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppp} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppp} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$



$$\vec{V}_{ppp} = \vec{V}_0 = 0$$

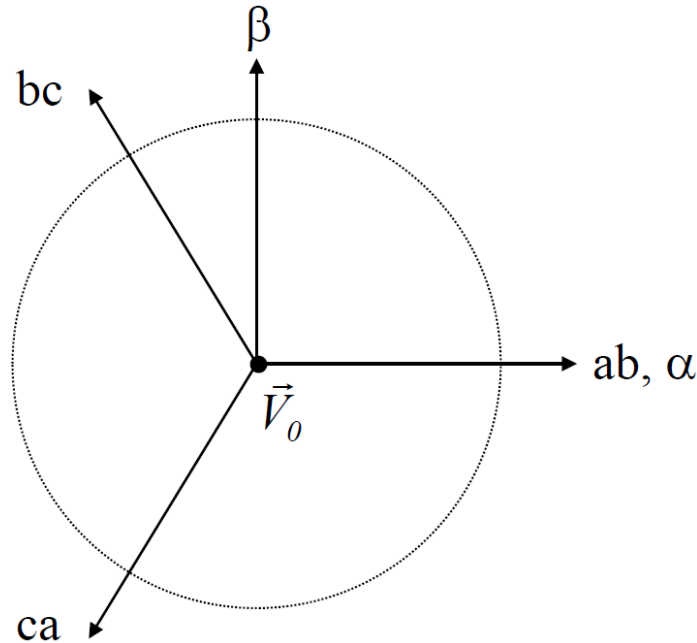


Switching State Vectors

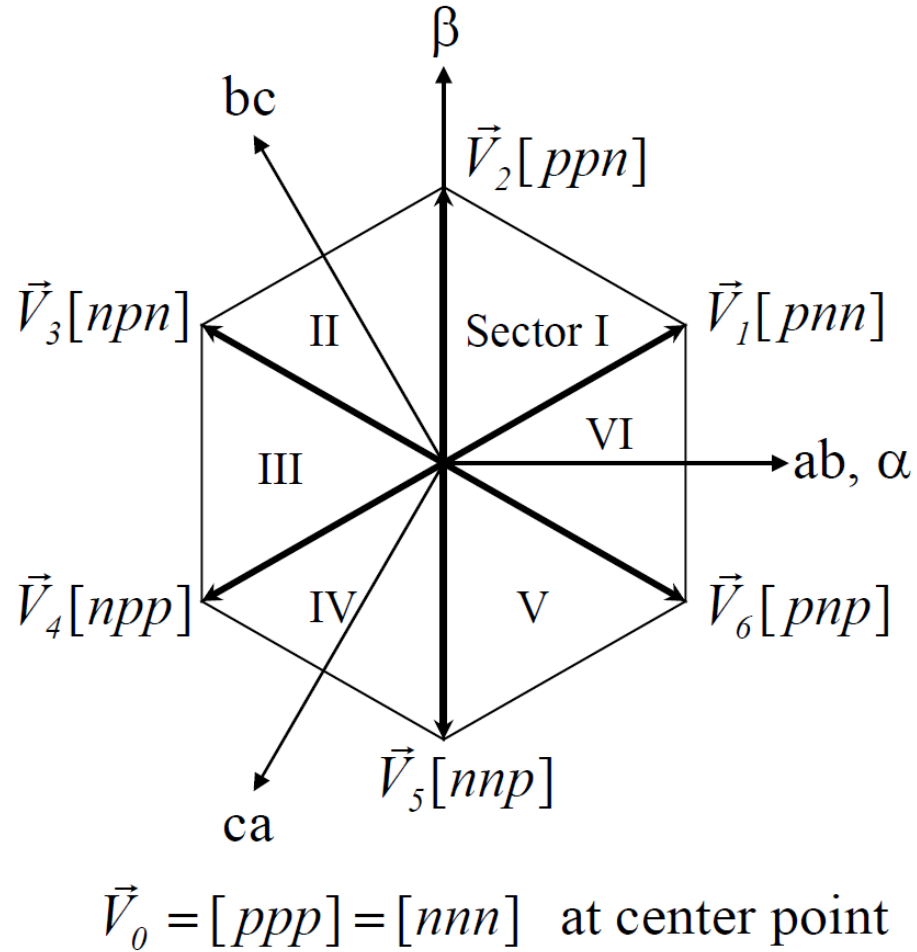


	ρ	$\theta (^{\circ})$
$\vec{V}_1[pnn]$	$\sqrt{2} \cdot V_{dc}$	30
$\vec{V}_2[ppn]$		90
$\vec{V}_3[npn]$		150
$\vec{V}_4[npp]$		-150
$\vec{V}_5[nnp]$		-90
$\vec{V}_6[pnp]$		-30
$\vec{V}_0[ppp]$	0	0
$\vec{V}_0[nnn]$		0

Vector synthesis (recap)

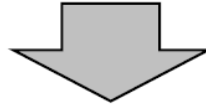Step 1 : Choose desired switching state vectors to synthesize \vec{V}_{ref}



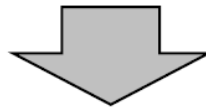Step 2 : Calculate the duty ratios of chosen switching state vectors




Step 3 : Make the sequence of chosen switching state vectors

Vector selection (recap)

- Minimize the number of switching
- Minimize the harmonic distortion


☞ **Nearest Three Vectors (NTV)**

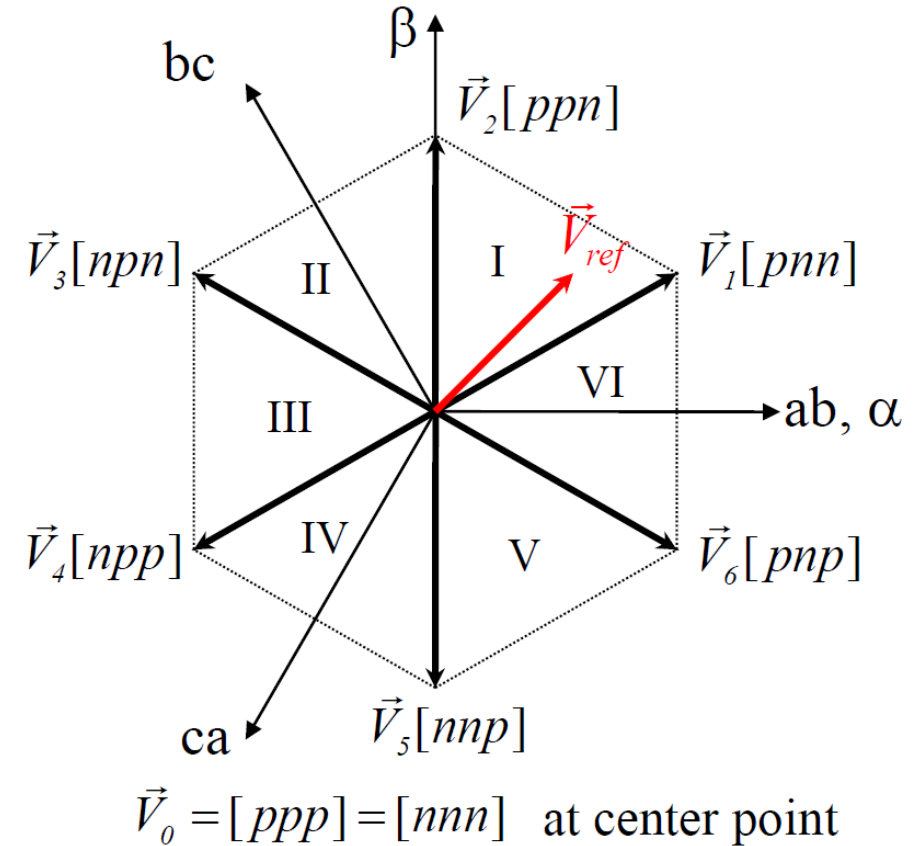


High frequency synthesis (recap)

$$\int_0^{T_S} \vec{V}_{ref} dt = \sum_i \left(\int_0^{T_i} \vec{V}_i dt \right), \quad \sum_i T_i = T_S$$

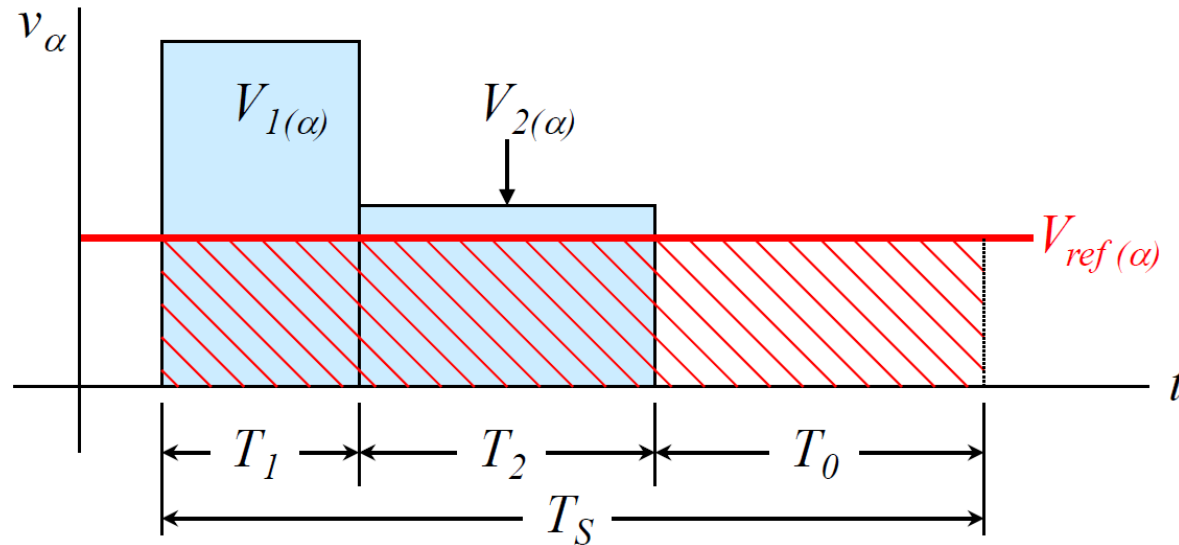For example
$$\int_0^{T_S} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_S} \vec{V}_0 dt$$



Total area of  = Area of 

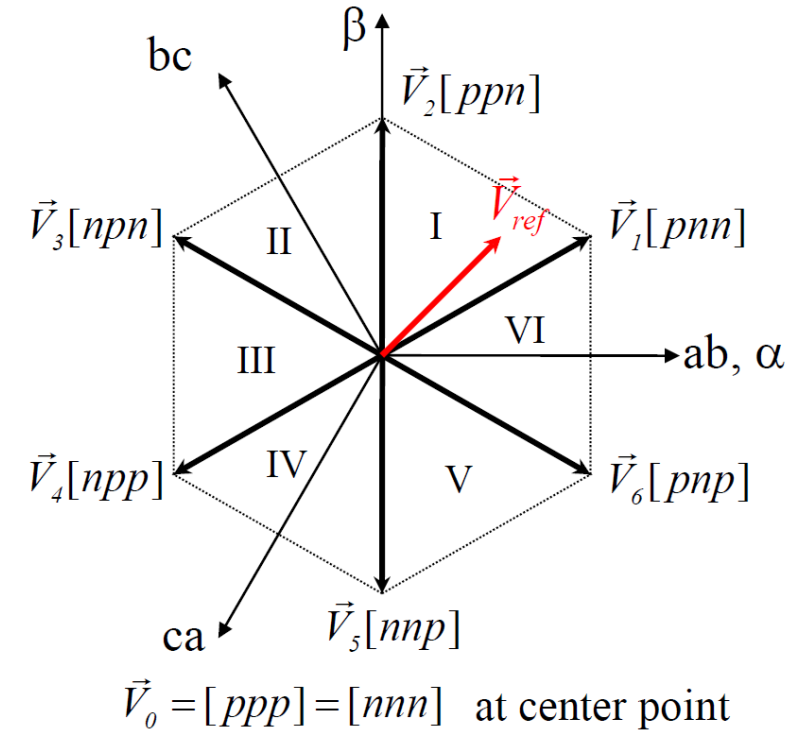

Duty ratio in sector I (recap)

From HF synthesis definition, $\int_0^{T_s} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_s} \vec{V}_0 dt$

Assume \vec{V}_{ref} is constant in T_s , $\vec{V}_{ref} \cdot T_s = \vec{V}_1 \cdot T_1 + \vec{V}_2 \cdot T_2$


$$\rho \cdot \begin{bmatrix} \cos \phi \\ \sin \phi \end{bmatrix} \cdot T_s = \|V_1\| \cdot \begin{bmatrix} 1 \\ 0 \end{bmatrix} \cdot T_1 + \|V_2\| \cdot \begin{bmatrix} \cos 60^\circ \\ \sin 60^\circ \end{bmatrix} \cdot T_2$$

where $\phi = \theta - 30^\circ$

$$\frac{T_1}{T_s} = d_1 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_1\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_2}{T_s} = d_2 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_2\|} \cdot \sin \phi$$

$$d_0 = 1 - d_1 - d_2$$

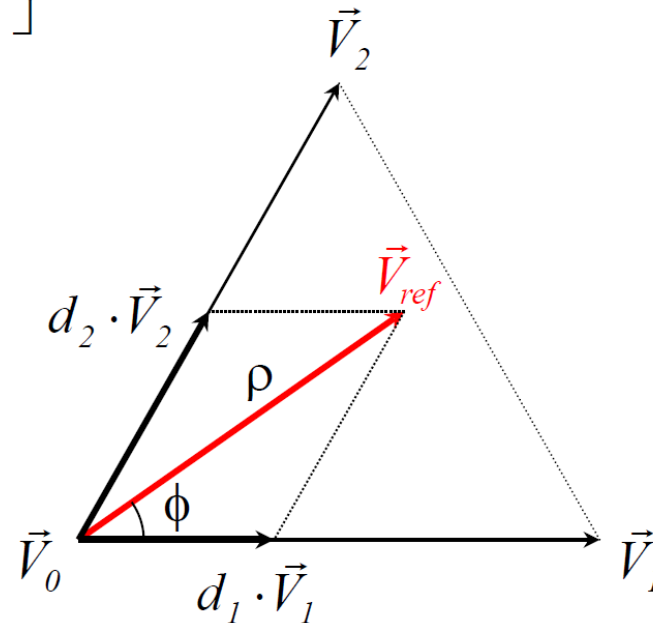

Duty ratio in other sectors (recap)


➡ Other sectors have the same results of duty ratio.

$$\frac{T_N}{T_S} = d_N = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_N\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_{N+1}}{T_S} = d_{N+1} = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_{N+1}\|} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

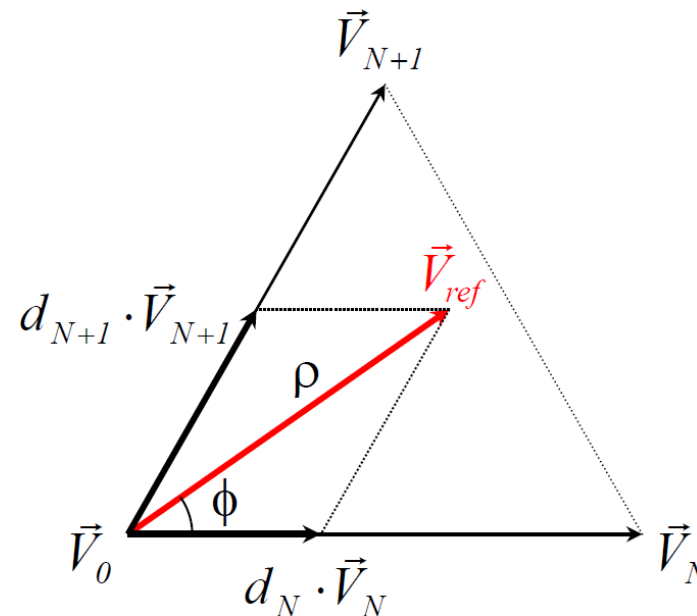where $\phi = \theta - (N-1) \cdot 60^\circ - 30^\circ$
 N : sector number (1 ~ 6)



$$\vec{V}_{ref(steady-state)} = \rho \cdot e^{j\theta} = \sqrt{\frac{3}{2}} \cdot V_m \cdot e^{j\omega t}$$

Modulation index (recap)

For all the switching state vectors, $\|V_N\| = \sqrt{2} \cdot V_{dc}$ and $\rho = \sqrt{\frac{3}{2}} \cdot V_m$

$$d_N = \frac{V_m}{V_{dc}} \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = \frac{V_m}{V_{dc}} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

Define the modulation index $M = \frac{V_m}{V_{dc}}$

$$d_N = M \cdot \sin(60^\circ - \phi)$$


$$d_{N+1} = M \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

Vector sequence – 3ph, symmetric (recap)



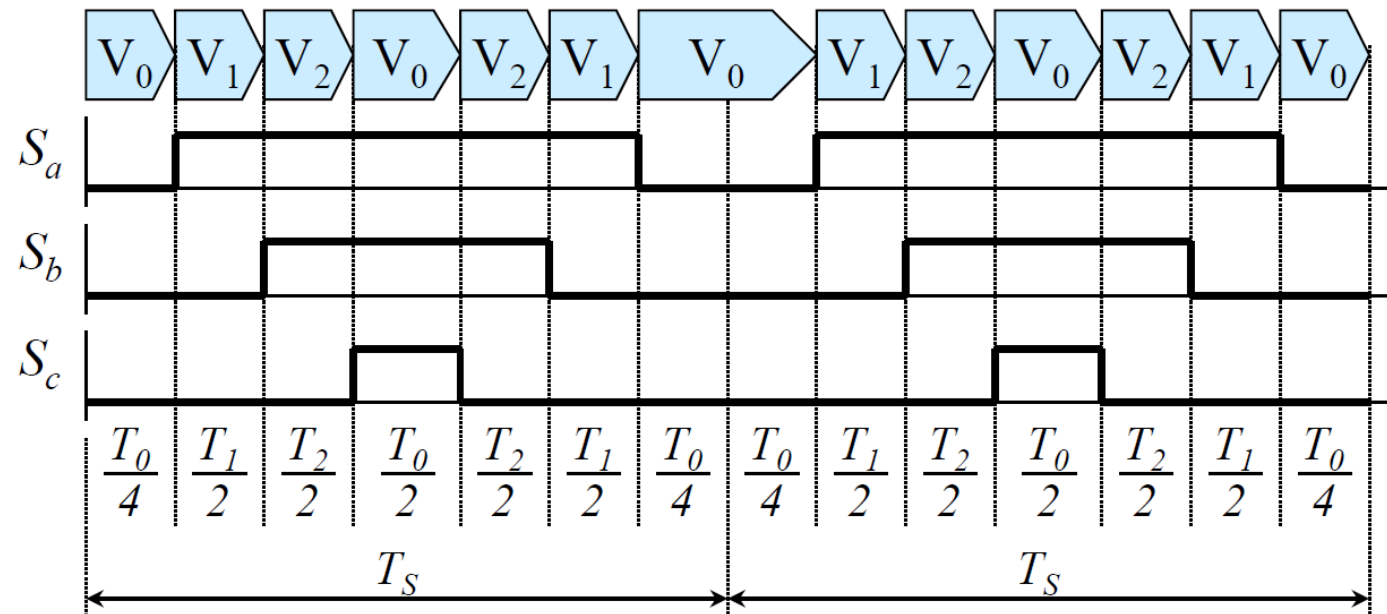
- Use both zero switching state vectors
- Symmetrical sequence \longrightarrow Low THD
- Six commutations per switching cycle



Vector sequence – 2ph, asymmetric (recap)




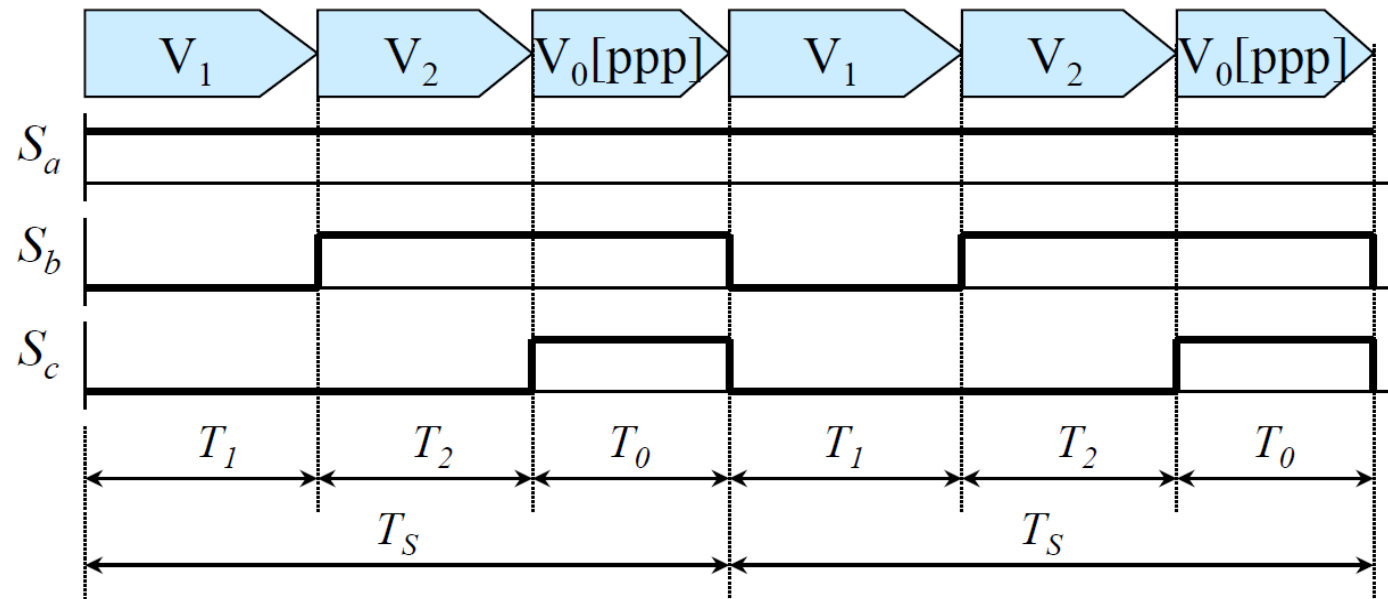- Use a zero vector in one switching cycle $\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Asymmetrical sequence
- Four commutations \longrightarrow Reduced switching losses



Vector sequence – 2ph, symmetric

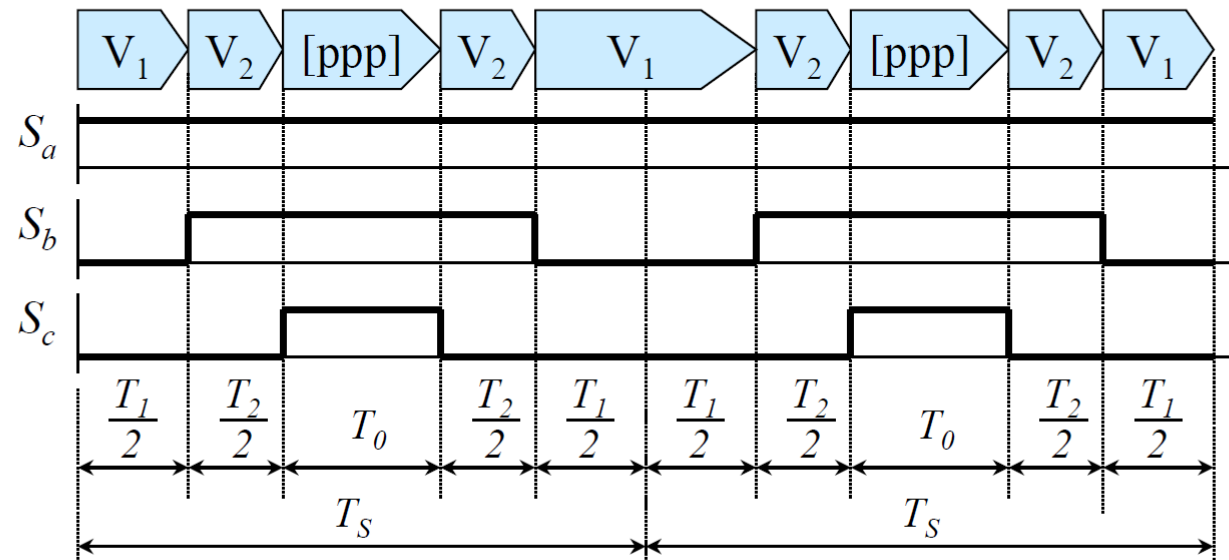- Use a zero vector in one switching cycle $\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Symmetrical sequence \longrightarrow Low THD
- Four commutations \longrightarrow Reduced switching losses




< Example in sector I >

AC voltage generation with space vector


Example:

- DC voltage, $V_{dc} = 400V$
- Switching frequency, $f_{sw} = 100 \text{ kHz}$
- Line frequency, $f_{line} = 100 \text{ Hz}$
- R-L load, $1\Omega, 1\mu H$


VSI simulation

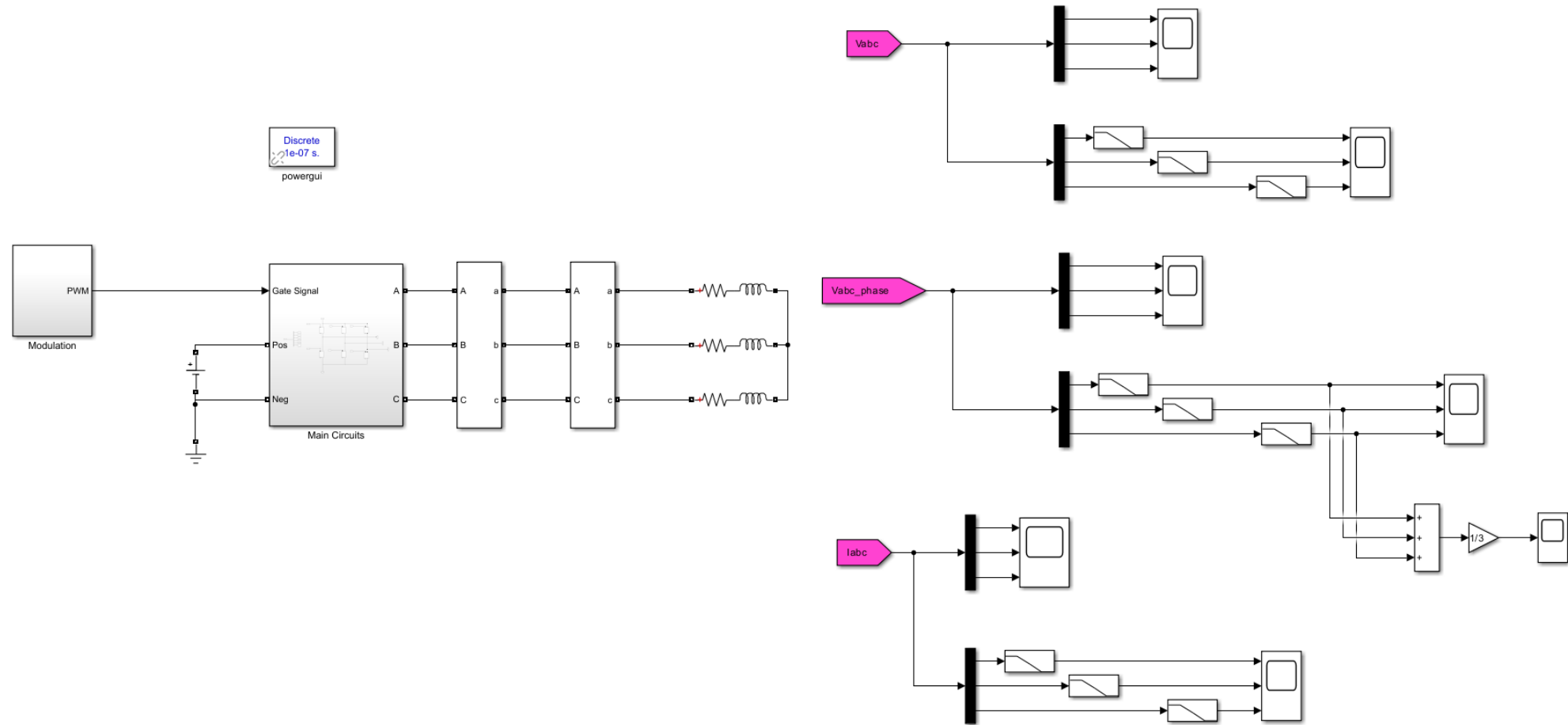

VSI simulation

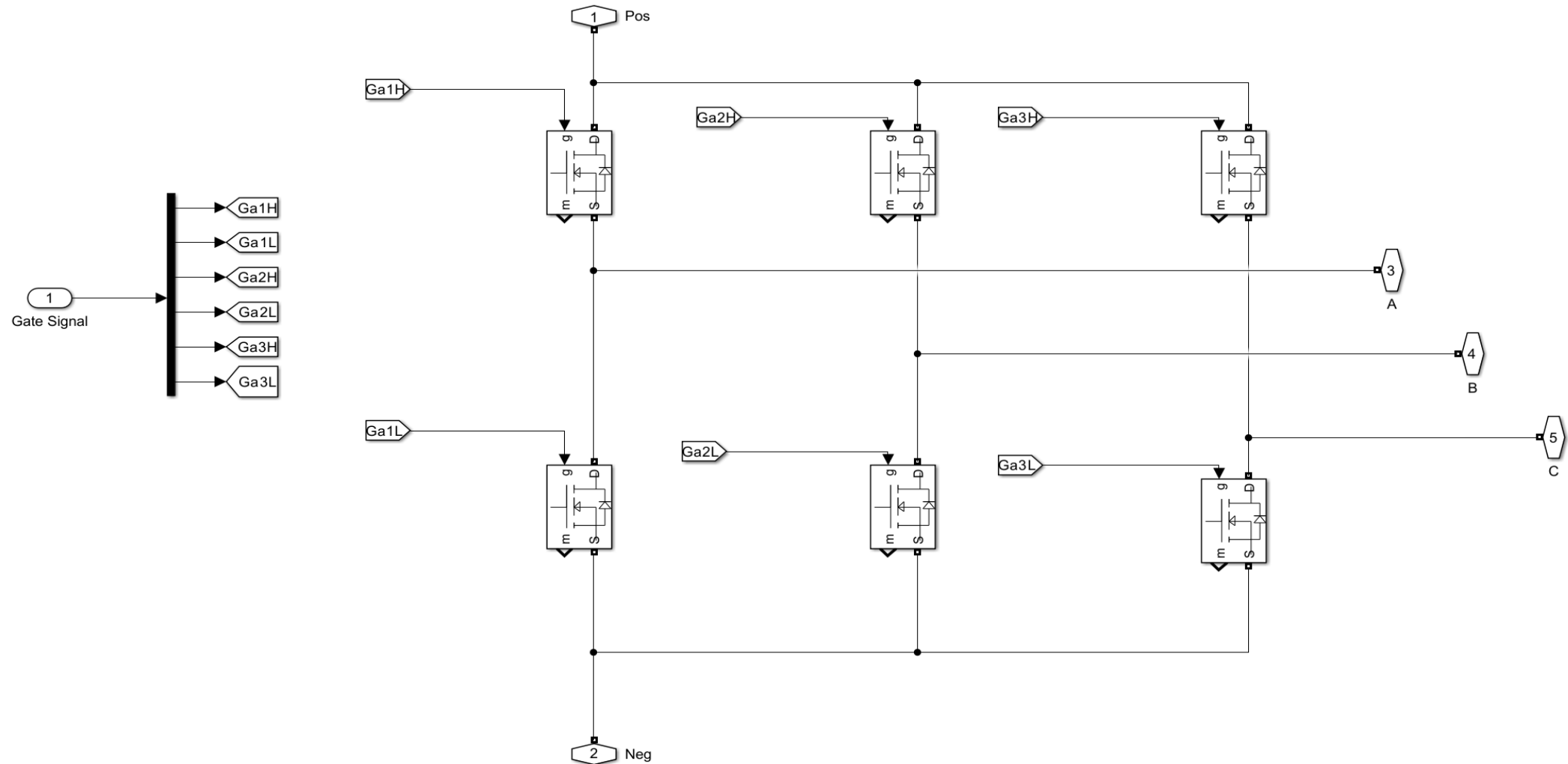

VSI simulation - modulation

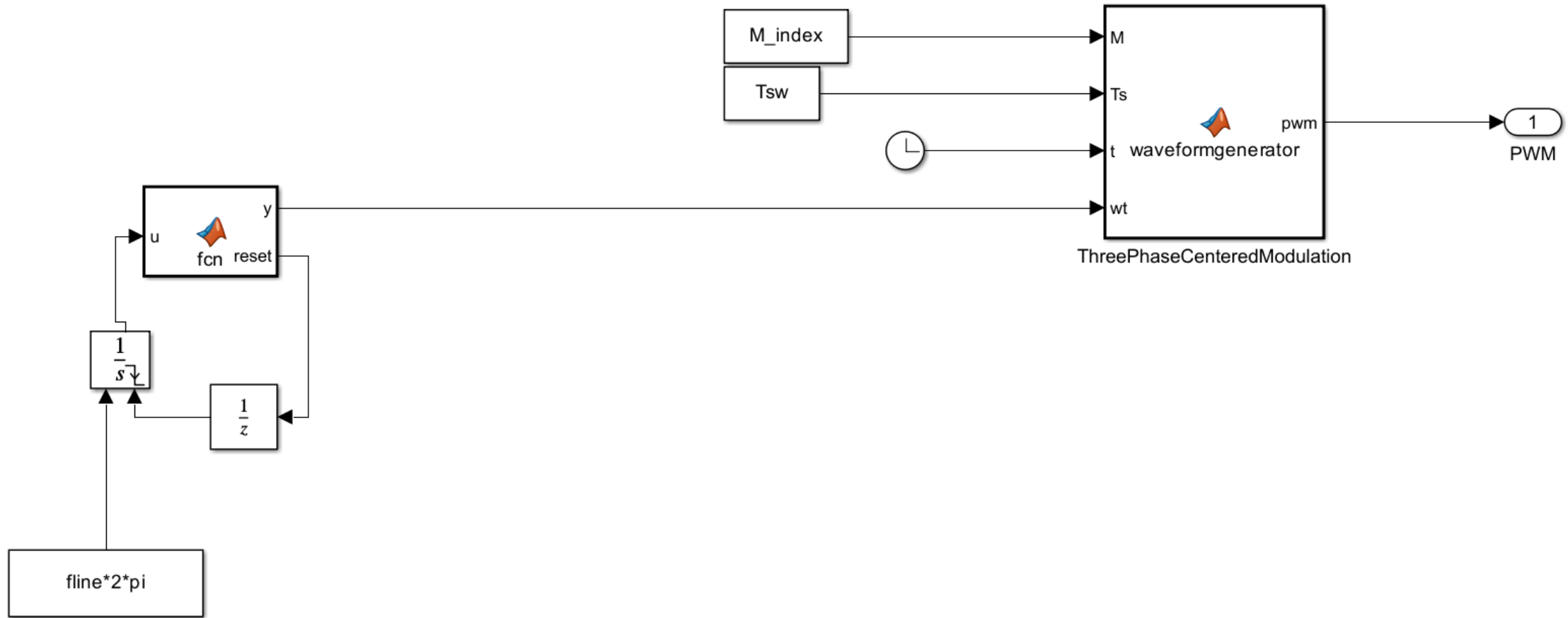

VSI simulation - modulation

```
% inputs: M=modulation index, Ts=switching period, t=simulation time,
% wt=fundamental angle
function pwm = waveformgenerator(M,Ts,t,wt)
```

```
p=[1;0]; n=[0;1];
% find the current sector and relative angle phi
```

```
theta=rem((wt),2*pi)-pi/6;
if theta<0
    theta=theta+2*pi;
end

if theta<(pi/3)
    phi=theta; V1=[p;n;n]; V2=[p;p;n]; % sector 1
elseif theta<(2*pi/3)
    phi=theta-pi/3; V1=[p;p;n]; V2=[n;p;n]; % sector 2
elseif theta<(3*pi/3)
    phi=theta-2*pi/3; V1=[n;p;n]; V2=[n;p;p]; % sector 3
elseif theta<(4*pi/3)
    phi=theta-3*pi/3; V1=[n;p;p]; V2=[n;n;p]; % sector 4
elseif theta<(5*pi/3)
    phi=theta-4*pi/3; V1=[n;n;p]; V2=[p;n;p]; % sector 5
else
    phi=theta-5*pi/3; V1=[p;n;p]; V2=[p;n;n]; % sector 6
end
```

```
V0=[n;n;n];
V7=[p;p;p];
```

```
% find time durations for vectors
T1=M*sin(pi/3-phi)*Ts;
T2=M*sin(phi)*Ts;
T0=Ts-T1-T2;
```

```
% relative time in a switching period
tsec=rem(t,Ts);
```

```
% apply the vectors -- for three phase centered modulation (0127-7210)
if tsec<T0/4
    pwm=V0;
elseif tsec<(T0/4+T1/2)
    pwm=V1;
elseif tsec<(T0/4+T1/2+T2/2)
    pwm=V2;
elseif tsec<(T0/4+T1/2+T2/2+T0/2)
    pwm=V7;
elseif tsec<(T0/4+T1/2+T2/2+T0/2+T2/2)
    pwm=V2;
elseif tsec<(T0/4+T1/2+T2/2+T0/2+T2/2+T1/2)
    pwm=V1;
else
    pwm=V0;
end
```

VSI simulation - modulation

Exercise:

Implement modulation with three phase symmetric (0127210) and two phase symmetric (01210) PWM

- Compare filtered voltage and current waveforms
- Compare common mode voltage waveforms
- Compare unfiltered current waveforms
- Which one is better?

Thank you!